

Problems

Chapter 11

1. An ac power source is connected to an inductor of inductance $L = 15.0\text{H}$. The emf of the power source is given by

$$\mathcal{E} = \mathcal{E}_m \sin(\omega_d t),$$

where $\mathcal{E}_m = 25.0\text{V}$ and $\omega_d = 400\text{rad/sec}$.

- (a) Find the maximum current in the circuit.
 - (b) Find the emf of the source at the time the current is a maximum.
2. An ac power source is connected to a capacitor of capacitance $C = 5.00\mu\text{F}$. The emf of the power source is given by


$$\mathcal{E} = \mathcal{E}_m \sin(\omega_d t),$$

where $\mathcal{E}_m = 25.0\text{V}$ and $\omega_d = 400\text{rad/sec}$.

- (a) Find the maximum current in the circuit.
 - (b) Find the emf of the source at the time the current is a maximum.
3. A series RLC circuit is connected to an ac source of variable frequency. The maximum emf is $\mathcal{E}_m = 10.0\text{V}$, $R = 4.00\Omega$, $L = 2.00\text{H}$ and $C = 2.00\mu\text{F}$.

- (a) Find the resonant frequency of the circuit.
 - (b) Find the amplitude of the voltage across the inductor at resonance.
 - (c) Explain why the voltage across an individual component (inductor) can be greater than the source voltage.
4. A coil of wire has both a resistance and an inductance. The inductance is known to be $L = 0.095\text{H}$, but the resistance is unknown. This coil is connected in series to a capacitor of capacitance $C = 0.90\mu\text{F}$ and an ac source of frequency 1000 Hz . The resulting phase constant is found to be 72° . Find the resistance of the coil.
5. A series RLC circuit is connected to an ac source of $\mathcal{E}_m = 450\text{V}$ and $\omega_d = 950\text{rad/sec}$. $R = 40\Omega$, $L = 0.50\text{H}$ and $C = 2.5\mu\text{F}$.

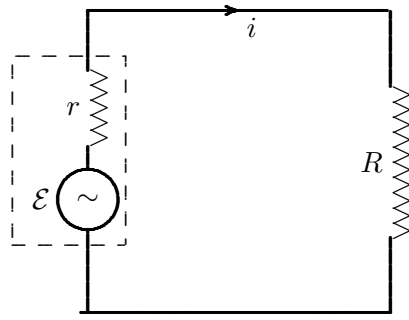- (a) Find the impedance of the circuit.
 - (b) Find the current amplitude of the circuit.
 - (c) Find the phase constant between the emf and the current.
6. The figure below shows an ac power source of emf \mathcal{E} and internal resistance r connected to an external resistance R . Show that maximum power is dissipated across the external resistance if $R = r$.



7. A transformer has a 100V ac power source connected to its primary coil of 500 turns. If the secondary coil has 20 turns, find the secondary coil voltage.