

Name: \_\_\_\_\_

Problem 1 (10 Points)

Design a one-bit 5MR voter using basic gates.

Problem 2 (20 Points)

A cyclic code is to be based on the Generator polynomial  $X^7 + X^5 + X^4 + X^3 + 1$ . Show the logic diagram for the code encoder.

- Generate a codeword for the input data 10011.
- Using logic gates, design an appropriate encoder and decoder the given cyclic code.

Problem 3 (20 Points)

A 2M X 16 memory system is design using 1 M X 4 chips. Assume chip failure modes are single-bit cell (55%), single-row all-0's (25%), single-column all-0's (15%), and whole-chip all-0's (5%). Also, assume 0 and 1 values are equally likely. Compare and comment on relative performance (single-error-detection coverage) and overhead of the following approaches.

- Bit per chip
- Bit per multiple chips
- Duplication
- Single precision checksum (one sum for the entire memory).

Problem 4 (10 Points)

- Draw a block diagram showing the overall structure of a reconfigurable NMR system (i.e. N-modular redundancy with spares) based on hybrid redundancy. Briefly explain how the system tolerates fault.
- Compare and contrast hybrid redundancy with active redundancy scheme. Discuss the main advantages and disadvantages of the two methods.

Problem 5 (20 Points)

Consider a low-cost residue code based on module 7.

- Show how do you obtain residue-7 check bits of  $X_7 X_6 X_5 X_4 X_3 X_2 X_1 X_0$  using recursive addition technique?
- What is the theoretical base for this easy encoding process? Hint: use the weights of bit groups.

Problem 6 (10 Points)

Convert 0 to 14 to RNS using modules [3,5,7]. Within this range would you say a single fault is detectable or not. Justify your answer

Problem 7 (20 Points)

- a. Using full adders and basic gates, design a  $3N$  code encoder, where  $N$  is a 4-bit binary number.
- b. Design a circuit to detect an error in the above  $3N$  code.

Due September 20, 2007