

EGC220

Digital Logic Fundamentals

Design Using Verilog



Baback Izadi

Division of Engineering Programs

bai@enr.newpaltz.edu

Basic Verilog


- Lexical Convention
- Lexical convention are close to C++.
- Comment
 - // to the end of the line.
 - /* to */ across several lines
- Keywords are lower case letter & it is **case sensitive**
- VERILOG uses 4 valued logic: 0, 1, x and z
- **Comments:** // Verilog code for AND-OR-INVERT gate

```
module <module_name> (<module_terminal_list>);  
  <module_terminal_definitions>  
  ...  
  <functionality_of_module>  
  ...  
endmodule
```

Taste of Verilog

```
module Add_half ( Module name sum, c_out, a, b );  
Module ports  
input a, b;  
output sum, c_out;  
wire c_out_bar;  
  
xor (sum, a, b);  
// xor G1(sum, a, b);  
nand (c_out_bar, a, b);  
not (c_out, c_out_bar);  
endmodule
```

Verilog keywords

 

Lexical Convention

- Numbers are specified in the traditional form or below .
 <size><base format><number>
- Size: contains *decimal* digitals that specify the size of the constant in the number of bits.
- Base format: is the single character ' followed by one of the following characters *b(binary), d(decimal), o(octal), h(hex)*.
- Number: legal digital.

Example :

- 347 -- decimal number
- 4'b101 -- 4-bit 0101_2
- 2'o12 -- 2-bit octal number
- 5'h87f7 -- 5-digit $87F7_{16}$
- 2'd83 -- 2-digit decimal
- String in double quotes
 “ this is a introduction”


Three Modeling Styles in Verilog

- Structural modeling (Gate-level)
 - Use predefined or user-defined primitive gates.
- Dataflow modeling
 - Use assignment statements (assign)
- Behavioral modeling
 - Use procedural assignment statements (always)



Structural Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Verilog structural model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_structural(A, B, A_greater_than_B); // 3
  input [1:0] A, B; // 4
  output A_greater_than_B; // 5
  wire B0_n, B1_n, and0_out, and1_out, and2_out; // 6
  not // 7
    inv0(B0_n, B[0]), inv1(B1_n, B[1]); // 8
  and // 9
    and0(and0_out, A[1], B1_n), // 10
    and1(and1_out, A[1], A[0], B0_n), // 11
    and2(and2_out, A[0], B1_n, B0_n); // 12
  or // 13
    or0(A_greater_than_B, and0_out, and1_out, and2_out); // 14
endmodule // 15
```

 

Copyright ©2016 Pearson Education, All Rights Reserved

Dissection

- **Module and Port declarations**
 - Verilog-2001 syntax
 - **module** AOI (input A, B, C, D, output F);
 - Verilog-1995 syntax

```
module AOI (A, B, C, D, F);  
    input A, B, C, D;  
    output F;
```
- **Wires:** Continuous assignment to an internal signal



A Simple Dataflow Design

```
// Verilog code for AND-OR-INVERT gate
```

```
module AOI (input A, B, C, D, output F);
```

```
  wire F; // the default
```

```
  wire AB, CD, O; // necessary
```

```
  assign AB = A & B;
```

```
  assign CD = C & D;
```


```
  assign O = AB | CD;
```

```
  assign F = ~O;
```


```
endmodule
```

```
// end of Verilog code
```

Continuous Assignments

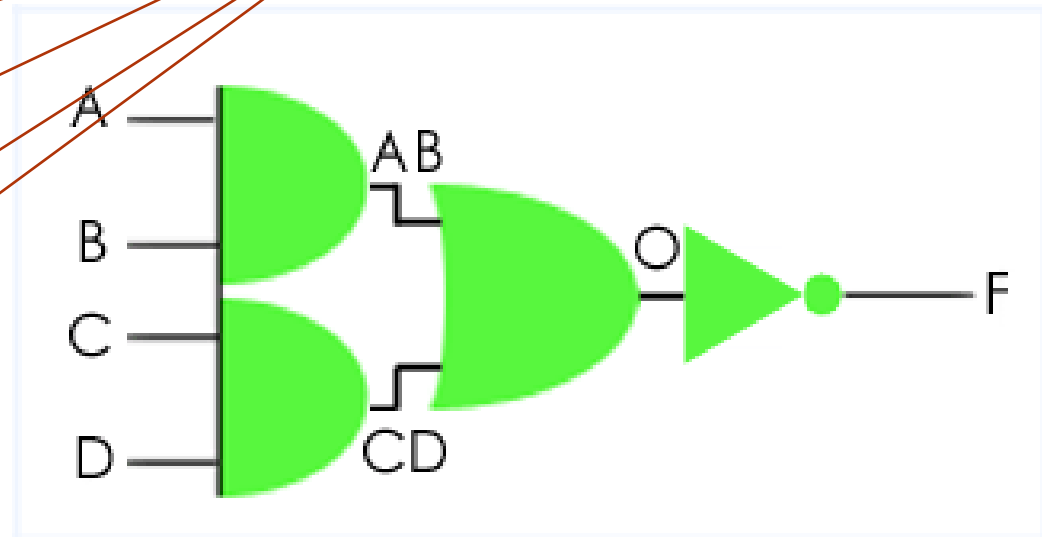

A Simple Dataflow Design

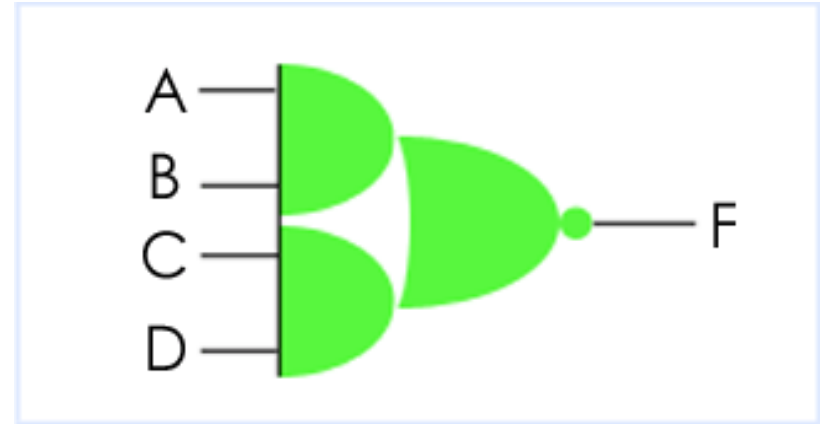

// Verilog code for AND-OR-INVERT gate

```
module AOI (input A, B, C, D, output F);
```

```
    assign F = ~((A & B) | (C & D));
```

```
endmodule
```

// end of Verilog code

'&' for AND, '|' for OR, '^' for XOR '^~' for XNOR, '&~' for NAND

Dataflow Verilog Description of Two-Bit Greater-Than Comparator

```
// Two-bit greater-than circuit: Dataflow model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_dataflow(A, B, A_greater_than_B); // 3
  input [1:0] A, B; // 4
  output A_greater_than_B; // 5
  wire B1_n, B0_n, and0_out, and1_out, and2_out; // 6
  assign B1_n = ~B[1]; // 7
  assign B0_n = ~B[0]; // 8
  assign and0_out = A[1] & B1_n; // 9
  assign and1_out = A[1] & A[0] & B0_n; // 10
  assign and2_out = A[0] & B1_n & B0_n; // 11
  assign A_greater_than_B = and0_out | and1_out | and2_out; // 12
endmodule // 13
```

Copyright ©2016 Pearson Education, All Rights Reserved



Conditional Dataflow Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Conditional model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_conditional2(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B; // 5
    assign A_greater_than_B = (A > B)? 1'b1 : // 6
        1'b0; // 7
endmodule // 8
```

Copyright ©2016 Pearson Education, All Rights Reserved



Verilog Description of Two-Bit Greater-Than Circuit

```
// Two-bit greater-than circuit: Behavioral model // 1
// See Figure 2-27 for logic diagram // 2
module comparator_greater_than_behavioral(A, B, A_greater_than_B); // 3
    input [1:0] A, B; // 4
    output A_greater_than_B; // 5
    assign A_greater_than_B = A > B; // 6
endmodule // 7
```

Copyright ©2016 Pearson Education, All Rights Reserved



A Design Hierarchy

- **Module Instances**

- MUX_2 module contains references to each of the lower level modules


```
// Verilog code for 2-input multiplexer
module MUX2 (input SEL, A, B, output F);
// 2:1 multiplexer
// wires SELB and FB are implicit
// Module instances...
INV G1 (SEL, SELB);
AOI G2 (SELB, A, SEL, B, FB);
INV G3 (.A(FB), .F(F)); // Named mapping
endmodule
// end of Verilog code
```

```
// Verilog code for 2-input multiplexer
module INV (input A, output F); // An inverter
assign F = ~A;
endmodule
```

```
module AOI (input A, B, C, D, output F);
assign F = ~((A & B) | (C & D));
endmodule
```

- $F = (\text{SEL})'.A + (\text{SEL}).B$
 $\text{SELB} = (\text{SEL})'$
 $F = (\text{SELB}).A + (\text{SEL}).B$
1. Invert SEL and get SELB
 2. Use AOI and get F'
 3. Invert F' and get F

MUX_2

 

Another Example

```
module decoder (A,B, D0,D1,D2,D3);
```

```
input A,B;
```

```
output D0,D1,D2,D3;
```

```
assign D0 = ~A&~B;
```

```
assign D1 = ~A&B;
```

```
assign D2 = A&~B;
```

```
assign D3 = A&B;
```

```
endmodule
```


 


Figure 6. Logic diagram of 2-to-4 decoder

Hierarchical representation of Adder

```
module fulladder (A,B,CIN, S,COOUT);  
input A,B,CIN;  
output S,COOUT;  
assign S = A ^ B ^ CIN;  
assign COOUT = (A & B) | (A & CIN)  
| (B & CIN);  
endmodule
```

 

Logic diagram of full adder

```

module four_bit_adder (CIN, X3,X2,X1,X0,Y3,Y2,Y1,Y0, S3,S2,S1,S0,COOUT);
input  CIN, X3, X2, X1, X0,Y3,Y2,Y1,Y0;
output S3, S2, S1, S0, COOUT;
wire  C1, C2, C3;
fulladder FA0 (X0,Y0, CIN, S0, C1);
fulladder FA1 (X1,Y1, C1, S1, C2);
fulladder FA2 (X2,Y2, C2, S2, C3);
fulladder FA3 (X3,Y3, C3, S3, COOUT);
endmodule

```


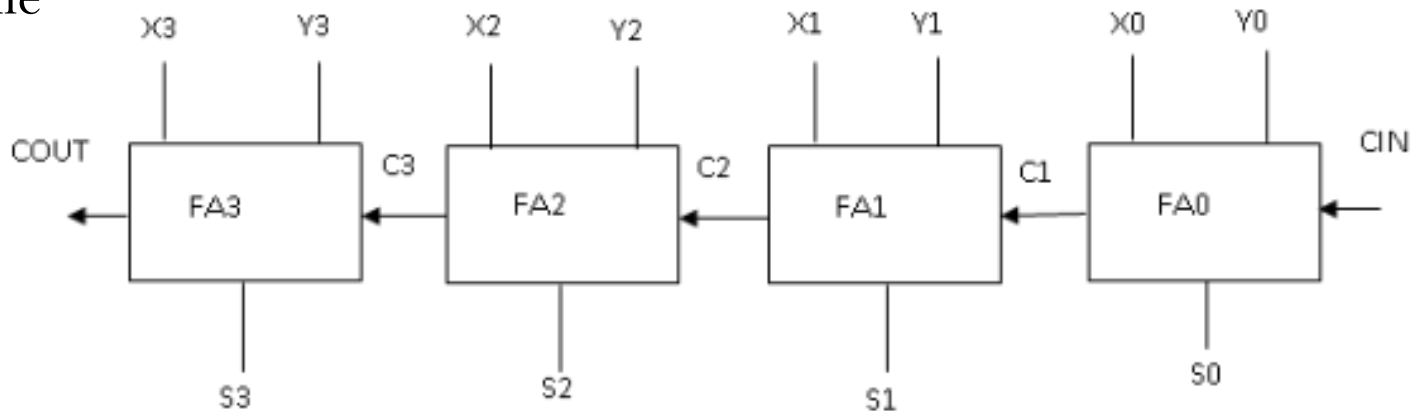


Figure9. Four bit Full Adder


```

module adder_4 (A, B, CIN, S ,COUT);
input [3:0] A,B;
input CIN;
output [3:0] S;
output COUT;
wire [4:0] C;
full_adder FA0 (B(0), A(0), C(0), S(0), C(1));
full_adder FA1 (B(1), A(1), C(1), S(1), C(2));
full_adder FA2 (B(2), A(2), C(2), S(2), C(3));
full_adder FA3 (B(3), A(3), C(3), S(3), C(4));
assign C(0) = CIN;
assign COUT = C(4);
endmodule

```

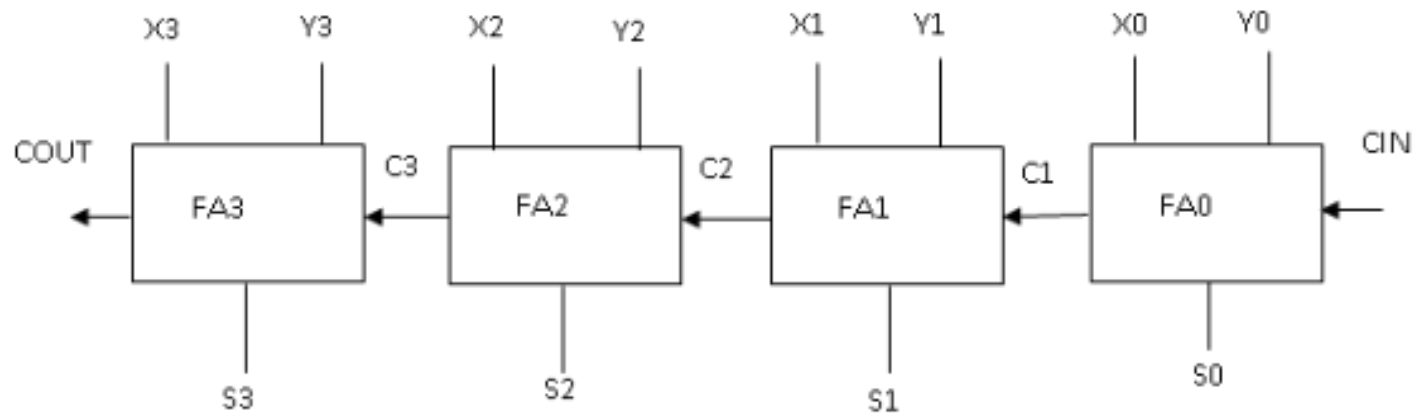

Verilog Statements

Verilog has two basic types of statements

1. Concurrent statements (combinational)

(things are happening concurrently, ordering does not matter)

- Gate instantiations
 - **and** (z, x, y), **or** (c, a, b), **xor** (S, x, y), etc.
- Continuous assignments
 - **assign** Z = x & y; c = a | b; S = x ^ y


2. Procedural statements (sequential)

(executed in the order written in the code)

- **always @** - executed continuously when the event is active
- **Initial** - executed only once (used in simulation)
- **if then else** statements

Behavioral Description
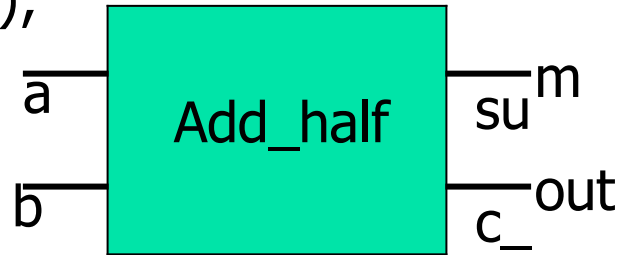
```
module Add_half ( sum, c_out, a, b );  
  input    a, b;  
  output   sum, c_out;  
  reg sum, c_out;  
  always @ ( a or b )  
  begin  
    sum = a ^ b;           // Exclusive or  
    c_out = a & b;         // And  
  end  
endmodule
```



Must be of the
'reg' type

Procedure
assignment
statements

Event control
expression or
sensitivity list

Conditional Statement

- Conditional_expression ? true_expression : false expression;

Example:

- Assign $A = (B < C) ? (D + 5) : (D + 2);$
 - if B is less than C, the value of A will be D + 5, or else A will have the value D + 2.

- An **if-else** statement is a procedural statement.

```
// Behavioral specification
module mux2to1 (w0, w1, s, F);
input w0, w1, s;
output F;
reg F;
```

```
always @ (w0,w1,s)
if (s==1) F = w1;
else F = w0;
endmodule
```

```
always @ (w0,w1,s)
F = s ? w1 : w2;
endmodule
```

sensitivity list

Mux 4-to-1

```
module mux4to1 (w0, w1, w2, w3, S, F);  
input w0, w1, w2, w3, [1:0] S;  
output F;  
reg F;  
always @ (w0, w1, w2, w3, S)  
if (S==0) F = w0;  
else if (S==1) F = w1;  
else if (S==2) F = w2;  
else F = w3;  
endmodule
```

Verilog Operator	Name	Functional Group
> >= < <=	greater than greater than or equal to less than less than or equal to	relational
== !=	case equality case inequality	equality
& ^	bit-wise AND bit-wise XOR bit-wise OR	bit-wise bit-wise
&&	logical AND logical OR	logical

Another Example

```
//Dataflow description of a 4-bit comparator.  
module mag_comp (A,B,ALTB,AGTB,AEQB);  
input [3:0] A,B;  
output ALTB,AGTB,AEQB;  
assign ALTB = (A < B),  
AGTB = (A > B),  
AEQB = (A == B);  
endmodule
```



Dataflow Modeling

```
//Dataflow description of 4-bit adder  
module binary_adder (A, B, Cin, SUM, Cout);  
input [3:0] A,B;  
input Cin;  
output [3:0] SUM;  
output Cout;  
assign {Cout, SUM} = A + B + Cin;  
endmodule
```

concatenation


Binary addition

Design of an ALU using Case Statement

S	Function
0	Clear
1	B-A
2	A-B
3	A+B
4	A XOR B
5	A OR B
6	A AND B
7	Set to all 1's

```
// 74381 ALU
module alu(s, A, B, F);
input [2:0] s;
input [3:0] A, B;
output [3:0] F;
reg [3:0] F;
always @(s or A or B)
case (s)
0: F = 4'b0000;
1: F = B - A;
2: F = A - B;
3: F = A + B;
4: F = A ^ B;
5: F = A | B;
6: F = A & B;
7: F = 4'b1111;
endcase
endmodule
```



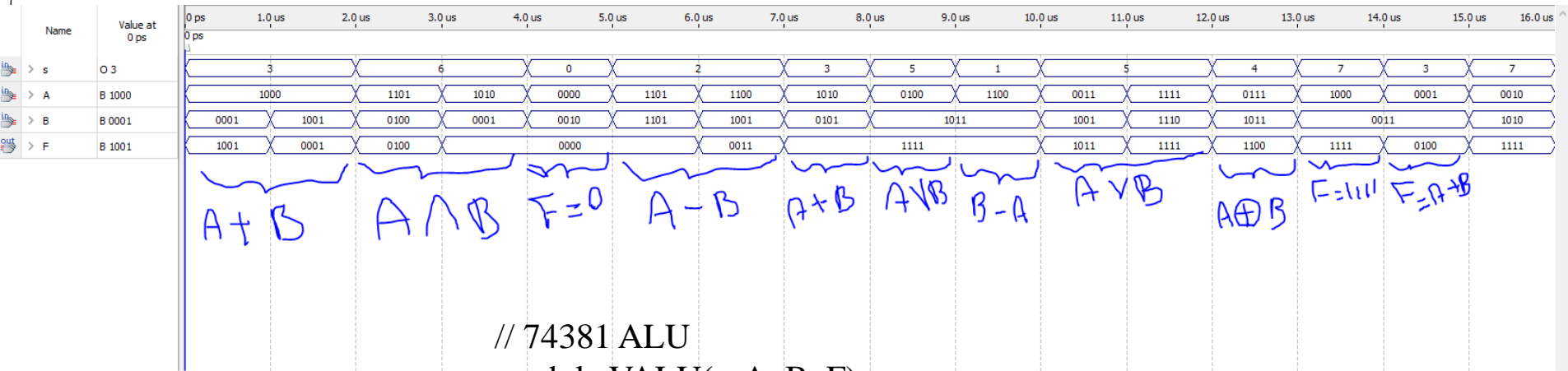

```
// 74381 ALU
module VALU(s, A, B, F);
input [2:0] s;
input [3:0] A, B;
output [3:0] F;
reg [3:0] F;
always @(s or A or B)
case (s)
0: F = 4'b0000;
1: F = B - A;
2: F = A - B;
3: F = A + B;
4: F = A ^ B;
5: F = A | B;
6: F = A & B;
7: F = 4'b1111;
endcase
endmodule
```



Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within *always* blocks, with subtly different behaviors.
- Blocking assignment*: evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
  x = a | b;           1. Evaluate a | b, assign result to x
```

```
  y = a ^ b ^ c;      2. Evaluate a^b^c, assign result to y
```

```
  z = b & ~c;         3. Evaluate b&(~c), assign result to z
```

```
end
```

- Nonblocking assignment*: all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
  x.<= a | b;          1. Evaluate a | b but defer assignment of x
```

```
  y.<= a ^ b ^ c;      2. Evaluate a^b^c but defer assignment of y
```

```
  z <= b & ~c;         3. Evaluate b&(~c) but defer assignment of z
```

```
end
```

```
  4. Assign x, y, and z with their new values
```

- Sometimes, as above, both produce the same result. Sometimes, not!

Blocking vs. Nonblocking Assignments

- The `=` token represents a blocking procedural assignment
 - ✓ Evaluated and assigned in a single step
 - ✓ Execution flow within the procedure is blocked until the assignment is completed
- The `<=` token represents a non-blocking assignment
 - ✓ Evaluated and assigned in two steps:
 1. The right hand side is evaluated immediately
 2. The assignment to the left-hand side is postponed until other evaluations in the current time step are completed

```
//swap bytes in word  
always @(posedge clk)  
begin  
word[15:8] = word[ 7:0];  
word[ 7:0] = word[15:8];  
end
```

```
//swap bytes in word  
always @(posedge clk)  
begin  
word[15:8] <= word[ 7:0];  
word[ 7:0] <= word[15:8];  
end
```

Why two ways of assigning values?

Conceptual need for **two kinds** of **assignment** (in always blocks):

<p>Blocking: Evaluation and assignment are immediate</p>	 $a = b$ $b = a$ 	$x = a \& b$ $y = x c$
<p>Non-Blocking: Assignment is postponed until all r.h.s. evaluations are done</p>	$a \leq b$ $b \leq a$	 $x \leq a \& b$ $y \leq x c$
<p>When to use: (only in always blocks!)</p>	<p>Sequential Circuits</p>	<p>Combinational Circuits</p>

Golden Rules

- **Golden Rule 1:**

- *To synthesize combinational logic using an always block, all inputs to the design must appear in the sensitivity list.*


- **Golden Rule 2:**

- *To synthesize combinational logic using an always block, all variables must be assigned under all conditions.*



Golden Rules
 
```
reg f;  
always @ (sel, a, b)  
begin :  
  if (sel == 1)  
    f = a;  
  else  
    f = b;  
end
```




- Proper as intended

```
Reg f;  
always @ (sel, a, b)  
begin f = b;  
  if (sel == 1)  
    f = a;  
end
```

- Setting variables to default values at the start of the always block
- OK as well!
 
```
reg f;  
always @ (sel, a)  
begin :  
  if (sel == 1)  
    f = a;  
end
```



- What if sel = 0?
 - Keep the current value
- Undesired functionality
 - Unintended latch
- Need to include else

Verilog Operator	Name	Functional Group	Verilog Operator	Name	Functional Group
[]	bit-select or part-select		+	binary plus	arithmetic
			-	binary minus	arithmetic
()	parenthesis		<<	shift left	shift
!	logical negation	logical	>>	shift right	shift
~	negation	bit-wise	>	greater than	relational
&	reduction AND	reduction	>=	greater than or equal	relational
	reduction OR	reduction	<	to	relational
~&	reduction NAND	reduction	<=	less than	relational
~	reduction NOR	reduction		less than or equal to	
^	reduction XOR	reduction	==	case equality	equality
~^ or ^~	reduction XNOR	reduction	!=	case inequality	equality
+	unary (sign) plus	arithmetic	&	bit-wise AND	bit-wise
-	unary (sign) minus	arithmetic	^	bit-wise XOR	bit-wise
{ }	concatenation	concatenation		bit-wise OR	bit-wise
{ { } }	replication	replication	&&	logical AND	logical
*	multiply	arithmetic		logical OR	logical
/	divide	arithmetic	?:	conditional	conditional
%	modulus	arithmetic			

Appendix



Arithmetic in Verilog

```
module Arithmetic (A, B, Y1, Y2, Y3, Y4, Y5);  
    input [2:0] A, B;  
    output [3:0] Y1;  
    output [4:0] Y3;  
    output [2:0] Y2, Y4, Y5;  
    reg [3:0] Y1;  
    reg [4:0] Y3;  
    reg [2:0] Y2, Y4, Y5;  
    always @(A or B)  
    begin  
        Y1=A+B; //addition  
        Y2=A-B; //subtraction  
        Y3=A*B; //multiplication  
        Y4=A/B; //division  
        Y5=A%B; //modulus of A divided by B  
    end  
endmodule
```

Sign Arithmetic in Verilog

```
module Sign (A, B, Y1, Y2, Y3);  
  
    input [2:0] A, B;  
    output [3:0] Y1, Y2, Y3;  
    reg [3:0] Y1, Y2, Y3;  
  
    always @(A or B)  
    begin  
        Y1 = +A / -B;  
        Y2 = -A + -B;  
        Y3 = A * -B;  
    end  
endmodule
```



Equality and inequality Operations in Verilog

```
module Equality (A, B, Y1, Y2, Y3);  
    input [2:0] A, B;  
    output Y1, Y2;  
    output [2:0] Y3;  
    reg Y1, Y2;  
    reg [2:0] Y3;  
    always @(A or B)  
    begin  
        Y1=A==B; //Y1=1 if A equivalent to B  
        Y2=A!=B; //Y2=1 if A not equivalent to B  
        if (A==B) //parenthesis needed  
            Y3=A;  
        else  
            Y3=B;  
    end  
endmodule
```

Logical Operations in Verilog

```
module Logical (A, B, C, D, E, F, Y);  
    input [2:0] A, B, C, D, E, F;  
    output Y;  
    reg Y;  
    always @(A or B or C or D or E or F)  
    begin  
        if ((A==B) && ((C>D) || !(E<F)))  
            Y=1;  
        else  
            Y=0;  
    end  
endmodule
```



Bit-wise Operations in Verilog

```
module Bitwise (A, B, Y);  
    input [6:0] A;  
    input [5:0] B;  
    output [6:0] Y;  
    reg [6:0] Y;  
    always @(A or B)  
    begin  
        Y[0]=A[0]&B[0]; //binary AND  
        Y[1]=A[1]|B[1]; //binary OR  
        Y[2]=!(A[2]&B[2]); //negated AND  
        Y[3]=!(A[3]|B[3]); //negated OR  
        Y[4]=A[4]^B[4]; //binary XOR  
        Y[5]=A[5]~^B[5]; //binary XNOR  
        Y[6]=!A[6]; //unary negation  
    end
```

endmodule

. Concatenation and Replication in Verilog

- The concatenation operator "{ , }" combines (concatenates) the bits of two or more data objects. The objects may be scalar (single bit) or vectored (multiple bit). Multiple concatenations may be performed with a constant prefix and is known as replication.

```
module Concatenation (A, B, Y);  
    input [2:0] A, B;  
    output [14:0] Y;  
    parameter C=3'b011;  
    reg [14:0] Y;  
    always @(A or B)  
    begin  
        Y = {A, B, {2{C}}, 3'b110};  
    end  
endmodule
```

Shift Operations in Verilog

```
module Shift (A,Y1,Y2);  
    input [7:0] A;  
    output [7:0]Y1,Y2;  
    parameter B=3; reg [7:0]Y1,Y2;  
    always @(A)  
    begin  
        Y1=A<<B; //logical shift left  
        Y2=A>>B; //logical shift right  
    end  
endmodule
```



Conditional Operations in Verilog

```
module Conditional (Time,Y);  
    input [2:0]Time;  
    output [2:0]Y;  
    reg [2:0]Y;  
    parameter Zero =3b'000;  
    parameter TimeOut = 3b'110;  
    always @(Time)  
    begin  
        Y=(Time!=TimeOut) ?Time +1 : Zero;  
    end  
endmodule
```



Reduction Operations in Verilog

```
module Reduction (A,Y1,Y2,Y3,Y4,Y5,Y6);  
    input [3:0] A;  
    output Y1,Y2,Y3,Y4,Y5,Y6;  
    reg Y1,Y2,Y3,Y4,Y5,Y6;  
    always @(A)  
    begin  
        Y1=&A; //reduction AND  
        Y2=|A; //reduction OR  
        Y3=~&A; //reduction NAND  
        Y4=~|A; //reduction NOR  
        Y5=^A; //reduction XOR  
        Y6=~^A; //reduction XNOR  
    end  
endmodule
```

Stimulus module

Design module

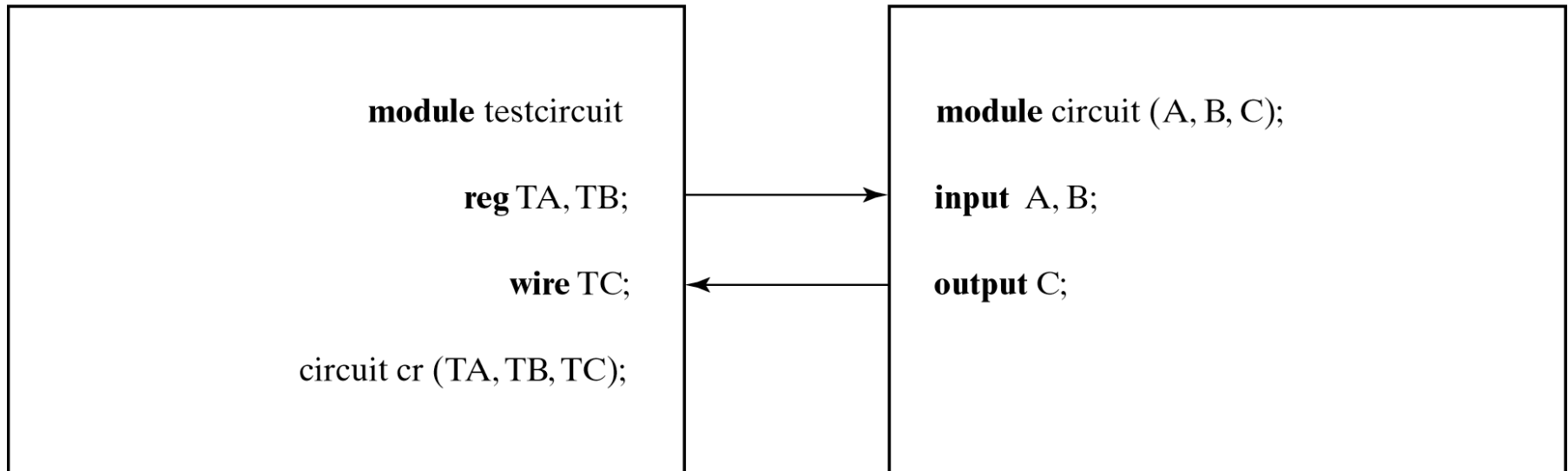


Fig. 4-33 Stimulus and Design Modules Interaction




Testbench for the Structural Model of the Two-Bit Greater-Than Comparator

```
// Testbench for Verilog two-bit greater-than comparator // 1
module comparator_testbench_verilog(); // 2
  reg [1:0] A, B; // 3
  wire struct_out; // 4
  comparator_greater_than_structural U1(A, B, struct_out); // 5
  initial // 6
  begin // 7
    A = 2'b10; // 8
    B = 2'b00; // 9
    #10; // 10
    B = 2'b01; // 11
    #10; // 12
    B = 2'b10; // 13
    #10; // 14
    B = 2'b11; // 15
  end // 16
endmodule // 17
```

Copyright ©2016 Pearson Education, All Rights Reserved




Propagation Delay for an Inverter

 

Copyright ©2016 Pearson Education, All Rights Reserved



Circuit to demonstrate an HDL (Verilog)

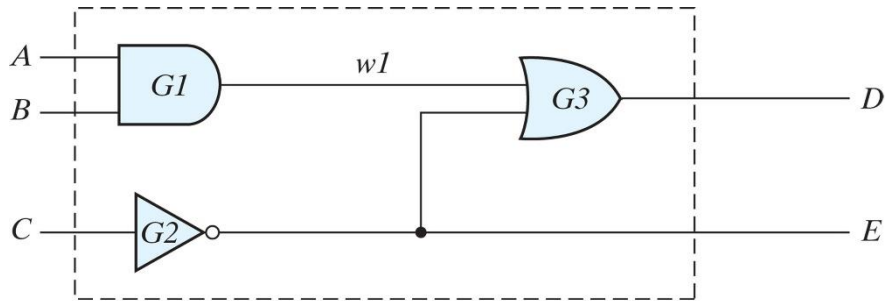


```

Module simpl_Circuit (A, B, C, D, E)
  input A, B, C;
  output D, E;
  wire w1;
  and # (30) G1 (w1, A, B);
  not #10 G2 (E, C);
  or #(20) G3 (D, w1, E);
endmodule
  
```

Table 3.5
Output of Gates after Delay

	Time Units (ns)	Input	Output		
		ABC	E	w1	D
Initial	—	0 0 0	1	0	1
Change	—	1 1 1	1	0	1
	10	1 1 1	0	0	1
	20	1 1 1	0	0	1
	30	1 1 1	0	1	0
	40	1 1 1	0	1	0
	50	1 1 1	0	1	1

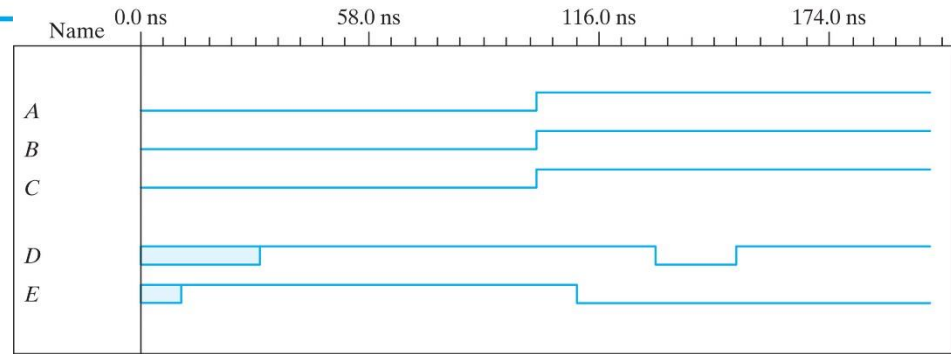

Copyright ©2012 Pearson Education, publishing as Prentice Hall

Copyright ©2013 Pearson Education, publishing as Prentice Hall

Interaction between stimulus and design modules

```
module t_circuit;  
  reg t_A, t_B;  
  wire t_C;  
  parameter stop_time = 1000 ;  
  
  circuit M ( t_C, t_A, t_B );  
  
  // Stimulus generators for  
  // t_A and t_B go here  
  initial # stop_time $finish;  
endmodule
```

```
module circuit ( C, A, B )  
  
  input      A, B;  
  
  output    C;  
  
  // Description goes here  
endmodule
```

Copyright ©2013 Pearson Education, publishing as Prentice Hall