 


Figure 4-3 Synchronous Clocked Sequential Circuit



(a) Block diagram




(b) Timing diagram of clock pulses

Table 4-1 Flip-Flop Characteristic Table

(a) JK Flip-Flop				(b) SR Flip-Flop			
J	K	$Q(t+1)$	Operation	S	R	$Q(t+1)$	Operation
0	0	$Q(t)$	No change	0	0	$Q(t)$	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	$\overline{Q}(t)$	Complement	1	1	?	Undefined

(c) D Flip-Flop			(d) T Flip-Flop		
D	$Q(t+1)$	Operation	T	$Q(t+1)$	Operation
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$\overline{Q}(t)$	Complement

 Figure 4-16 *JK* Flip-Flop with Direct Set and Reset


(a) Graphic symbols

S	R	C	J	K	Q	\bar{Q}
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	Undefined	
1	1	↑	0	0	No change	
1	1	↑	0	1	0	1
1	1	↑	1	0	1	0
1	1	↑	1	1	Complement	

(b) Function table

Analysis Procedure:

1. Obtain flip-flop input equations
2. Write down characteristic table of each type of flip-flop in use
3. Develop state table
4. Obtain state diagram

 □ **Example #1:****Step 1: Flip-flop input equations and output equation**

$$J_A = X$$

$$K_A = Q_B \oplus X = Q_B \odot X$$

$$J_B = Q_A X'$$


$$K_B = Q_A X$$

Step 2: Characteristic Table


J K	Q(t+1)
0 0	Q(t)
0 1	0
1 0	1
1 1	Q'(t)

Step 3: State Table

PS Q _A Q _B X	J _A	K _A	J _B	K _B	NS Q _A Q _B
000	0	1	0	0	00
001	1	0	0	0	10
010	0	0	0	0	01
011	1	1	0	0	11
100	0	1	1	0	01
101	1	0	0	1	10
110	0	0	1	0	11
111	1	1	0	1	00

 Step 4: State Diagram

□ **Example #2:**

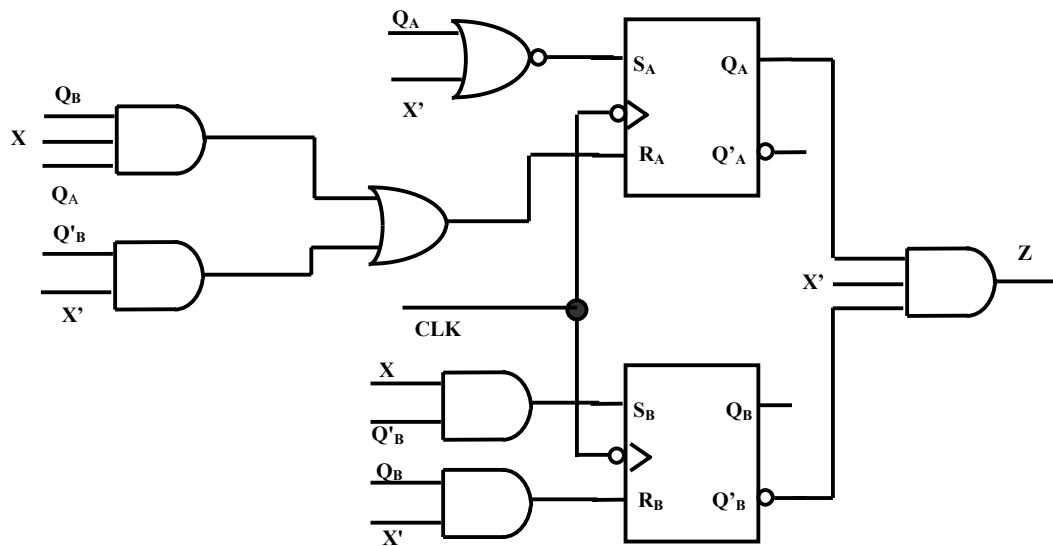

Step 1: Flip-flop input equations and output equation

$$S_A = (Q_A + X)' = Q'_A X$$

$$R_A = Q_A Q_B X + Q'_B X'$$

$$S_B = Q'_B X$$

$$R_B = Q_B X'$$

$$Z = Q_A Q'_B X'$$

Step 2: Characteristic Table

S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	-

Step 3: State Table

PS Q _A Q _B X	S _A	R _A	S _B	R _B	NS Q _A Q _B	Z
000	0	1	0	0	00	0
001	1	0	1	0	11	0
010	0	0	0	1	00	0
011	1	0	0	0	11	0
100	0	1	0	0	00	1
101	0	0	1	0	11	0
110	0	0	0	1	10	0
111	0	1	0	0	01	0

 
 
Step 4: State Diagram


Figure 4-19 Logic Diagram and State Table for $D_A = A \oplus X \oplus Y$ 

(a)

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b) State table

□ **Example #3:**

 

Step 1: Flip-flop input equations

$$D_A = Q_B Q_C Q_D + Q_A Q_D'$$

$$D_B = Q_B' Q_C Q_D + Q_B Q_C' + Q_B Q_D'$$

$$D_C = Q_A' Q_C' Q_D + Q_C Q_D'$$

$$D_D = Q_D'$$

Step 2: Characteristic Table

D	Q(t+1)
0	0
1	1

Step 3: State Table

PS Q_AQ_BQ_CQ_D	D_A	D_B	D_C	D_D	NS Q_AQ_BQ_CQ_D
0 0 0 0	0	0	0	1	0 0 0 1
0 0 0 1	0	0	1	0	0 0 1 0
0 0 1 0	0	0	1	1	0 0 1 1
0 0 1 1	0	1	0	0	0 1 0 0
0 1 0 0	0	1	0	1	0 1 0 1
0 1 0 1	0	1	1	0	0 1 1 0
0 1 1 0	0	1	1	1	0 1 1 1
0 1 1 1	1	0	0	0	1 0 0 0
1 0 0 0	1	0	0	1	1 0 0 1
1 0 0 1	0	0	0	0	0 0 0 0
1 0 1 0	1	0	1	1	1 0 1 1
1 0 1 1	0	1	0	0	0 1 0 0
1 1 0 0	1	1	0	1	1 1 0 1
1 1 0 1	0	1	0	0	0 1 0 0
1 1 1 0	1	1	1	1	1 1 1 1
1 1 1 1	1	0	0	0	1 0 0 0

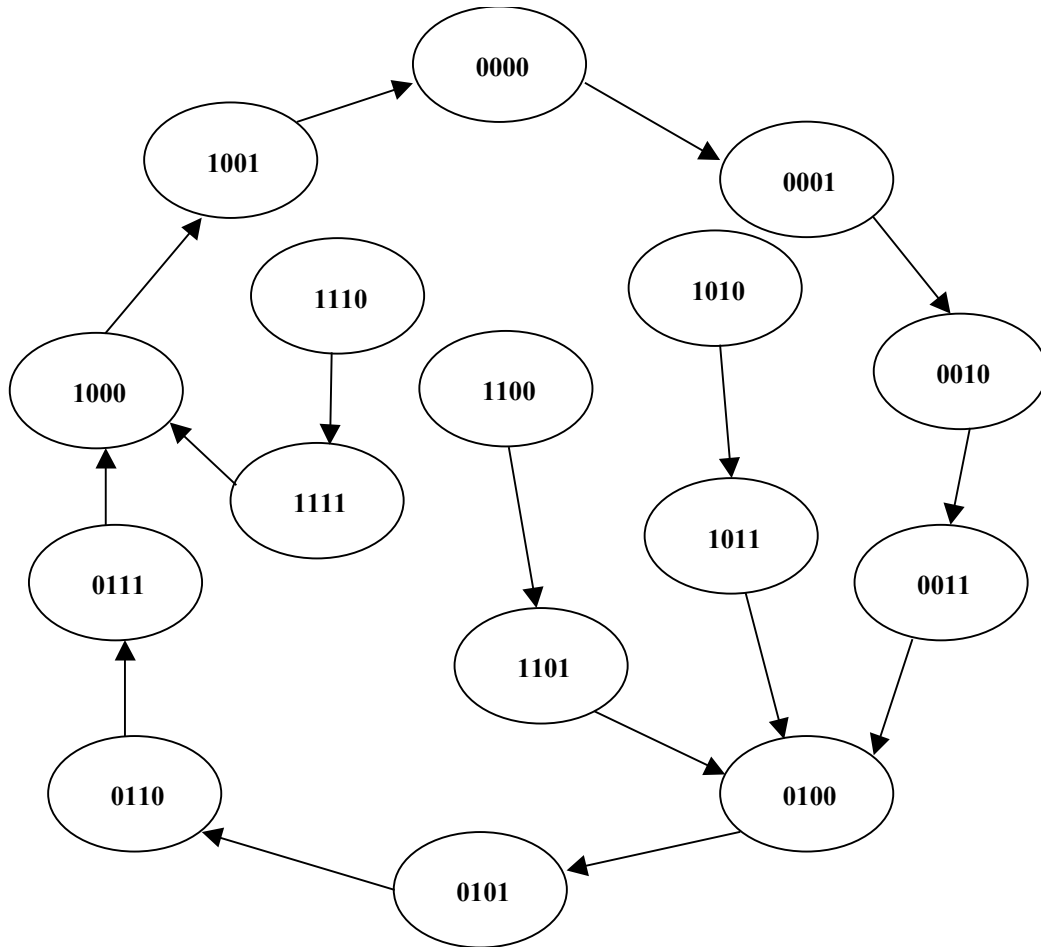
Step 4: State Diagram

Table 4-10 Flip-Flop Excitation Table

(a) <i>JK</i> Flip-Flop				(b) <i>SR</i> Flip-Flop			
$Q(t)$	$Q(t+1)$	J	K	$Q(t)$	$Q(t+1)$	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0

(c) <i>D</i> Flip-Flop			(d) <i>T</i> Flip-Flop		
$Q(t)$	$Q(t+1)$	D	$Q(t)$	$Q(t+1)$	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0