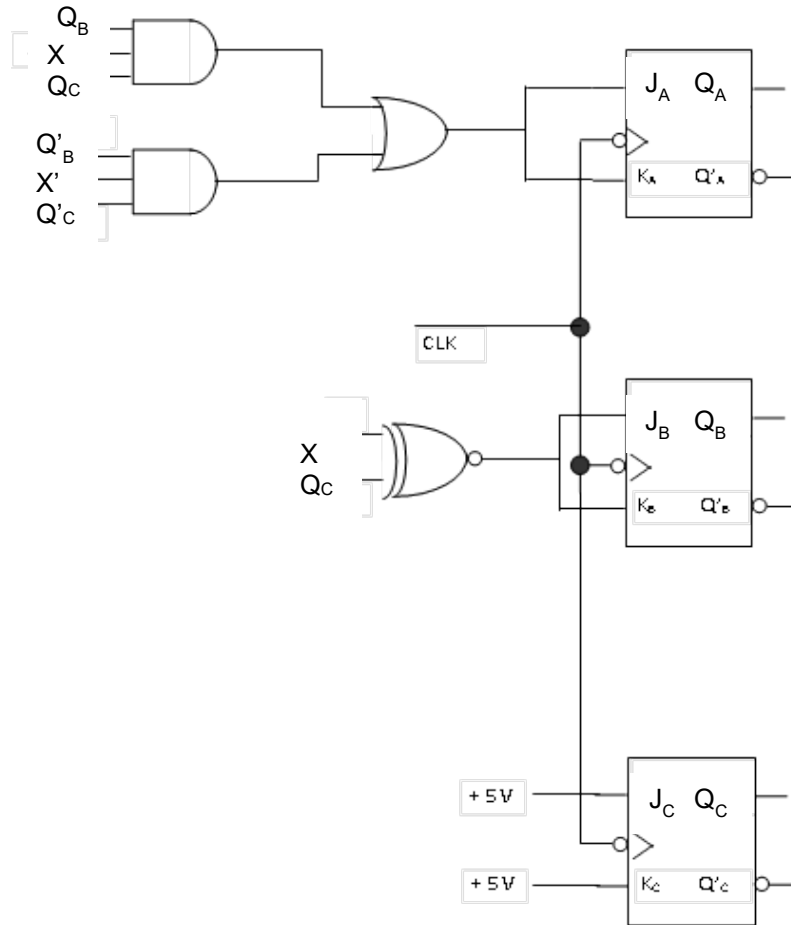


First Name: \_\_\_\_\_ Last Name: \_\_\_\_\_

20 Points

Problem 1


Analyze the following sequential circuits leading to a state diagram.



20 Points

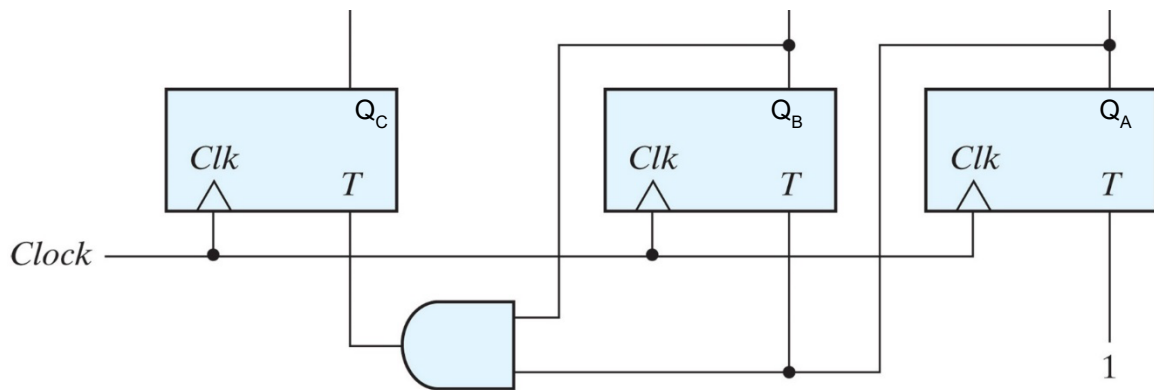Problem 2


Analyze the following sequential circuits leading to a state diagram.



20 Points

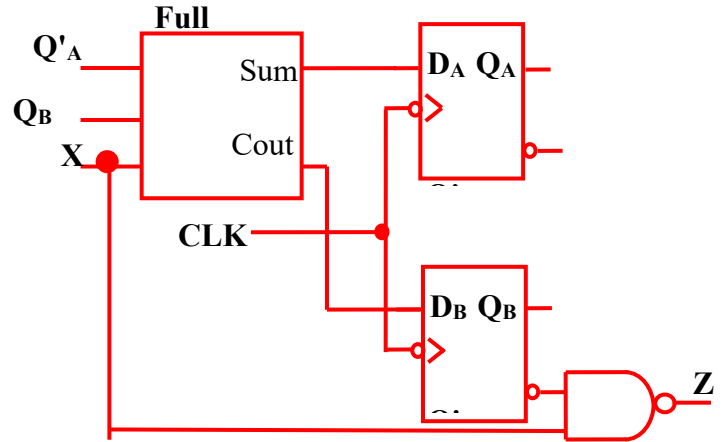Problem 3

Analyze the following circuit leading to its state diagram.



20 Points


Problem 4

Using JK flip flops, design an up/down synchronous counter that counts from 3 to 6.

20 Points

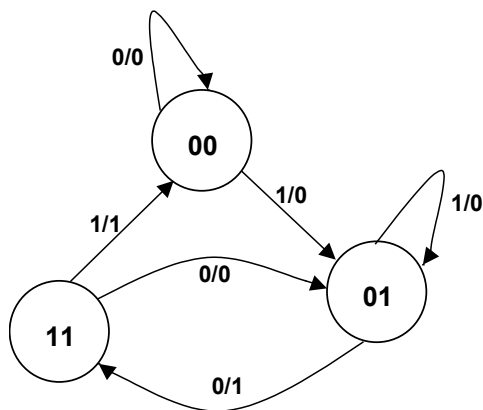Problem 5


Using JK flip-flops, design a circuit for the following state diagram.



20 Points

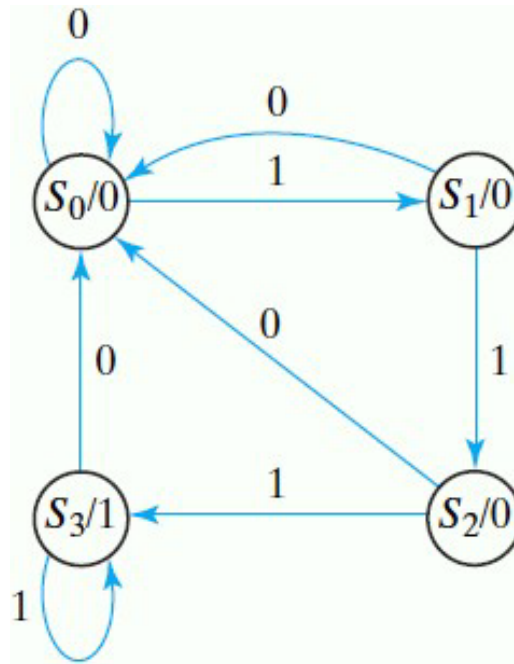Problem 6

Using T flip-flops, design a circuit for the following state diagram. You may make the following state assignments:  $S_0 = 00$ ,  $S_1 = 10$ ,  $S_2 = 11$ ,  $S_3 = 01$



25 Points

Problem 7

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume no overlapping, namely 10101 generates output 00100.

25 Points


Problem 8

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume overlapping of sequence is allowed, namely 10101 generates output 00101.

25 Points

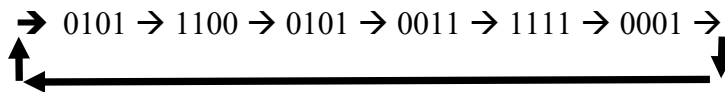Problem 9

Using D flip flops, design a circuit to generate the following sequence.



Your design should be race free.

Due 5/2/2023