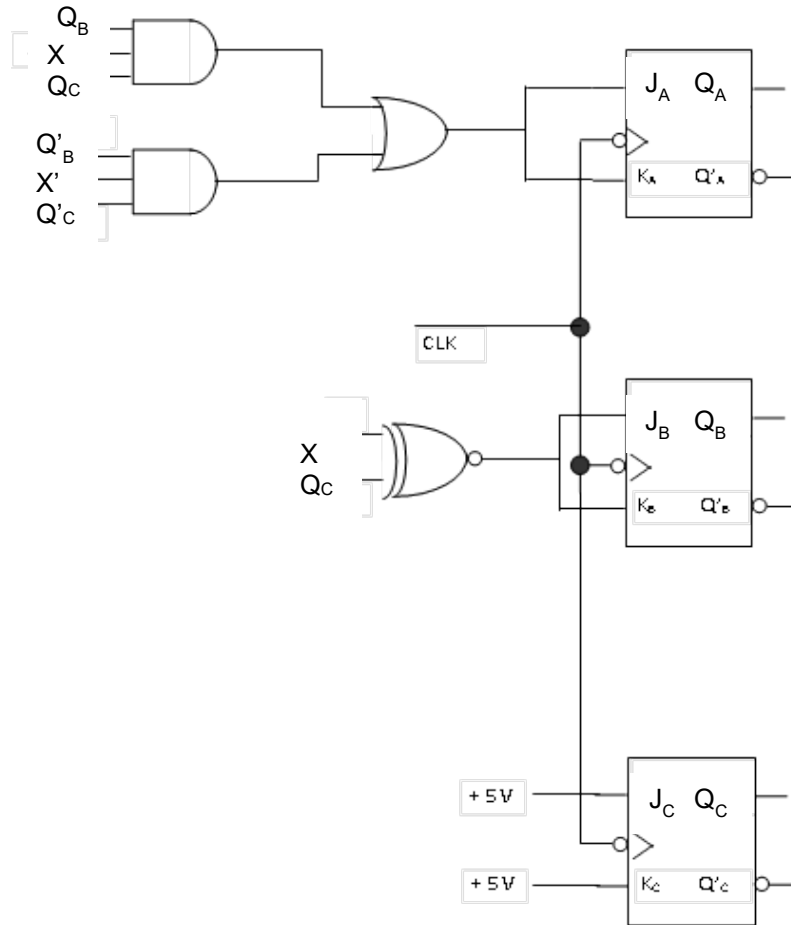


First Name: _____ Last Name: _____

20 Points

Problem 1


Analyze the following sequential circuits leading to a state diagram.



20 Points

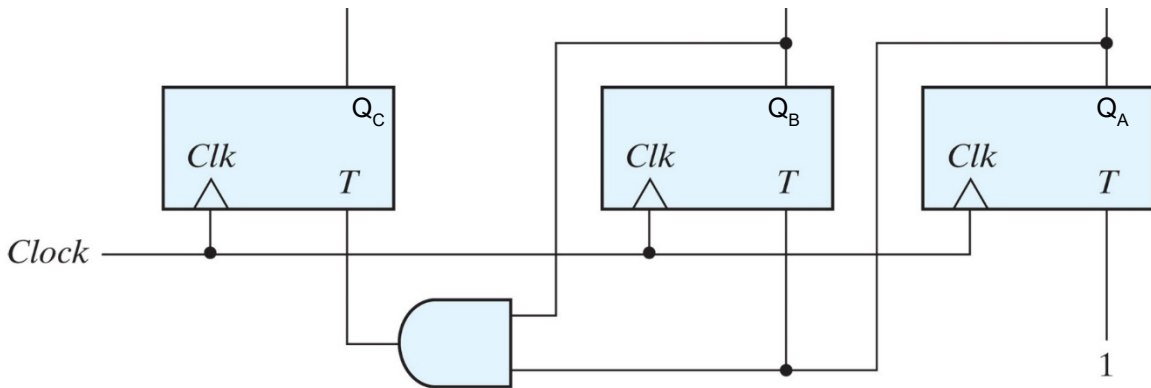Problem 2


Analyze the following sequential circuits leading to a state diagram.



20 Points

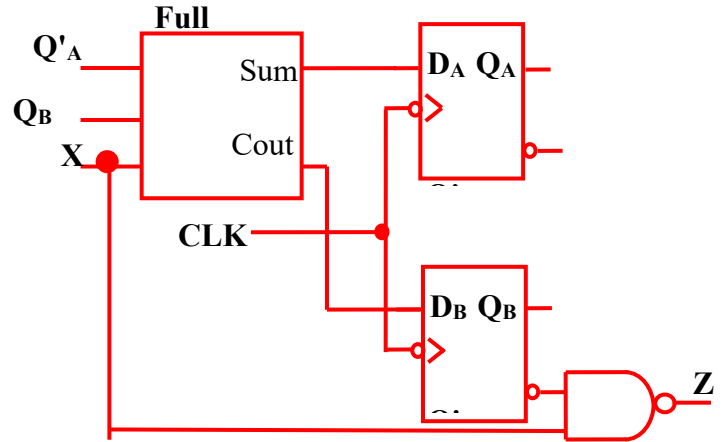Problem 3

Analyze the following circuit leading to its state diagram.



20 Points


Problem 4

Using JK flip flops, design an up/down synchronous counter that counts from 3 to 6.

20 Points

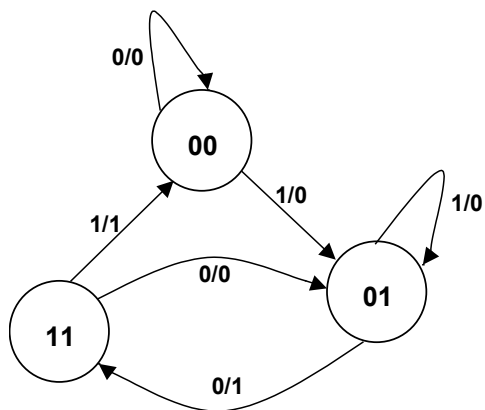Problem 5


Using JK flip-flops, design a circuit for the following state diagram.



20 Points

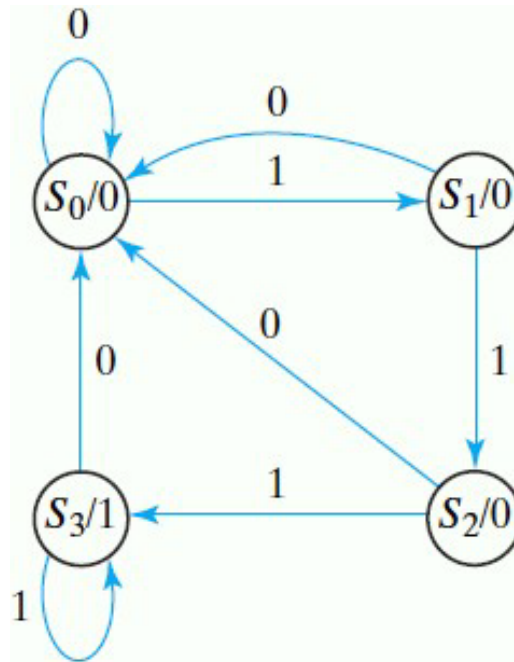Problem 6

Using T flip-flops, design a circuit for the following state diagram. You may make the following state assignments: $S_0 = 00$, $S_1 = 10$, $S_2 = 11$, $S_3 = 01$



25 Points

Problem 7

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume no overlapping, namely 10101 generates output 00100.

25 Points


Problem 8

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume overlapping of sequence is allowed, namely 10101 generates output 00101.

25 Points

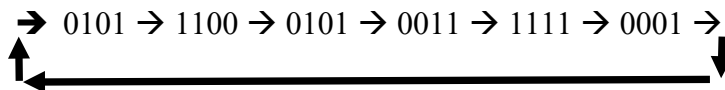Problem 9

Using D flip flops, design a circuit to generate the following sequence.



Your design should be race free.


Due 5/2/2023

First Name: Key Last Name: _____

20 Points

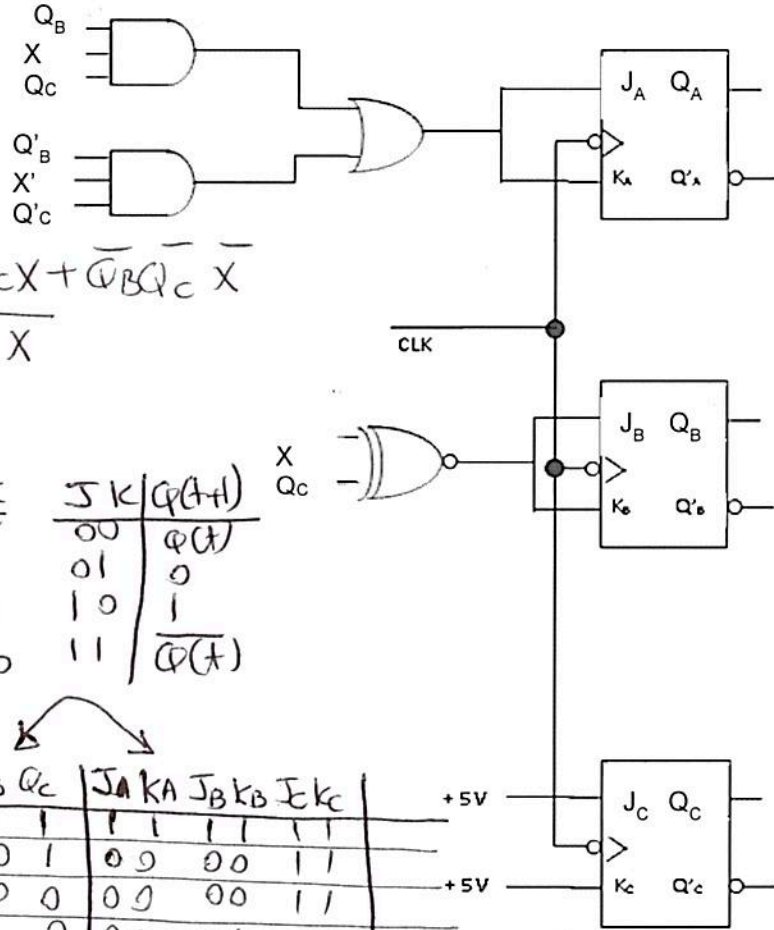Problem 1

Analyze the following sequential circuits leading to a state diagram.



1) $J_A = K_A = Q_B Q_C X + \overline{Q_B} \overline{Q_C} \overline{X}$

$J_B = K_B = Q_C \oplus X$


$J_C = K_C = 1$

2.

$Q(t)$	$Q(t+1)$	J	K	$Q(t+1)$
0	0	0	X	$\overline{Q(t)}$
0	1	1	X	0
1	0	X	1	1
1	1	X	0	$\overline{Q(t)}$

3/ Ps


Q_A	Q_B	Q_C	X	Q_A	Q_B	Q_C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	0	0	0	0	0	1	1
0	0	1	1	0	1	0	0	0	1	1	1	1
0	1	0	0	0	0	1	0	0	0	0	1	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	0	0	0	0	0	1	1
0	1	1	1	1	0	0	1	1	1	1	1	1
1	0	0	0	0	1	1	1	1	1	1	1	1
1	0	0	1	1	0	1	0	0	0	0	1	1
1	0	1	0	1	0	0	0	0	0	0	1	1
1	0	1	1	1	1	0	0	0	1	1	1	1
1	1	0	0	1	0	1	0	0	0	0	1	1
1	1	0	1	1	1	1	0	0	0	0	1	1
1	1	1	0	1	1	0	0	0	0	0	1	1
1	1	1	1	0	0	0	1	1	1	1	1	1

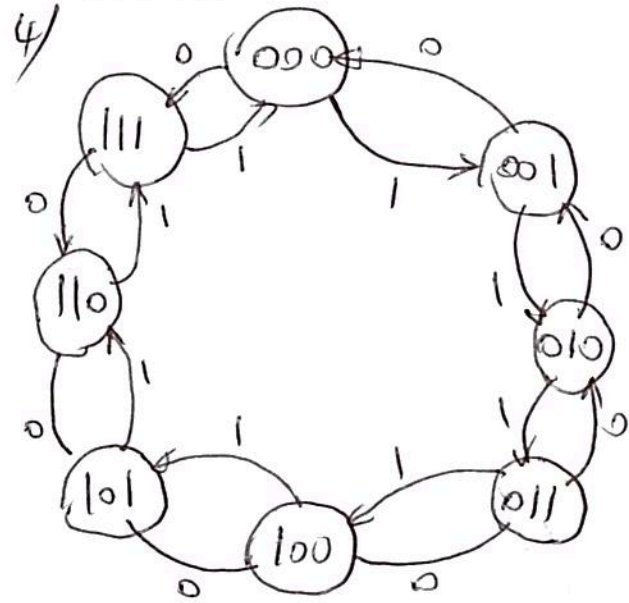

20 Points

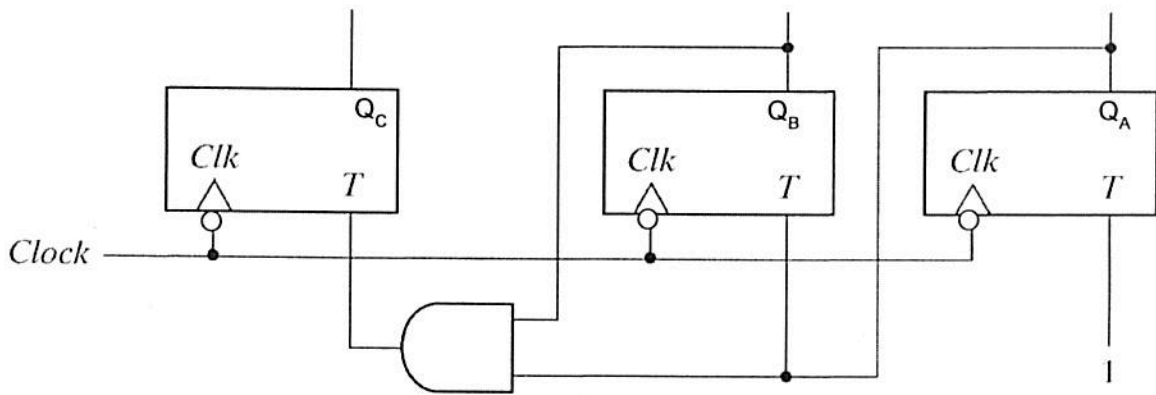Problem 2

Analyze the following sequential circuits leading to a state diagram.



1. $T_A = 1$


$T_B = Q_A$

$T_C = Q_A Q_B$

2.

T	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

PS						NS		
Q_A	Q_B	Q_C	T_A	T_B	T_C	Q_A	Q_B	Q_C
0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0	1
0	1	0	1	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	1	1	1	0	0	0

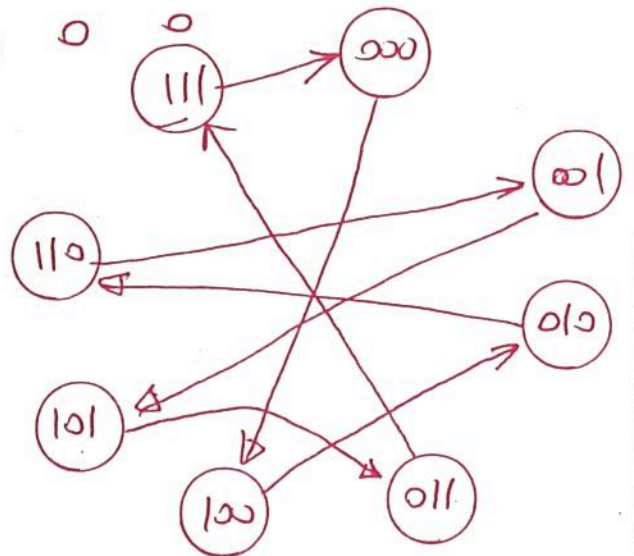

20 Points
Problem 3

Analyze the following circuit leading to its state diagram.

1) $D_A = \overline{Q_A} \oplus Q_B \oplus X$
 $D_B = C_{out} = \overline{Q_A} Q_B + Q_A X + Q_B X$

2) $Q(t) \quad Q(t+1) \quad D$


0	0	0
0	1	0
1	0	0
1	1	0

$Z = \overline{Q_B} X$
 $= Q_B + X$


D	Q(t+1)
0	0
1	1

3)

PS			FF input		NS		output
Q_A	Q_B	X	D_A	D_B	Q_A	Q_B	Z
0	0	0	1	0	1	0	1
0	0	1	0	1	0	1	0
0	1	0	0	1	0	1	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1
1	0	1	1	0	1	0	0
1	1	0	1	0	1	0	1
1	1	1	0	1	0	1	1

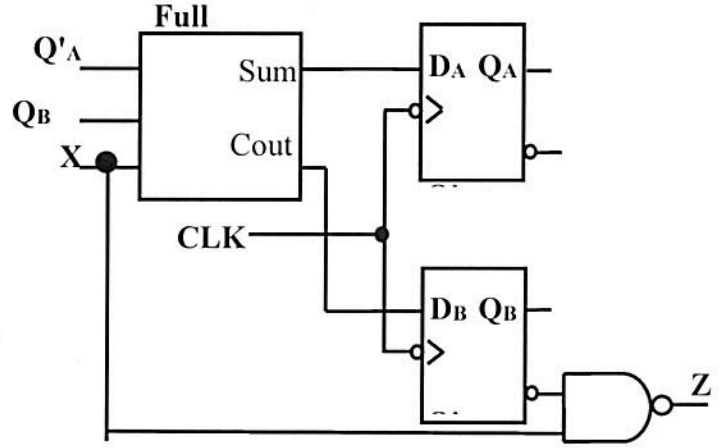

4.

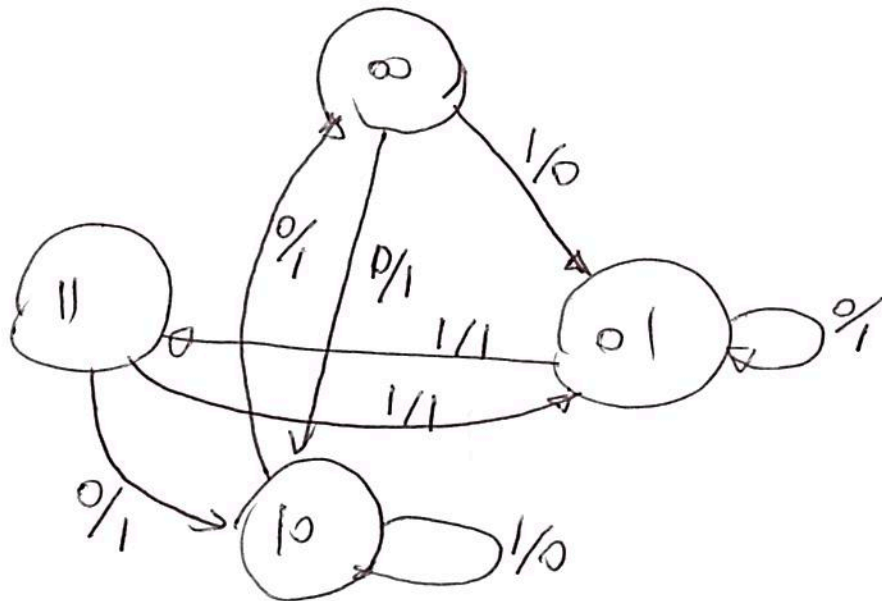


First Name: Key Last Name: key Sec: _____

20 Points


Problem 4

Using JK flip flops, design an up/down synchronous counter that counts from 3 to 6.

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

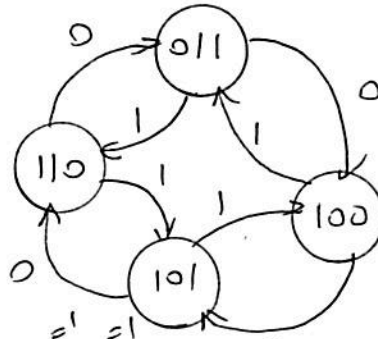



PS input			NS			$\Sigma = 1$			$\Sigma = 1$		
Q_A	Q_B	Q_C	Q_A	Q_B	Q_C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	X	X	X	X	X	X	X	X	X
0	0	1	X	X	X	X	X	X	X	X	X
0	0	0	X	X	X	X	X	X	X	X	X
0	0	1	X	X	X	X	X	X	X	X	X
0	1	0	X	X	X	X	X	X	X	X	X
0	1	0	X	X	X	X	X	X	X	X	X
0	1	1	1	0	0	1	X	X	1	X	1
0	1	1	1	0	0	1	X	X	1	X	1
1	0	0	1	0	1	X	1	1	X	1	X
1	0	0	1	0	1	X	1	1	X	1	X
1	0	1	1	0	0	X	0	1	X	X	1
1	0	1	1	0	0	X	0	1	X	X	1
1	1	0	0	1	1	X	1	X	0	1	X
1	1	0	1	0	1	X	0	X	1	1	X
1	1	1	X	X	X	X	X	X	X	X	X
1	1	1	X	X	X	X	X	X	X	X	X

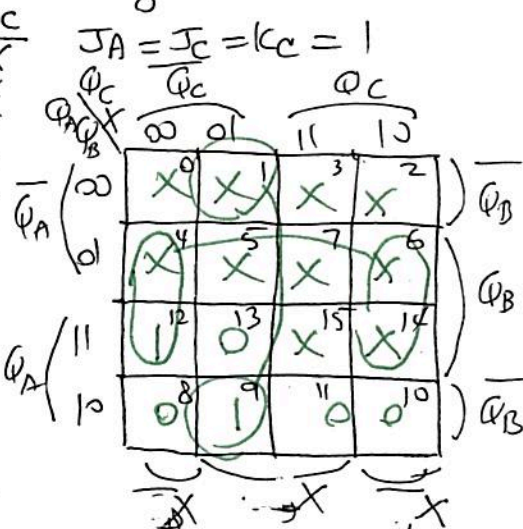

$J_A = J_C = K_C = 1$

$J_B = K_B = Q_C$

$K_A = Q_B X + Q_B Q_C X$

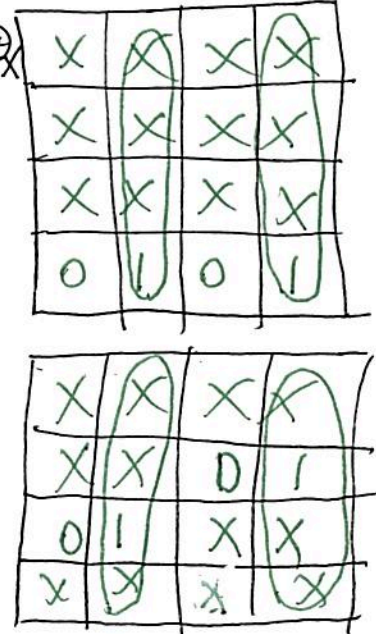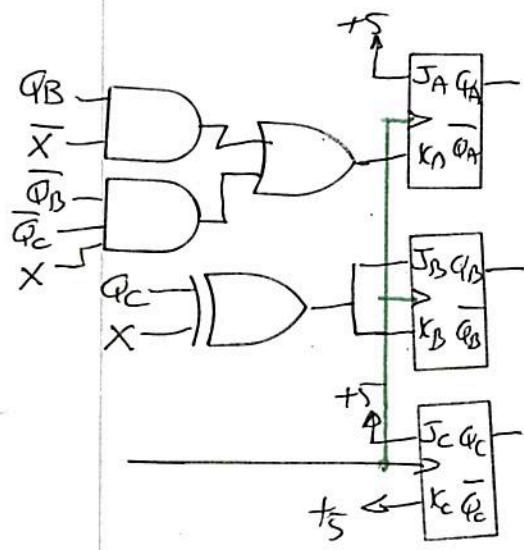


20 Points

Problem 5


Using JK flip-flops, design a circuit for the following state diagram.

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

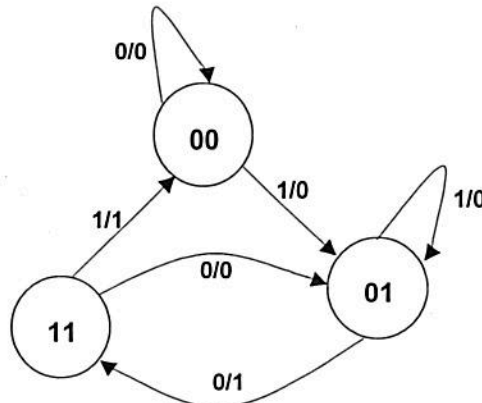

Q_A	Q_B	X	Q_A	Q_B	J_A	K_A	J_B	K_B	Z
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	1	1	1	X	X	0	1
0	1	1	0	1	0	X	X	0	0
1	0	0	X	X	X	X	X	X	X
1	0	1	X	X	X	X	X	X	X
1	1	0	0	1	X	1	X	0	0
1	1	1	0	0	X	1	X	1	1

$K=1$

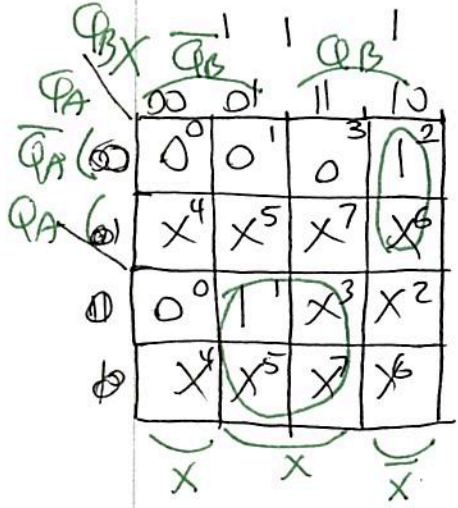


$J_A = Q_B \bar{X}$


$J_B = X$



$K_B = Q_A X$

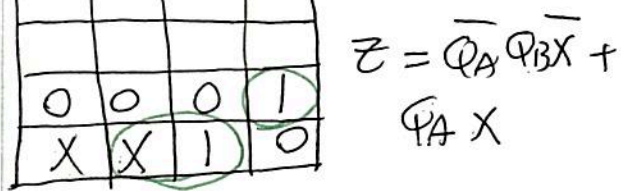


$Z = \bar{Q}_A \bar{Q}_B X + Q_A X$

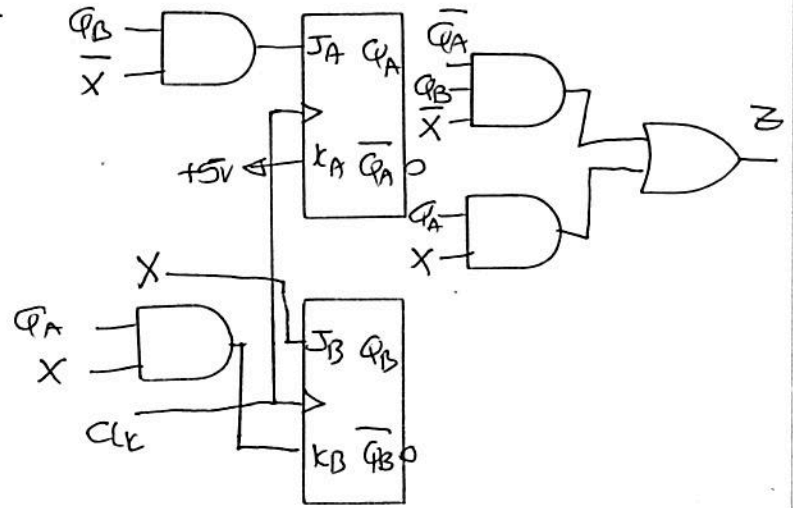


20 Points

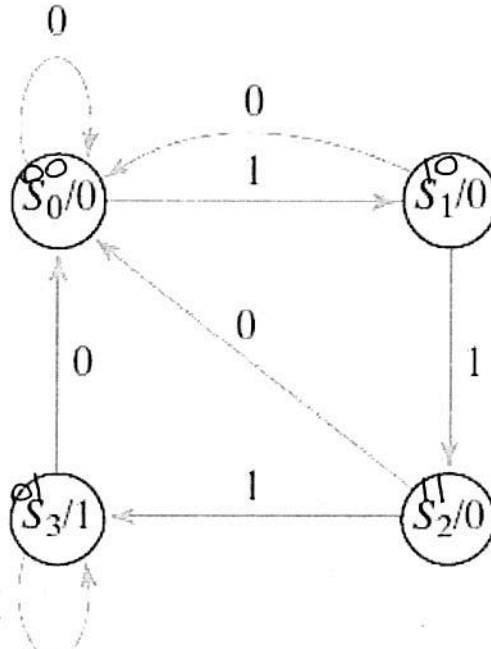Problem 6


Using T flip-flops, design a circuit for the following state diagram. You may make the following state assignments: S0 = 00, S1 = 10, S2 = 11, S3 = 01



PS			QA QB		TA	TB	Z
QA	QB	X	QA	QB	TA	TB	Z
0	0	0	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	0	1	1
0	1	1	0	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	0
1	1	1	0	1	1	0	0

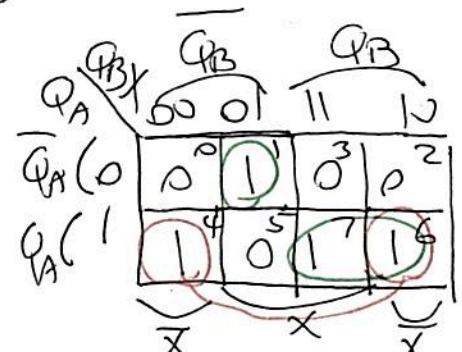

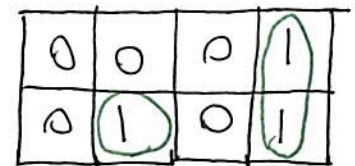
$$T_A = \overline{Q_A} \overline{Q_B} X + Q_A \overline{X} + Q_A Q_B$$



$$T_B = Q_B \overline{X} + Q_A \overline{Q_B} X$$


$$Z = \overline{Q_A} Q_B$$

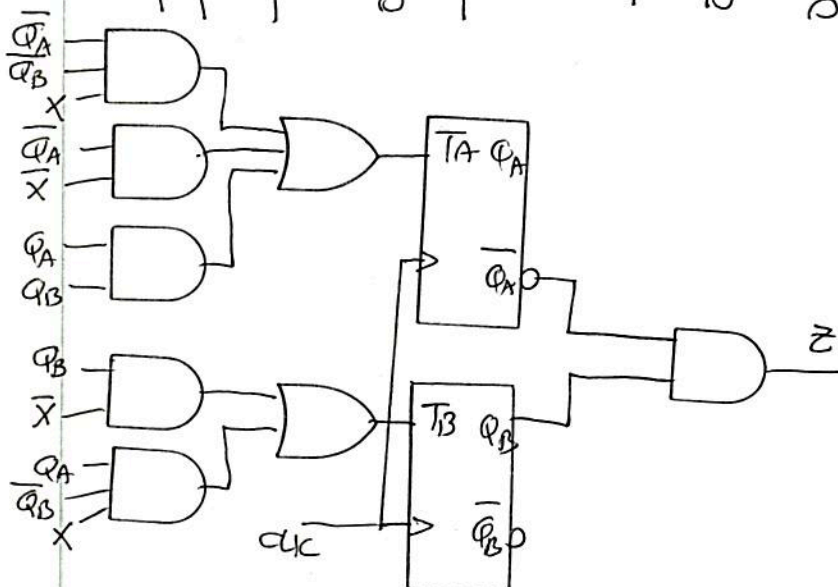

25 pt.

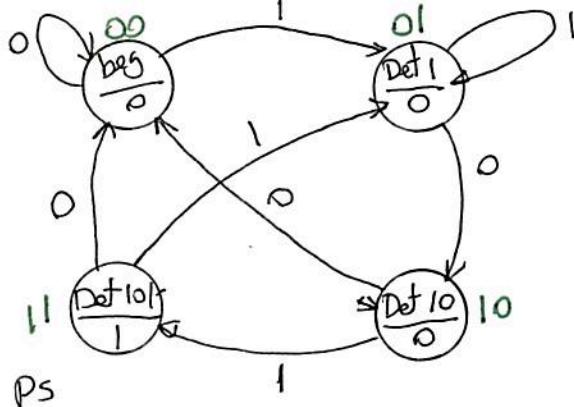Problem 7

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume no overlapping, namely 10101 generates output 00100.



$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q_A	Q_B	X	Q_A	Q_B	J_A	K_A	J_B	K_B	Z
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	1	0	1	X	X	1	0
0	1	1	0	0	0	X	X	0	0
1	0	0	0	0	X	1	0	1	0
1	0	1	1	1	X	0	1	X	0
1	1	0	0	0	X	1	X	1	1
1	1	1	0	1	X	1	X	0	1

Q_A	Q_B	X	Z
00	01	11	10
0 ⁰	0 ¹	0 ³	1 ²
X ⁴	X ⁵	X ⁷	X ⁶

$J_A = Q_B \bar{X}$

X	X	X	X
1	0	1	1

$K_A = \bar{X} + Q_B$


0	1	X	X
0	1	X	X

$J_B = X$

X	X	0	1
X	X	0	1

$K_B = \bar{X}$

$Z = Q_A Q_B$

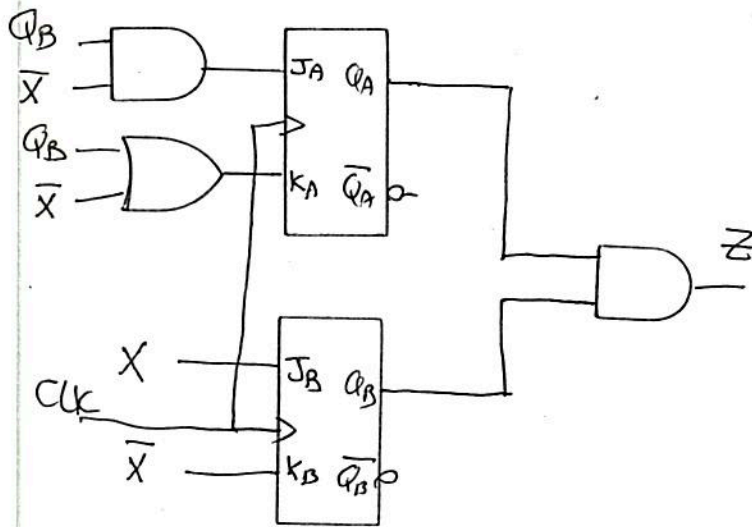


25 pt.

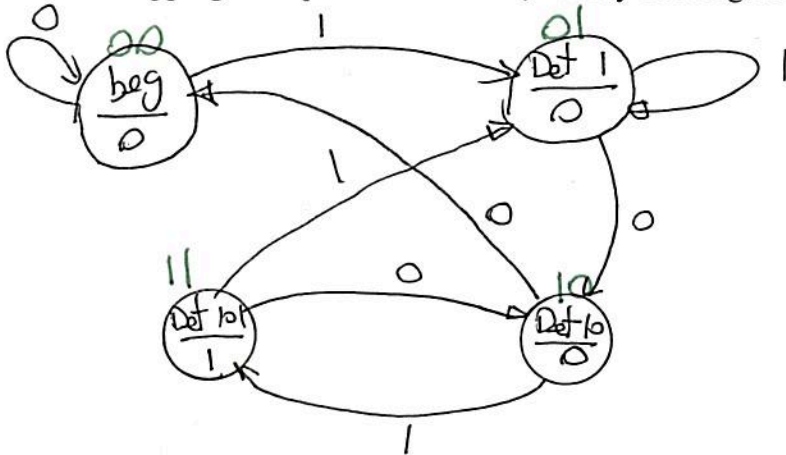Problem 8

Using JK flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101.

Assume overlapping of sequence is allowed, namely 10101 generates output 00101.



0	beg	Det 1
1	Det 10	Det 101

Q_A	Q_B	X	Q_A	Q_B	J_A	K_A	J_B	K_B	Z
0	0	0	0	0	0	X	0	X	0
0	0	1	0	1	0	X	1	X	0
0	1	0	1	0	1	X	X	1	0
0	1	1	0	0	0	X	X	0	0
1	0	0	0	0	X	1	0	X	0
1	0	1	1	1	X	0	1	X	0
1	1	0	1	0	X	0	X	1	1
1	1	1	0	1	X	1	X	0	1

$Q_B \backslash Q_A$

	0	1	1	1
0	0 ⁰	0 ¹	0 ³	1 ²
1	X ⁴	X ⁵	X ⁷	X ⁶

$J_A = Q_B \bar{X}$

X	X	X	X
1	0	1	0

$K_A = Q_B \oplus X$


1	0	1	X	X
0	1	X	X	X

$J_B = X$

X	X	0	1
X	X	0	1

$K_B = \bar{X}$


$Z = Q_A Q_B$

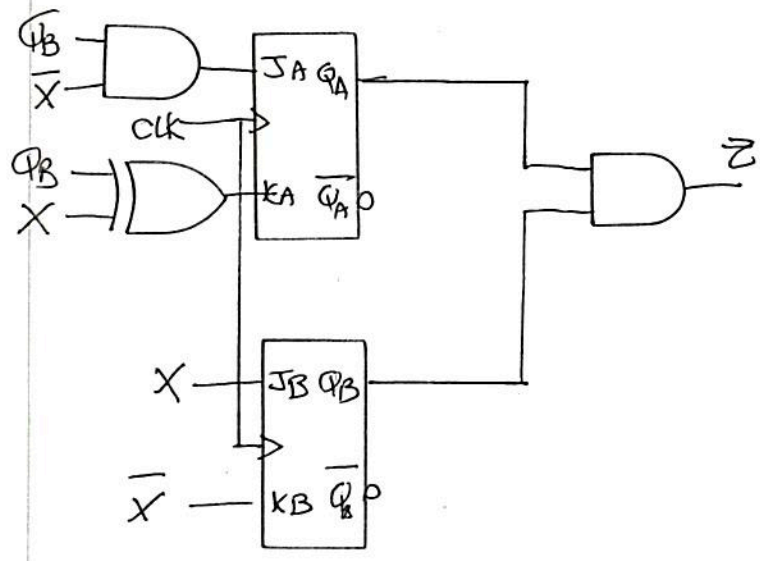

25 pt.

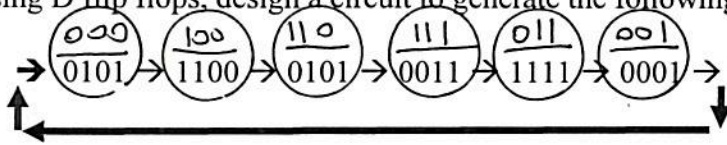Problem 9

Using D flip flops, design a circuit to generate the following sequence.




Your design should be race free.

PS			NS			Zs			
QA	QB	QC	QA	QB	QC	Z3	Z2	Z1	Z0
0	0	0	1	0	0	0	1	0	1
0	0	1	0	0	0	0	0	0	1
0	1	0	X	X	X	X	X	X	X
0	1	1	0	0	1	1	1	1	1
1	0	0	1	1	0	1	1	0	0
1	0	1	X	X	X	X	X	X	X
1	1	0	1	1	1	0	1	0	1
1	1	1	0	1	1	0	0	1	1

$$D_A = \overline{Q_C}$$


$$D_B = Q_A$$

$$D_C = Q_B$$

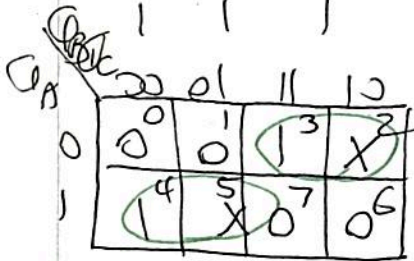


$$Z_3 = Q_A \overline{Q_B} + \overline{Q_A} Q_B$$

$$= Q_A \oplus Q_B$$

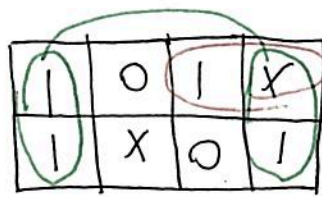
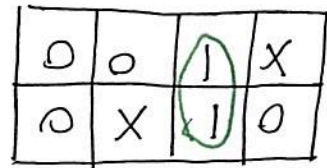
$$Z_2 = \overline{Q_C} + \overline{Q_A} Q_B$$



$$Z_1 = Q_B Q_C$$

$$Z_0 = \overline{Q_A} + Q_B$$

