



EGC220

Class Notes

12/6/2021

Baback Izadi

Division of Engineering Programs

bai@engr.newpaltz.edu

Final: Thursday 12/16, 10:15 AM - 12:15 PM

Closed book and notes, no calculator

- Number systems
- Simplification using K-map
 - SOP, POS, Standard SOP and POS, Min. SOP and POS
- Design of combinational circuits
- Circuit conversion to all NAND or NOR gates
- Multiplexers, Demultiplexers, Decoders, Encoders
- Design of combinational circuits using PLD's
- Latch and flip flops characteristics and excitation tables, design of ripple counters
- Analysis of sequential circuits
- Design of sequential circuits
 - Design using Mealy and Moore model
 - Design of a sequence detector
 - Design of a shift register
 - Design of a controller

000
100
110
111
011
001

Problem 9

Using D flip flops, design a circuit to generate the following sequence.

0101 → 1100 → 0101 → 0011 → 1111 → 0001 →

Your design should be race free.

	0	0	1	1	1
0	A	B	C		
1	F	E	D		

ps	NS	DA	DB	DC	Z3	Z2	Z1	Z0
QA QB QC	QA QB QC							
0 0 0	0 0 0	0	0	1	0	1	0	1
0 0 1	0 0 1	0	1	1	1	1	0	0
0 1 0	X X X	X	X	X	X	X	X	X
0 1 1	1 1 1	1	1	1	0	1	0	1
1 0 0	0 0 0	0	0	0	0	0	0	1
1 0 1	1 0 0	1	0	0	1	1	1	1
1 1 0	X X X	X	X	X	X	X	X	X
1 1 1	1 0 1	0	0	1	0	0	1	1

$$D_A = Q_B Q_C$$

$$D_B = \overline{Q_A} Q_C$$

$$D_C = \overline{Q_A} + Q_B$$

$$Z_3 = Q_B + Q_A Q_C$$

$$Z_2 = \overline{Q_A} + \overline{Q_B} Q_C$$

$$Z_1 = Q_A Q_C$$

$$Z_0 = \overline{Q_A} Q_B + \overline{Q_C}$$

QA QB QC	0	0	1	1	1
QA=0	0	1	0	0	X
QA=1	0	1	0	0	X

1	1	1	X
0	0	1	X

1	1	1	X
0	1	0	X

0	0	0	X
0	1	1	X

1	0	1	X
1	1	1	X

$$Z_0 = \overline{Q_A} Q_B + \overline{Q_C}$$

$$84 - 96 = -12$$

$$\begin{array}{r} 84 \\ 96 \\ \hline -96 \end{array}$$

S	64	32	16	8	4	2	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	0	0
1	0	1	0	0	0	0	0

$$\begin{array}{r} 010100 \\ + 10100000 \\ \hline \end{array}$$

NEG.

$$\textcircled{1}1110100 \xrightarrow{2's}$$

$$\begin{array}{r} 8421 \\ -00001100 \\ \hline -12 \end{array}$$

011010 unsigned subtraction

9.5
4.25

$$\begin{array}{r} \leftarrow 1001.10 \\ - 0100.01 \\ \hline \end{array}$$

$$\begin{array}{r} 1001.10 \\ + 1011.11 \\ \hline 0101.01 \end{array}$$

$(23.5)_6$
 $\times (34.3)_6$
 \hline
 $\begin{array}{r} 1153 \\ 1432 \\ 1153 \end{array}$
 \hline
 $(1352.13)_6$

$$\begin{array}{l} 15 \div 6 = 2 \quad R=3 \\ 11 \div 6 = 1 \quad R=5 \\ 7 \div 6 = 1 \quad R=1 \\ 20 \div 6 = 3 \quad R=2 \\ 15 \div 6 = 2 \quad R=3 \\ 10 \div 6 = 1 \quad R=4 \\ 8 \div 6 = 1 \quad R=2 \end{array}$$

$Cx=1$