

EGC220

Class Notes

2/17/2023

Baback Izadi

Division of Engineering Programs

bai@engr.newpaltz.edu

TABLE 2-6
Basic Identities of Boolean Algebra

1. $X + 0 = X$	2. $X \cdot 1 = X$	
3. $X + 1 = 1$	4. $X \cdot 0 = 0$	
5. $X + X = X$	6. $X \cdot X = X$	
7. $X + \bar{X} = 1$	8. $X \cdot \bar{X} = 0$	
9. $\overline{\bar{X}} = X$		
10. $X + Y = Y + X$	11. $XY = YX$	Commutative
12. $X + (Y + Z) = (X + Y) + Z$	13. $X(YZ) = (XY)Z$	Associative
14. $X(Y + Z) = XY + XZ$	15. $X + YZ = (X + Y)(X + Z)$	Distributive
16. $\overline{X + Y} = \bar{X} \cdot \bar{Y}$	17. $\overline{X \cdot Y} = \bar{X} + \bar{Y}$	DeMorgan's

sum of products

product of sums

$$XY + X\bar{Y} = X(X + \bar{Y})$$

$$\bar{C} + XC = (\bar{C} + X)(\bar{C} + C)$$

1. Find the complement of $F = XY + Z'$. Then show that $FF' = 0$ and $F + F' = 1$


$$F' = \overline{XY + Z}$$

$$= \overline{XY} \cdot \overline{Z}$$




$$= (\bar{X} + \bar{Y}) \cdot Z$$

~~$$= \bar{X} + \bar{Y} \cdot Z$$~~

wrong

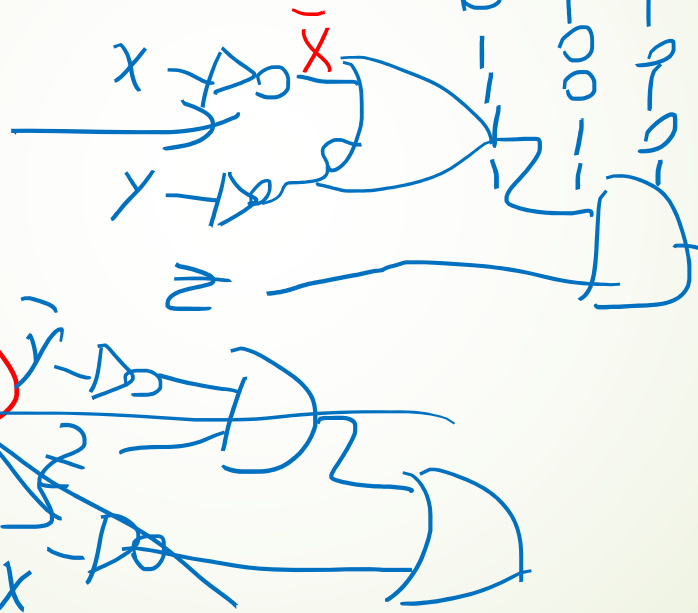


X	Y	Z	F	F'	FF'	F+F'
0	0	0	0	1	0	1
0	0	1	0	0	0	0
0	1	0	0	1	0	1
0	1	1	0	0	0	0
1	0	0	0	1	0	1
1	0	1	0	0	0	0
1	1	0	1	0	0	1
1	1	1	1	0	0	1

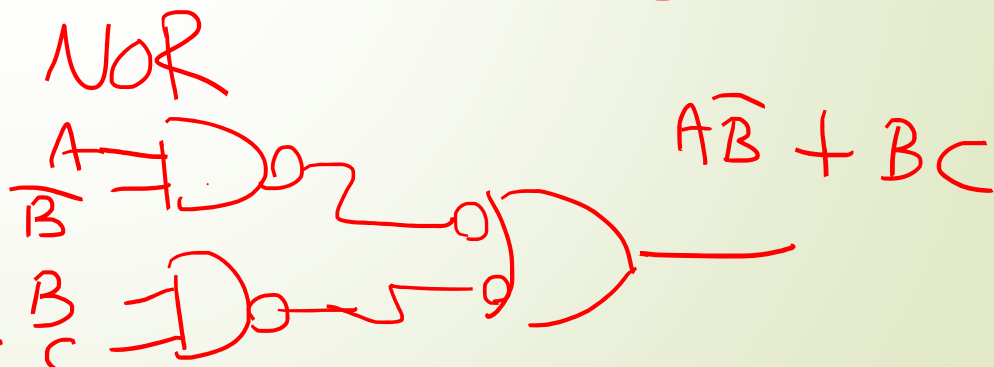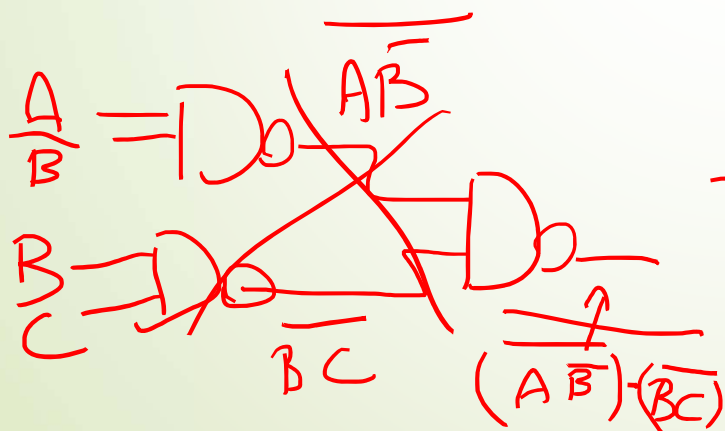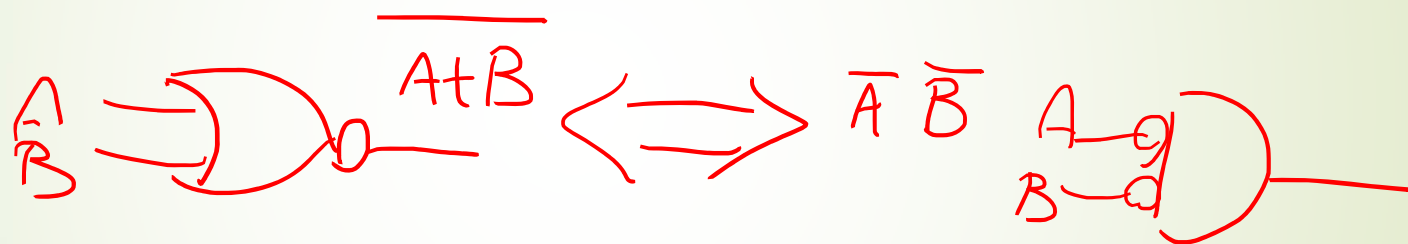

1. For function $F = XY + XY' + Y'Z$

a. Truth table

X	Y	Z	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

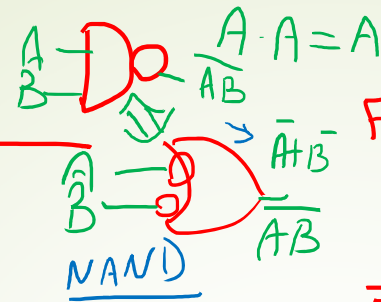

a. Minimum sum of products

$$F = \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z} + X\bar{Y}Z + X\bar{Y}Z + XY\bar{Z} + XYZ$$

$$= \bar{Y}Z(\bar{X} + X) + X\bar{Y}(\bar{Z} + Z) + XY(\bar{Z} + Z)$$

$$= \bar{Y}Z + X\bar{Y} + XY = \bar{Y}Z + X(\bar{Y} + Y)$$

$$= \bar{Y}Z + X$$

b. Minimum products of sums

$$F = (X + Y + \bar{Z})(X + \bar{Y} + Z)(X + \bar{Y} + \bar{Z})$$

$$= (X + Z + Y\bar{Y})(X + \bar{Y} + Z\bar{Z}) = (X + Z)(X + \bar{Y})$$

b. Sum of min terms

$$F = \sum m(1, 4, 5, 6, 7)$$

c. Product of max terms

$$F = \prod M(0, 2, 3)$$


d. Standard sum of products

$$F = \bar{X}\bar{Y}Z + X\bar{Y}\bar{Z} + X\bar{Y}Z + X\bar{Y}Z + XY\bar{Z} + XYZ$$


e. Standard product of sums

$$F = (\bar{X} + \bar{Y} + Z)(\bar{X} + Y + \bar{Z})(X + \bar{Y} + \bar{Z})(X + Y + Z)$$

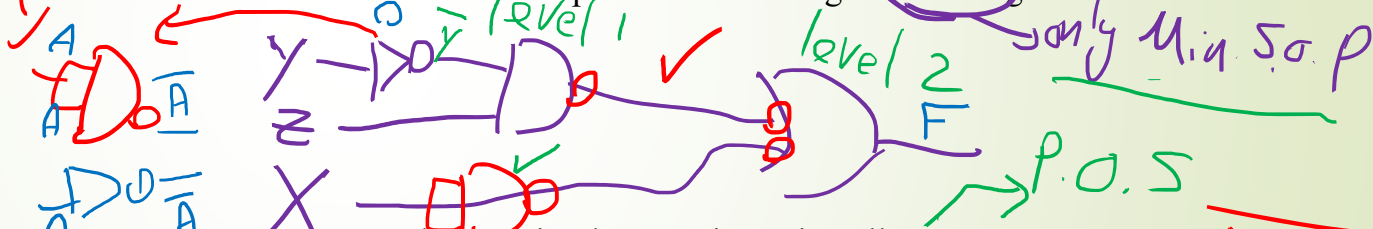c. Gate implementation using all NAND gates



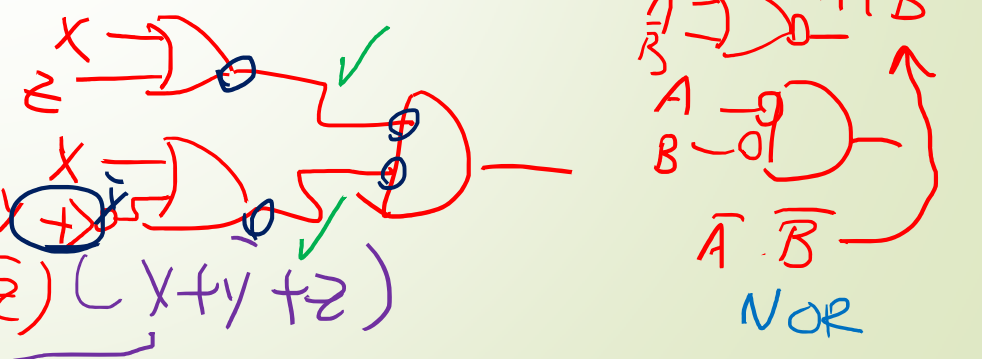d. Gate implementation using all NOR gates





a. Using AND and OR gates, draw the logic diagrams for the following Boolean expressions without expanding or simplifying them.


i. $Y = (A'+B')C + B(A+C)$

ii. ~~$G = (A+B')(C+D')$~~



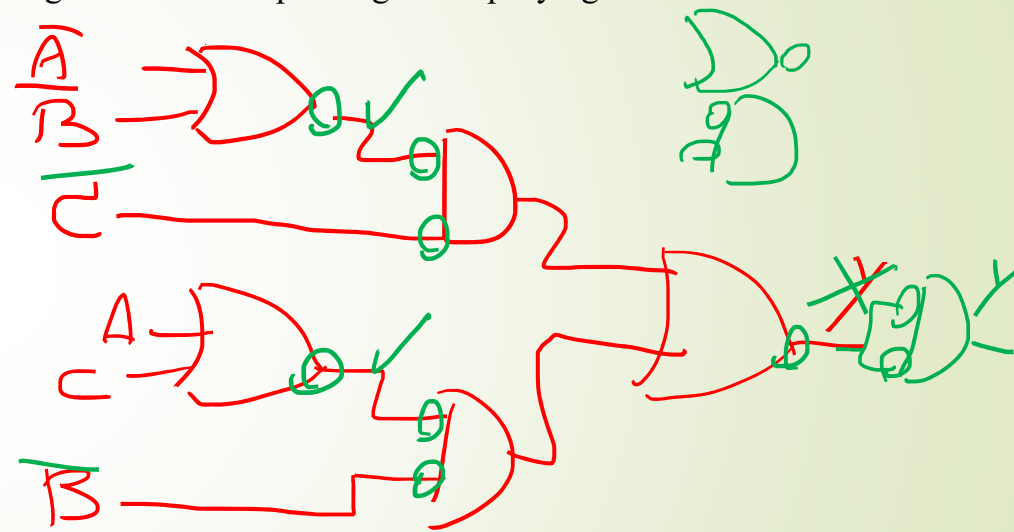
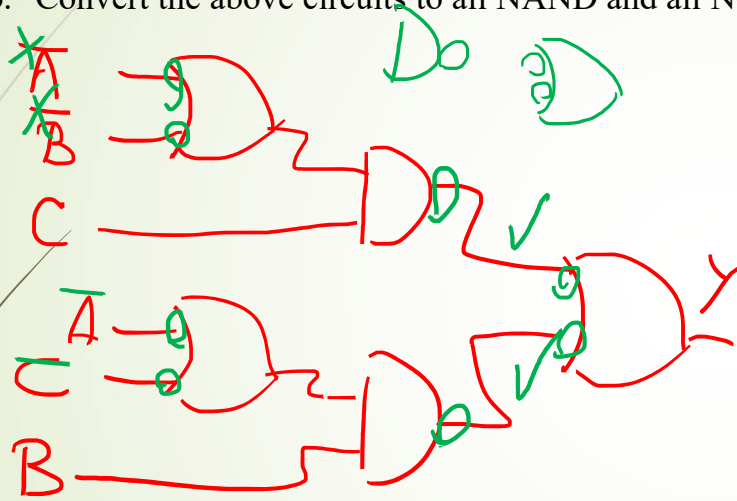
b. Convert the above circuits to all NAND and all NOR gates without expanding or simplifying the functions.



NAND

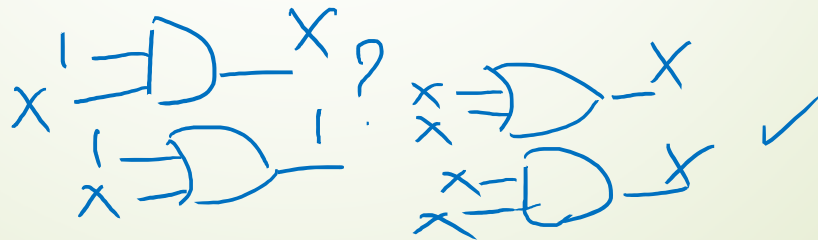

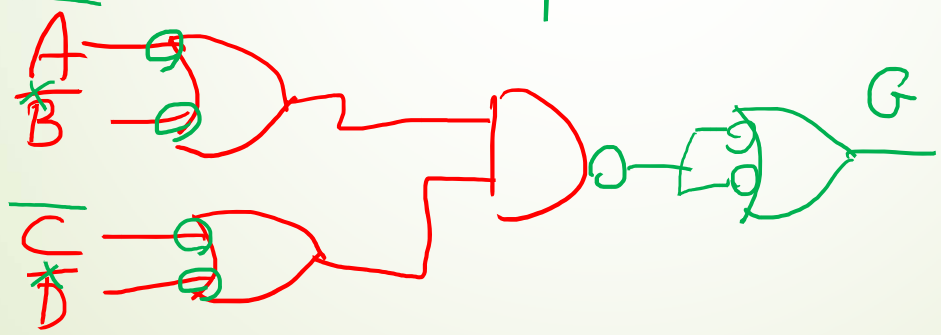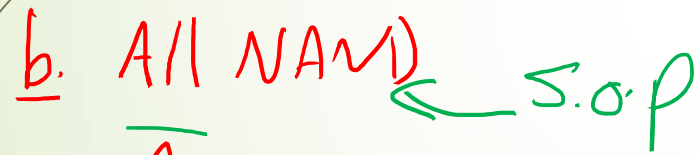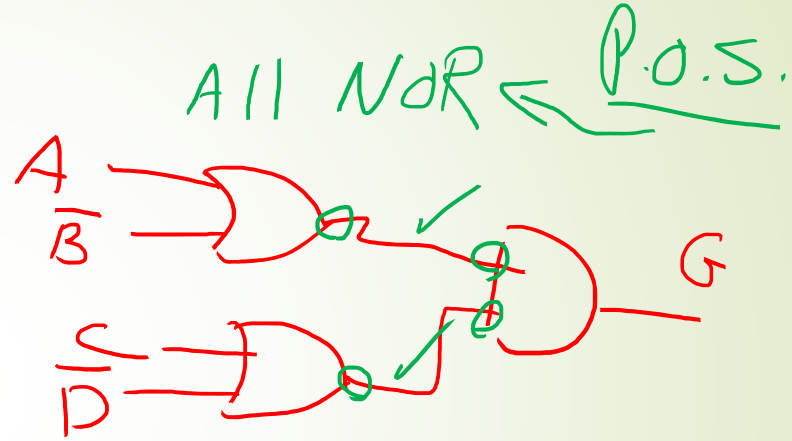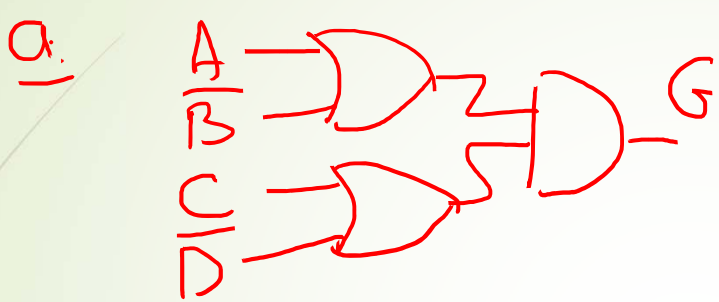- a. Using AND and OR gates, draw the logic diagrams for the following Boolean expressions without expanding or simplifying them $G = (A+B')(C+D')$
- b. Convert the above circuits to all NAND and all NOR gates without expanding or simplifying the functions.



1. For the following Boolean expression $F = X'Y' + Y'Z + XZ + XY + YZ'$, determine

- Truth table
- Sum of min terms
- Product of max terms
- Standard sum of products
- Standard product of sums
- Minimum sum of products
- Minimum products of sums
- Gate implementation using all NAND gates
- Gate implementation using all NOR gates.

X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$F = \bar{X}\bar{Y}(\bar{Z}+Z)$
 ~~$+ X\bar{Z}(\bar{Y}+Y)$~~
 ~~$+ XY(\bar{Z}+Z)$~~
 $F = \bar{X}\bar{Y} + Y\bar{Z} + XZ$



b. $F = \sum m(0, 1, 2, 5, 6, 7)$

c. $F = \prod M(3, 4)$

d. $F = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z}$
 ~~$+ X\bar{Y}Z + XY\bar{Z}$~~

e. $\bar{F} = \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} \Rightarrow F = (X + \bar{Y} + \bar{Z})(X + Y + Z)$

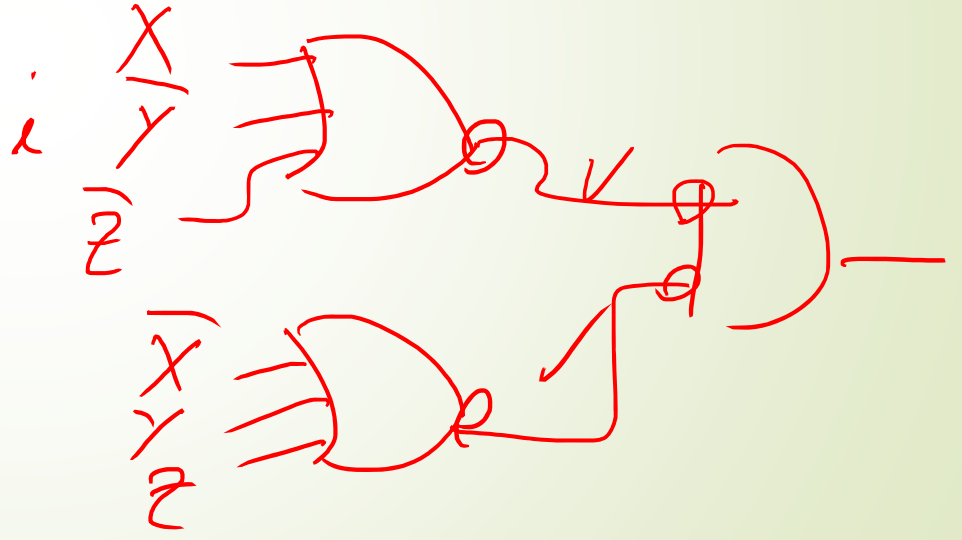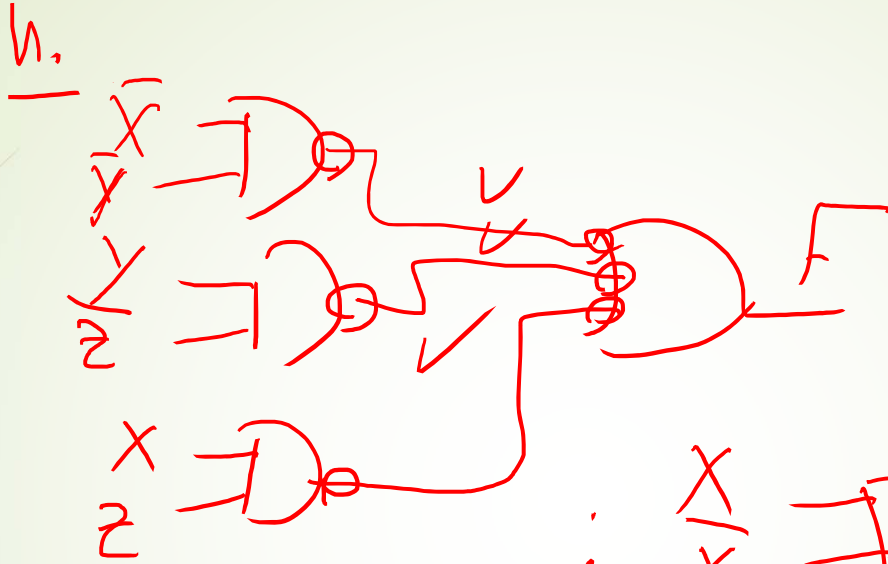g. $F = (X + \bar{Y} + \bar{Z})(\bar{X} + Y + Z)$



extra simplify

$$F = \overline{X} \overline{Y} \overline{Z} + \overline{X} \overline{Y} Z + \overline{X} Y \overline{Z} + \overline{X} Y Z$$

3 copies

XYZ XYZ

$$= YZ(\overline{X} + X) + XZ(\overline{Y} + Y) + XY(\overline{Z} + Z)$$

$$= YZ + XZ + XY$$