

EGC220

Class Notes

2/21/2023



Baback Izadi

Division of Engineering Programs

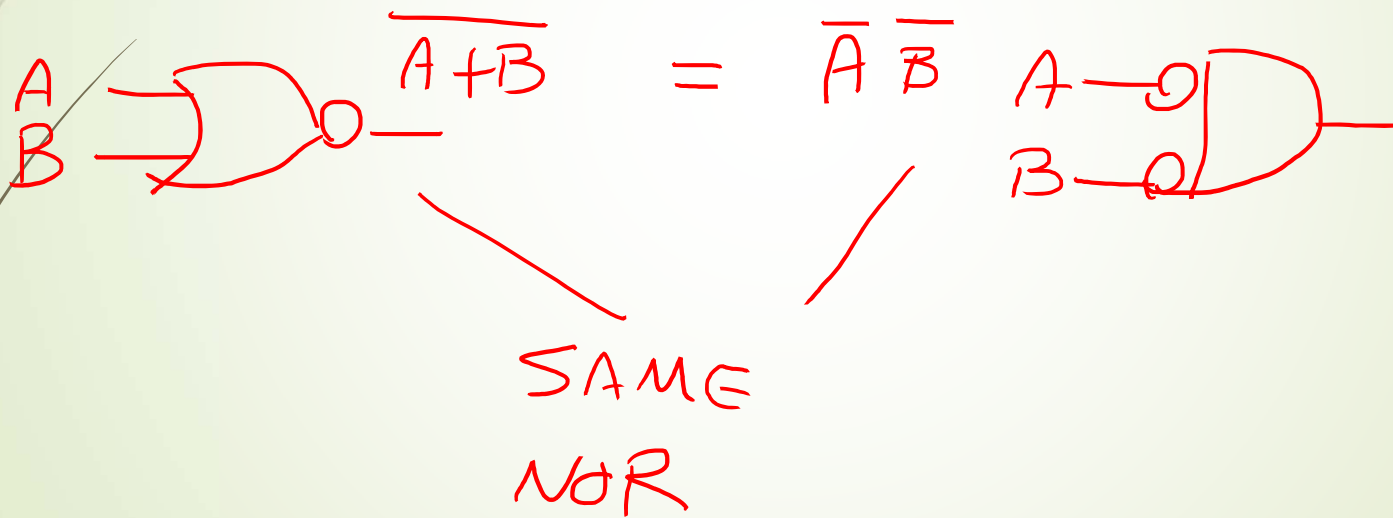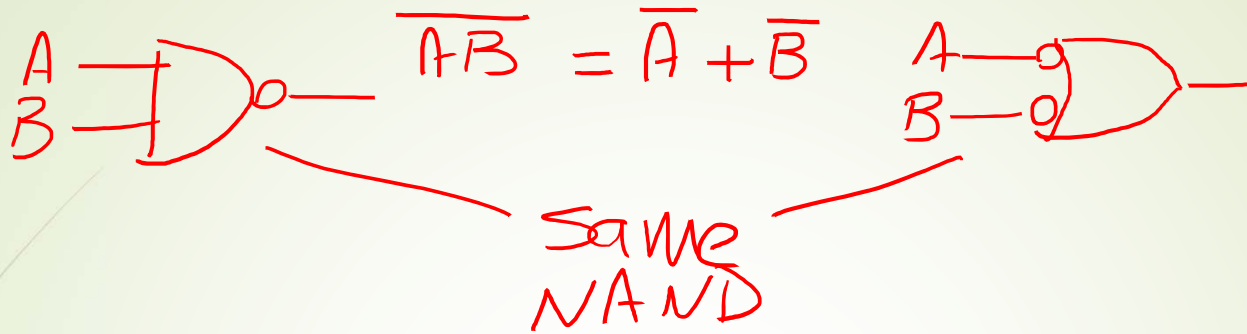bai@enr.newpaltz.edu


Test 1:

- Number systems
 - Convert any base to any base
 - Quick conversion between base 2, 4, 8, and 16
 - Add, subtract, multiply in any base
- Logic gate implementation of a Boolean function
- Boolean properties and laws
- Simplification of Boolean algebra using Boolean laws
- Representing Boolean functions in terms of
 - Sum of min-terms, product of max-terms, standard sum of products, standard product of sums, minimum sum of products, minimum product of sums
 - Representing Boolean functions using all NAND or NOR gates.
- Simplification using K-map (up to 5 variables)
 - SOP, POS, Standard SOP and POS, Min. SOP and POS
- Design of combinational circuits



Simplification criteria in K-map

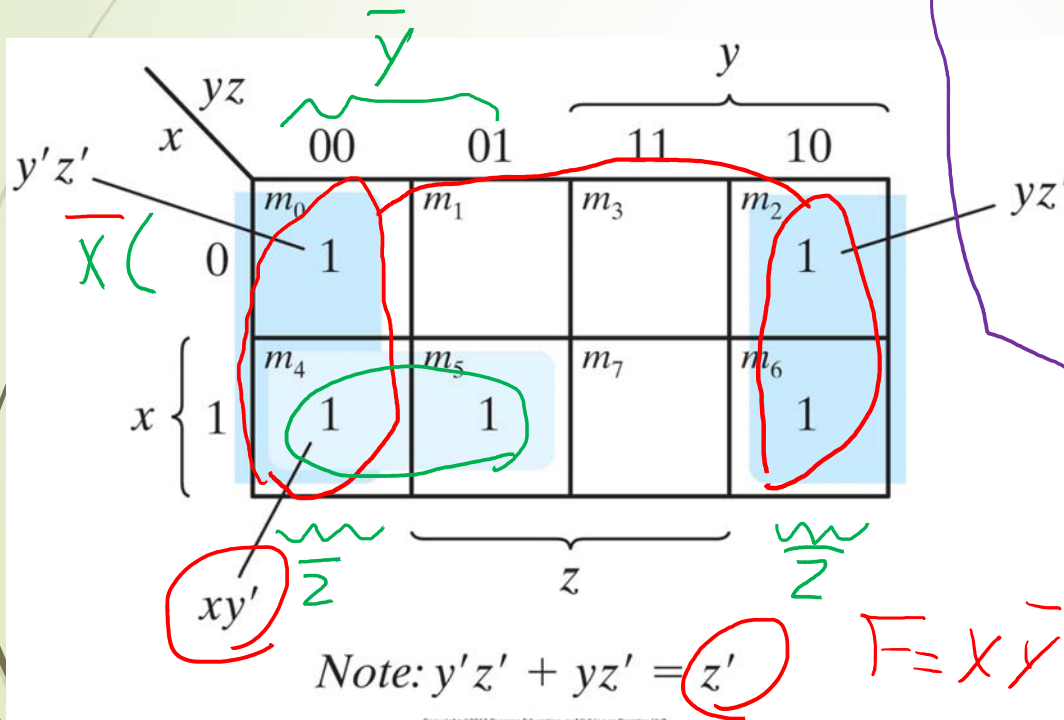- ✓ 1. Least number of groups. $y\bar{z} + yz$
2. Make each group as large as possible.
3. Make sure each group is essential



$$\bar{x}\bar{y}\bar{z} + x\bar{y}\bar{z} + \bar{x}y\bar{z} + xy\bar{z}$$

$m_0 \quad m_4 \quad m_2 \quad m_6$

$$\bar{y}\bar{z}(\bar{x} + x) + y\bar{z}(\bar{x} + x)$$

$$\bar{y}\bar{z} + y\bar{z} = \bar{z}(\bar{y} + y) = \bar{z}$$

$$x\bar{y}\bar{z} + x\bar{y}z = x\bar{y}(\bar{z} + z) = x\bar{y}$$

$m_4 \quad m_5$

essential → Non-essential
 ∴ should not be included

1. Simplify the following Boolean functions using three variables K-maps and express your answer in minimum sum of products and minimum product of sums.

a. $F(A,B,C) = \Sigma m(0, 1, 2, 3, 7)$

Min S.O.P

$F = \bar{A} + BC$

Min P.O.S

$\bar{F} = AB + A\bar{C}$

b. $F(A,B,C) = \Sigma m(3,5,6,7)$

Min S.O.P




$F = BC + AC + AB$

$\bar{F} = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C} \rightarrow F = (A+B)(B+C)(A+C)$

c. $F(A,B,C) = \Pi M(0, 2, 3, 4, 6)$

$F = \bar{B}C + AC$

min S.O.P

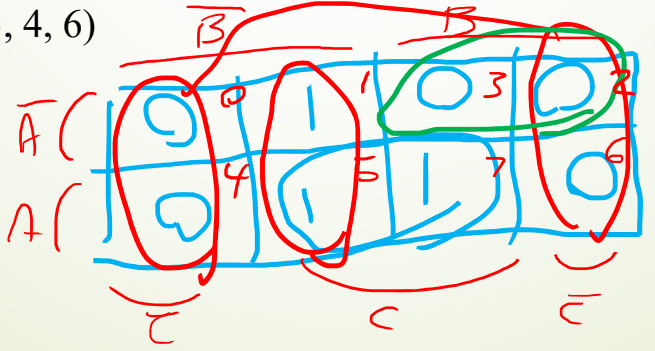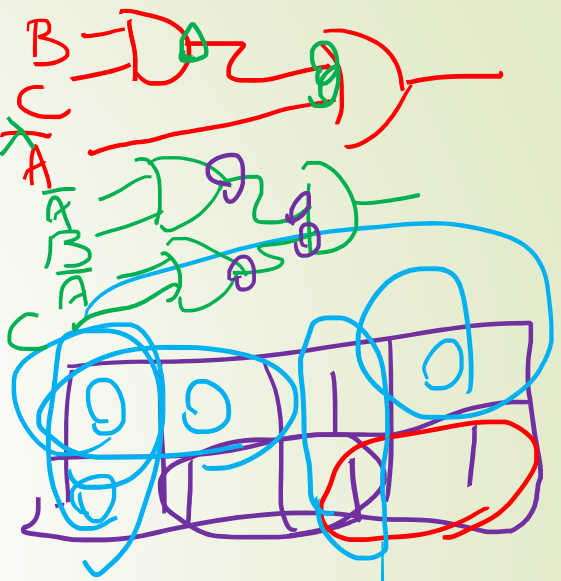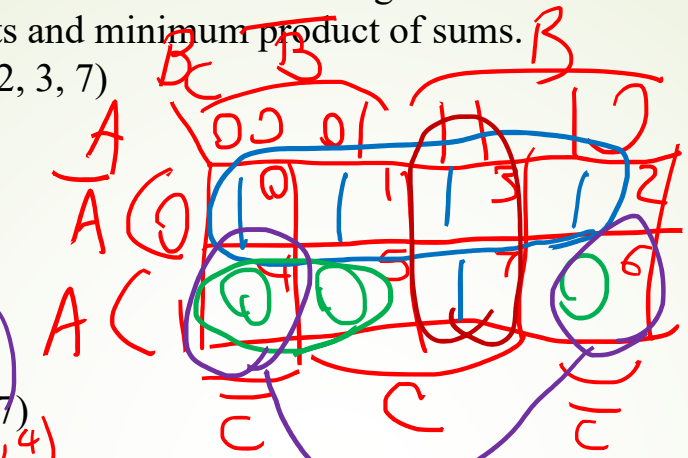


$\bar{F} = \bar{C} + \bar{A}B$

$F = C(A+B)$

min P.O.S.

2. Simplify the following Boolean functions using three variables K-maps and express your answer in minimum sum of products and minimum product of sums.

a. $F(A,B,C) = A'B' + BC + A'BC'$

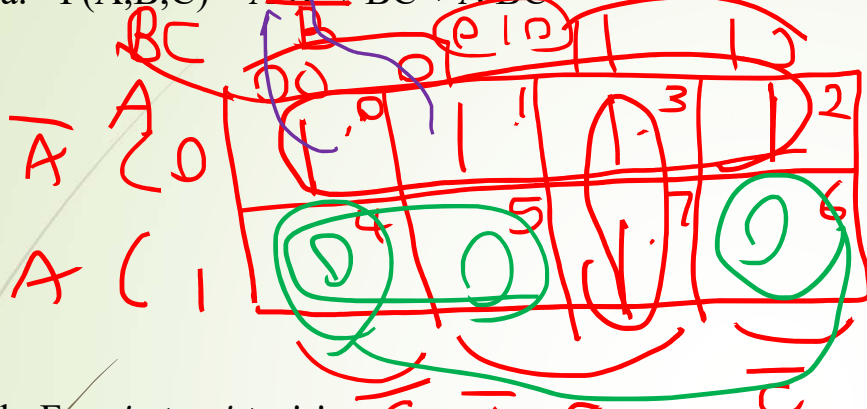


$F = \bar{A} + BC$ Min. S.o.P

$\bar{F} = A\bar{C} + A\bar{B}$

$F = (\bar{A} + C)(A + B)$

b. $F = x'y + yz' + y'z'$

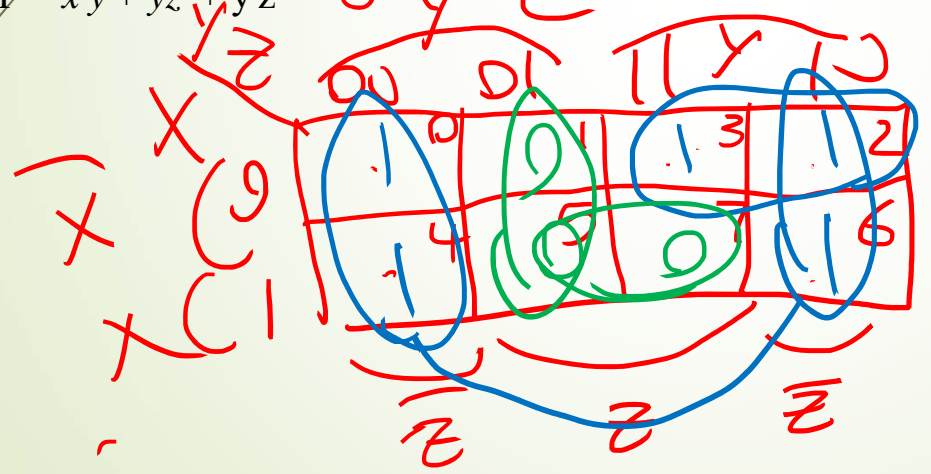


$F = \bar{z} + \bar{x}y$ Min. S.o.P

$\bar{F} = \bar{y}z + xz$

$F = (y + \bar{z})(\bar{x} + \bar{z})$
Min. P.o.S

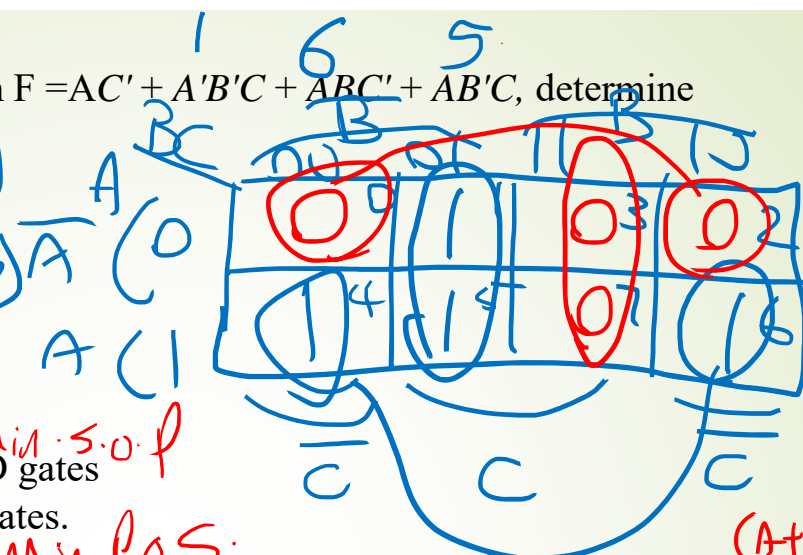3. For the following Boolean expression $F = AC' + A'B'C + ABC' + AB'C$, determine
- Truth table
 - Sum of min terms
 - Product of max terms
 - Standard sum of products
 - Standard product of sums
 - Minimum sum of products
 - Minimum products of sums
 - Gate implementation using all NAND gates
 - Gate implementation using all NOR gates.

$F = \sum m(1, 4, 5, 6)$
 $F = \prod M(0, 2, 3, 7)$



d. $\Rightarrow F = \overline{A} \overline{B} C + A \overline{B} \overline{C} + A \overline{B} C + A B \overline{C}$

e. $\Rightarrow \overline{F} = \overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} C + A B C$

$F = (A+B+C)(A+\overline{B}+\overline{C})(A+\overline{B}+\overline{C})(\overline{A}+\overline{B}+\overline{C})$

\rightarrow Min. S.O.P
 \rightarrow Min. P.O.S.

a.

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

b. $F = \overline{B} C + A \overline{C}$

c. $\overline{F} = \overline{B} C + A \overline{C}$
 $F = (\overline{B} + \overline{C})(A + C)$

