

# EGC220

## Class Notes

### 2/28/2023

**Baback Izadi**


Division of Engineering Programs

[bai@engr.newpaltz.edu](mailto:bai@engr.newpaltz.edu)

# Test 1:

- ▶ Number systems
  - ▶ Convert any base to any base
  - ▶ Quick conversion between base 2, 4, 8, and 16
  - ▶ Add, subtract, multiply in any base
- ▶ Logic gate implementation of a Boolean function
- ▶ Boolean properties and laws
- ▶ Simplification of Boolean algebra using Boolean laws
- ▶ Representing Boolean functions in terms of
  - ▶ Sum of min-terms, product of max-terms, standard sum of products, standard product of sums, minimum sum of products, minimum product of sums
  - ▶ Representing Boolean functions using all NAND or NOR gates.
- ▶ Simplification using K-map (up to 5 variables)
  - ▶ SOP, POS, Standard SOP and POS, Min. SOP and POS
- ▶ Design of combinational circuits

## Design Steps

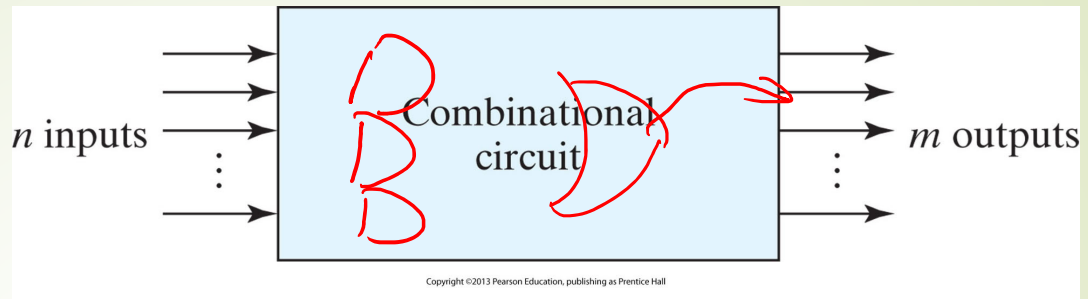

- From the specification of the circuit, determine the number of inputs and outputs and assign a symbol to each.
- Derive a truth table, assigning inputs to the left and outputs to the right.
- Place all possible combination of inputs i.e all 0's to all 1's
- Using the problem definition determine each output.
- If combinations are left without a specified output, mark them as don't cares.
- Simplify each output using K-map.
- Draw a circuit for each output per requirement ie. All NAND, all NOR, AND – OR, OR – AND, XOR, etc.

0 0 0  
0 0 1  
:  
:  
:  
1 1 1

### Problem 1


Design a circuit that counts the number of 0's present in 4 inputs A, B, C and D. Its output is a multi-bit, representing that count in binary. For example, 0101 has two zeros and therefore the output should be a binary representing 2.




- Write the truth table for this circuit.
- Find the minimized logic equations in SOP and POS for each output
- Draw the corresponding all NAND and all NOR gates logic diagram for this circuit. Label all inputs and outputs.

3 → 421 → 100 ← 4 0's → 100

A	B	C	D	X	Y	Z
0	0	0	0	1	0	0
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	0	1
1	0	0	0	0	1	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	0

$Y = \overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} C \overline{D} + \overline{A} \overline{B} C D + \overline{A} B \overline{C} \overline{D} + \overline{A} B \overline{C} D + \overline{A} B C \overline{D} + \overline{A} B C D$   
 $Z = \overline{A} B C D + \overline{A} B C \overline{D} + \overline{A} B \overline{C} D + \overline{A} B \overline{C} \overline{D} + \overline{A} \overline{B} C D + \overline{A} \overline{B} C \overline{D} + \overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} \overline{C} \overline{D}$

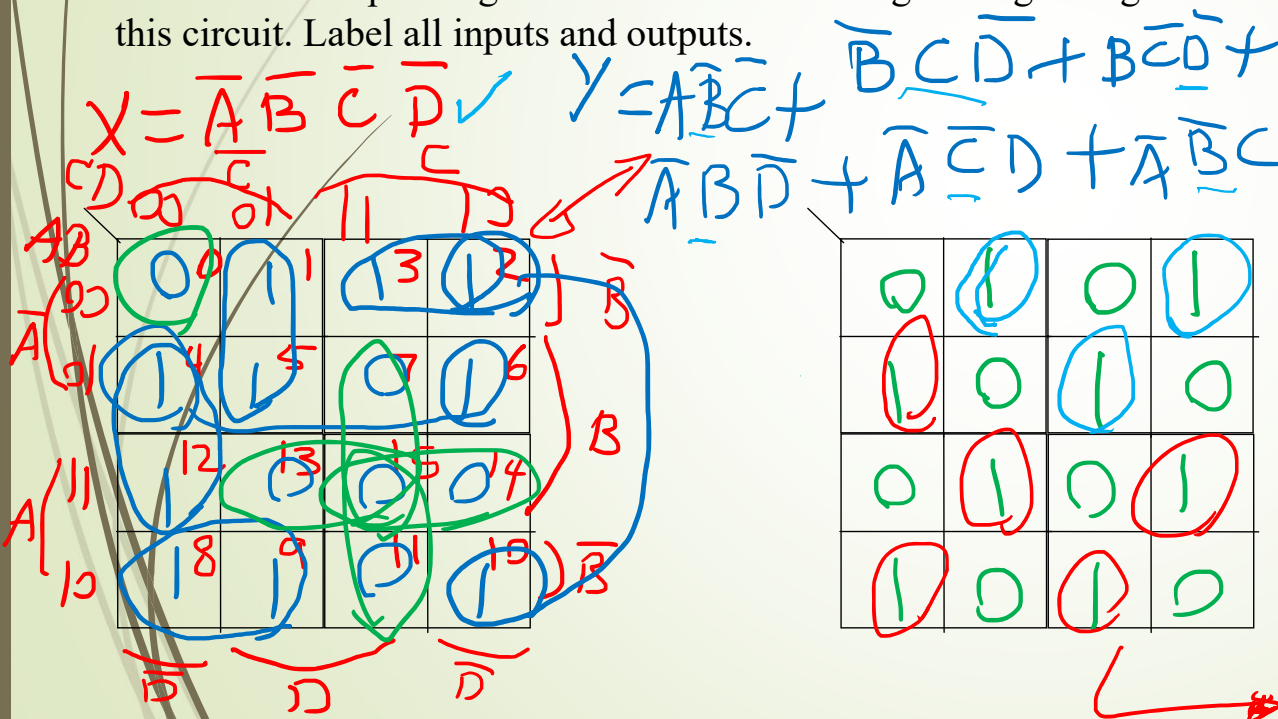

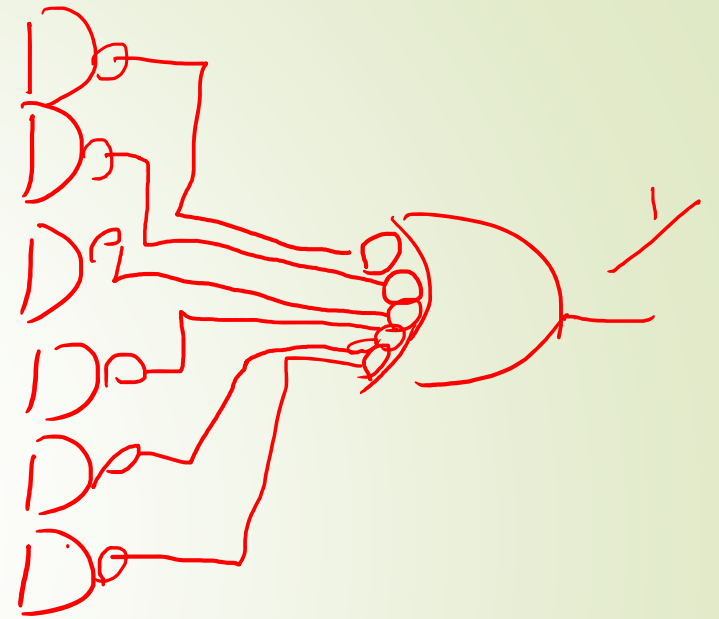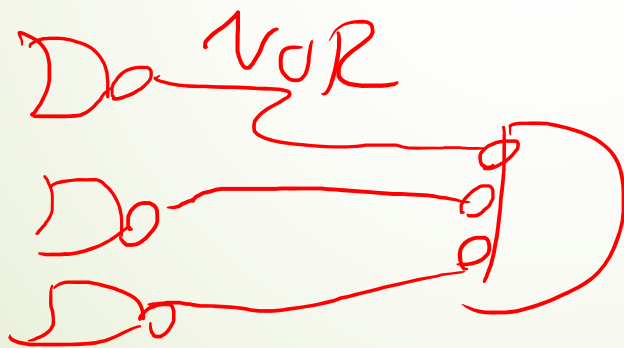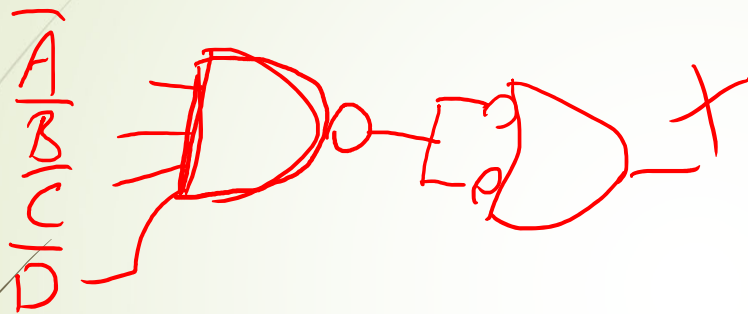

Problem 1 Design a circuit that counts the number of 0's present in 4 inputs A, B, C and D. Its output is a multi-bit, representing that count in binary. For example, 0101 has two zeros and therefore the output should be a binary representing 2.

a. Write the truth table for this circuit.

b. Find the minimized logic equations in SOP and POS for each output.

c. Draw the corresponding all NAND and all NOR gates logic diagram for this circuit. Label all inputs and outputs.

A	B	C	D	X	Y	Z
0	0	0	0	1	0	0
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	0	1
0	1	1	0	0	0	1
0	1	1	1	0	0	0
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	0	0	1
1	1	0	1	0	1	0
1	1	1	0	0	0	1
1	1	1	1	0	0	0

All NAND NOR

$$X = \bar{A}\bar{B}\bar{C}\bar{D} + BCD + ACD + ABC + ABD$$



$$Y = (A+B+C+D)(B+\bar{C}+\bar{D})(\bar{A}+\bar{C}+\bar{D})(\bar{A}+\bar{B}+\bar{C})(\bar{A}+\bar{B}+\bar{D})$$

$$X = \bar{A}\bar{B}\bar{C}\bar{D}$$

$$Y = \bar{A}B\bar{D} + \bar{A}B\bar{C} + \bar{A}C\bar{D}$$

$$Y = \sum m(0, 7, 11, 13, 14, 15) + \bar{A}\bar{B}\bar{C} + \bar{B}C\bar{D} + \bar{A}C\bar{D}$$
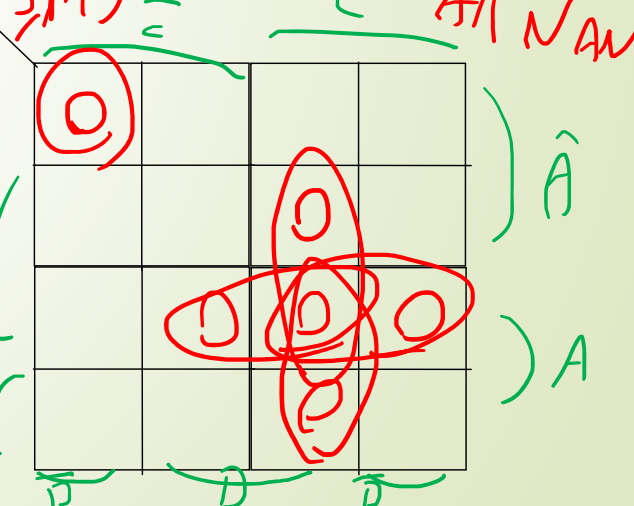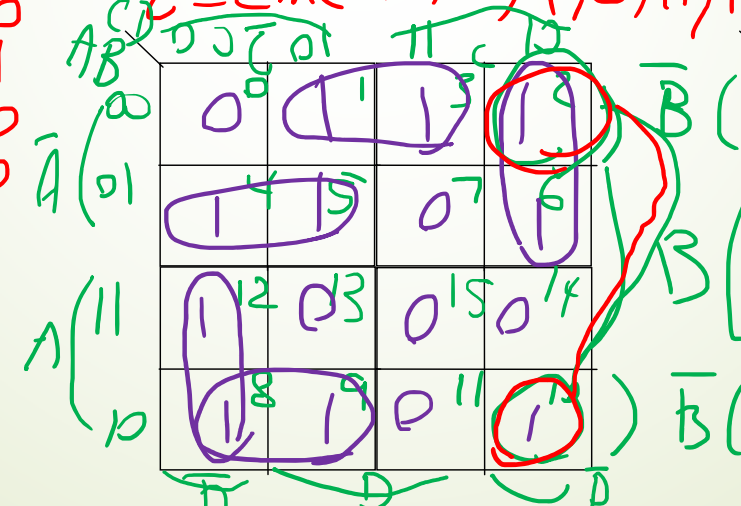
$$Z = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$



All NAND

$Z = \{2, 5, 7, 8, 11, 13, 14\}$  ✓ All NAM

$Z = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}c\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}cD + A\bar{B}c\bar{D} + ABC\bar{D}$

	0	1	3	2
1	4	5	7	6
	12	13	15	14
1	8	9	11	10


$+ A\bar{B}cD$   
 $+ A\bar{B}c\bar{D}$

All NAM

$Z = \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}cD + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}D + A\bar{B}c\bar{D} + A\bar{B}cD + ABC\bar{D}$

$Z = (A+B+c+D)(A+B+c+\bar{D})(A+\bar{B}+C+\bar{D})(A+\bar{B}+\bar{C}+D)(\bar{A}+B+c+\bar{D})(\bar{A}+B+\bar{C}+D)(\bar{A}+B+c+D)$

### Problem 1


Design a circuit that counts the number of 0's present in 4 inputs A, B, C and D. the input is BCD. Its output is a multi-bit, representing that count in binary. For example, 0101 has two zeros and therefore the output should be a binary representing 2.

- Write the truth table for this circuit.
- Find the minimized logic equations in SOP and POS for each output
- Draw the corresponding all NAND and all NOR gates logic diagram for this circuit. Label all inputs and outputs.


0-9 → BCD

A	B	C	D	X	Y	Z
0	0	0	0	1	0	0
0	0	0	1	0	1	1
0	0	1	0	0	1	1
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	0	1
1	0	0	0	0	1	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	1	0
1	1	0	0	0	1	0
1	1	0	1	0	1	0
1	1	1	0	0	1	0
1	1	1	1	0	0	1

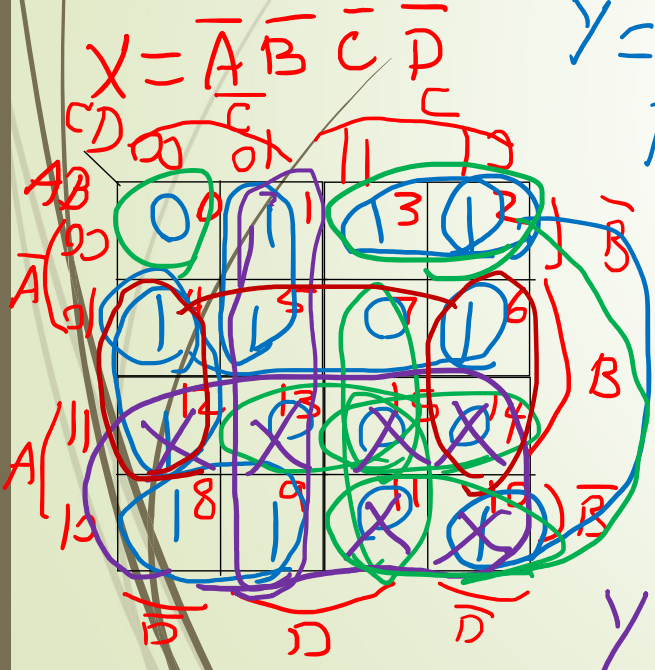$Y = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 11, 13, 14, 15)$   
 $Z = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 11, 13, 14, 15)$



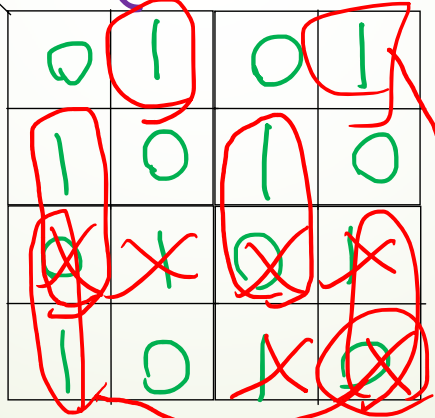~~$Y = \overline{A} \overline{B} \overline{C} + \overline{B} \overline{C} \overline{D} + \overline{B} \overline{C} D + \overline{A} B \overline{D} + \overline{A} C D + \overline{A} B C$~~



$Y = A + \overline{C} D + B \overline{D} + \overline{B} C$



	$\bar{C}$	$C$	
	0	1	
$AB$ (0)	X	0	X
$\bar{A}$ (1)	0	0	X
$A$ (1)	X	0	1
$\bar{A}$ (0)	0	0	X

Min. S.O.P

$$F = C$$

All NAND

$C \text{ --- } F \checkmark$

Problem 2

$$G = \sum m(4, 8, 9, 12, 13, 14) \quad E = \sum m(0, 5, 10, 15)$$

Design a circuit with inputs A, B, C, and D. Let the two inputs AB represent a two-bit number with A as the high order bit, and CD represent another two-bit number. That is, the values on AB represent four values 00 (0), 01 (1), 10 (2), and 11 (3). The circuit has three outputs: G, E, and L. Output G, E, and L should be 1 only if the number represented by AB is greater, equal, and less than the number represented by CD, respectively.


- Write the truth table for this circuit.
- Find the minimized logic equations in SOP and POS for each output
- Draw the corresponding all NAND and all NOR gates logic diagram for this circuit. Label all inputs and outputs.

$AB > CD$   
 $AB = CD$   
 $AB < CD$


$$L = \sum m(1, 2, 3, 6, 7, 11)$$

A	B	C	D	G	E	L
0	0	0	0	0	1	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	0	0
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0


A	B	C	D	G	E	L
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

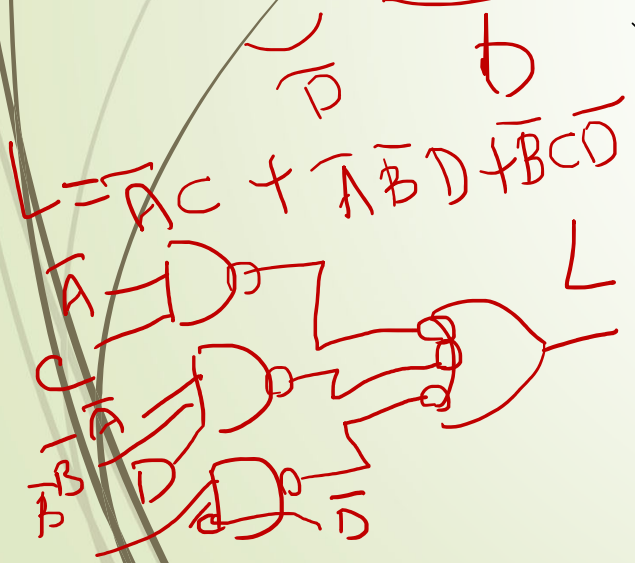
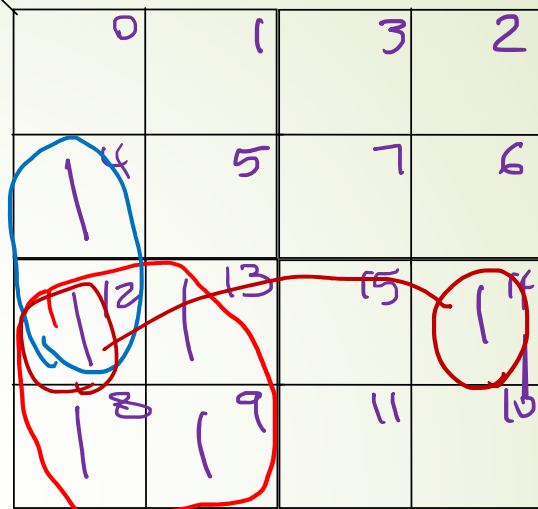
$$G = A\bar{C} + B\bar{C}\bar{D} + A\bar{B}\bar{D}$$


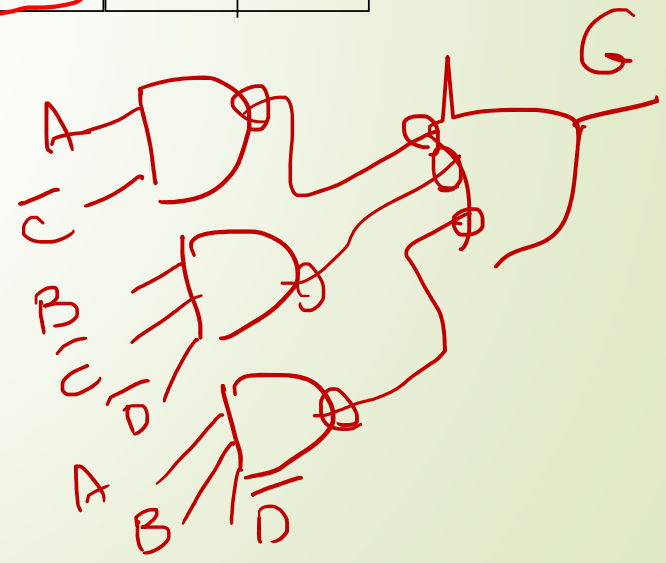
$$E = \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D$$



3. Design a circuit that can convert a BCD code into a Gray. a. Write the truth table for this circuit. b. Find the minimized logic equations in SOP and POS for each output c. Draw the corresponding all NAND and all NOR gates logic diagram for this circuit. Label all inputs and outputs.

0	00	0	000
1	01	1	001
	<hr/>	2	011
	11	3	010
	10	4	<hr/>
		5	110
		6	111
		7	101
			100
			3 bits

1 bit

2 bits

Binary  $\downarrow$        $\uparrow$  Gray

CKT to convert 2 bit binary to Gray

A	B	X	Y
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

$X = A$   
 $Y = A \oplus B$

Gray code to binary

X	Y	A	B
0	0	0	0
0	1	0	1
1	1	1	1
1	0	1	0

$A = X$   
 $B = X \oplus Y$

binary to Gray

A	B	Gray
0	0	000
0	1	001
0	0	010
0	1	011
1	0	100
1	1	101
1	0	110
1	1	111

$G = A$

# GRAY Code

00  
01  
—  
11  
10

0000  
0001  
0011  
0010  
—  
1100  
1101  
1111  
1011  
1010

$$Y = \sum m(1, 2, 5, 6) + d(9)$$

$$G(A, B, C, D) = \sum m(8, 9) + d(10, 11, 12, 13, 14, 15)$$

$$R(A, B, C, D) = \sum m(4, 5, 6, 7, 8, 9) + d( \quad )$$

$$E(A, B, C, D) = \sum m(2, 3, 4, 5) + d( \quad )$$

BCD → GRAY

BCD

A	B	C	D	GRAY	
0	0	0	0	0000	0
0	0	0	1	0001	1
0	0	1	0	0011	2
0	0	1	1	0010	
0	1	0	0	0110	
0	1	0	1	0111	
0	1	1	0	0101	
0	1	1	1	0100	
1	0	0	0	1100	
1	0	0	1	1101	
1	0	1	0	1111	don't
1	0	1	1	1110	care
1	1	0	0	1010	
1	1	0	1	1011	
1	1	1	0	1001	
1	1	1	1	1000	15

BCD → GRAY

ABCD	GREY
0000	0000
0001	0001
0010	<u>0011</u>
0011	0010
0100	0110
0101	0111
<u>0110</u>	0101
0111	<u>0100</u>
1000	1100 ←
1001	1101
1010	<del>1111</del>
1011	<del>1110</del>
1100	<del>1010</del>
1101	<del>1011</del>
1110	<del>1001</del>
1111	1000

GRAY → BCD

GREY	ABCD
0000	0000
0001	0001
0010	0011
0011	0010
0100	0110
0101	0111
0110	0101
0111	0100
1000	1100
1001	1101
1010	<del>1111</del>
1011	<del>1110</del>
1100	<del>1010</del>
1101	<del>1011</del>
1110	<del>1001</del>
1111	1000


$$A = \sum m(\quad)$$

$$B = \sum m(\quad)$$

ABCD | WXYZ

0000 0000  
0001 0001  
0010 0011  
0011 0010  
0100 0110  
0101 0111  
0110 0101  
0111 0100  
1000 1100  
1001 1101  
1010 1111  
1011 1110  
1100 1010  
1101 1011  
1110 1001  
1111 1000


W

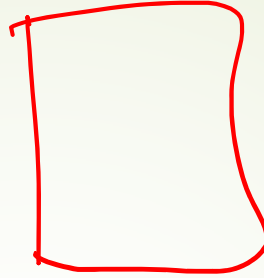


X



Y

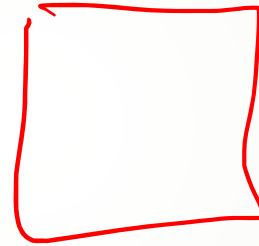


Z

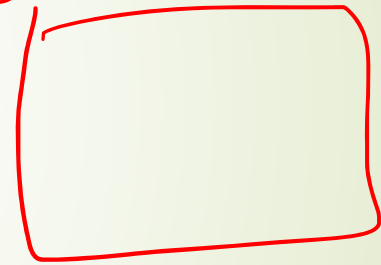



# FULL ADDER

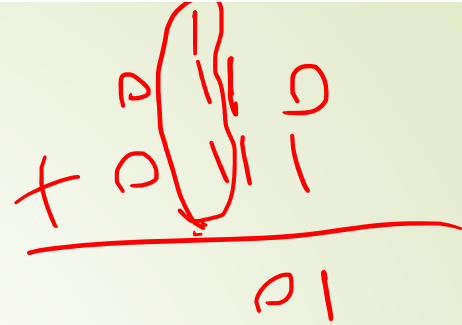

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$\bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$\bar{A}(B \oplus C) + A(\overline{B \oplus C})$$

$$\text{sum} = \bar{A}X + A\bar{X}$$

$$= A \oplus X$$

$$= A \oplus B \oplus C_{in}$$

K-MAP

$$C_{out} = AB + BC_{in} + AC_{in}$$

$$C_{out} = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$C(A \oplus B) + AB$$

