

EGC220 Class Notes 4/14/2023



Baback Izadi

Division of Engineering Programs

bai@enr.newpaltz.edu

Test 2 will cover the following topics


- ▶ Design of combinational circuits
 - ▶ Circuit conversion to all NAND or NOR gates
- ▶ Design and use of
 - ▶ Multiplexers
 - ▶ Demultiplexers
 - ▶ Decoders
 - ▶ Encoders
- ▶ Design of combinational circuits using PLD's
- ▶ Latch and flip flops characteristics and timing.
- ▶ Design of ripple counters
- ▶ Analysis of sequential circuits

CLK


QA

QB

QD	QC	QB	QA
0	0	0	0
1	0	1	0
BS	CLR	PS	

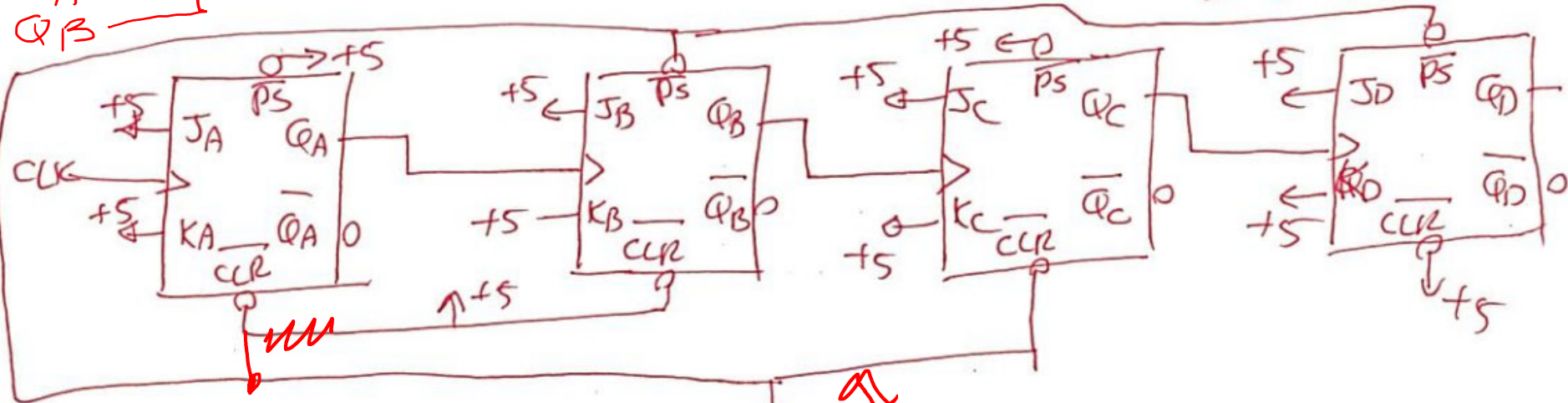

Synchronous Circuit

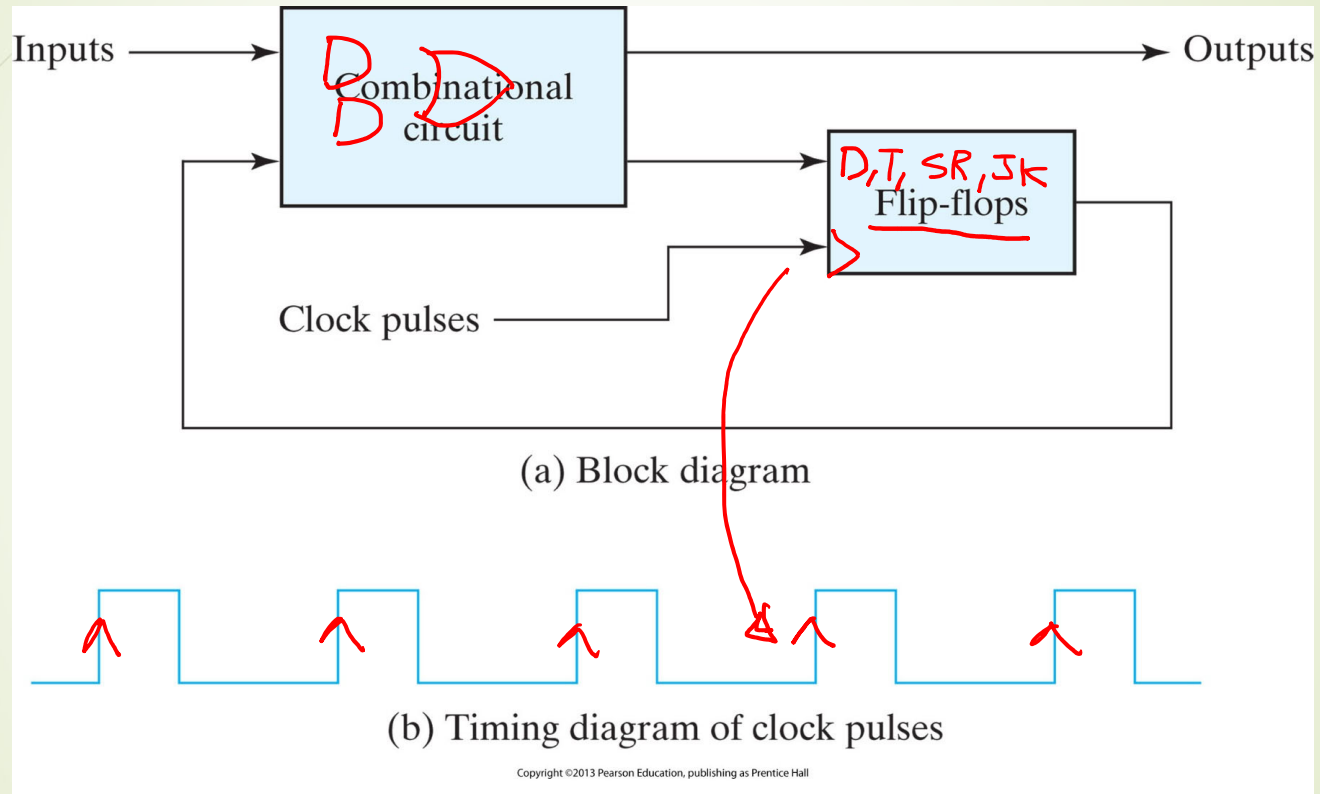

How do we determine its functionality?

Flip Flops Vs. Latches

- Flip flops are Edge Triggered
- ~~Latches are level triggered~~


only use F/F
for design & analysis

(a) JK Flip-Flop


J	K	Q (t + 1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	$\bar{Q}(t)$	Complement

(b) SR Flip-Flop


S	R	Q (t + 1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

 


┌ Triggered JK

 

┐ Triggered JK

 

┌ Triggered JK

 


┐ Triggered JK


Flip Flops Vs. ~~Latches~~

- Flip flops are Edge Triggered
- ~~Latches are level triggered~~


(c) D Flip-Flop			(d) T Flip-Flop		
D	Q (t + 1)	Operation	T	Q (t + 1)	Operation
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$\overline{Q}(t)$	Complement

 


┌ Triggered D

 

└ Triggered D

 

┌ Triggered T

 

└ Triggered T




Analysis of Sequential Circuits

- **Analysis Procedure:**
 - **Obtain flip-flop input equations**
 - **Write down characteristic table of each type of flip-flop in use**
 - **Develop state table**
 - **Obtain state diagram**

Example #1:

system
input

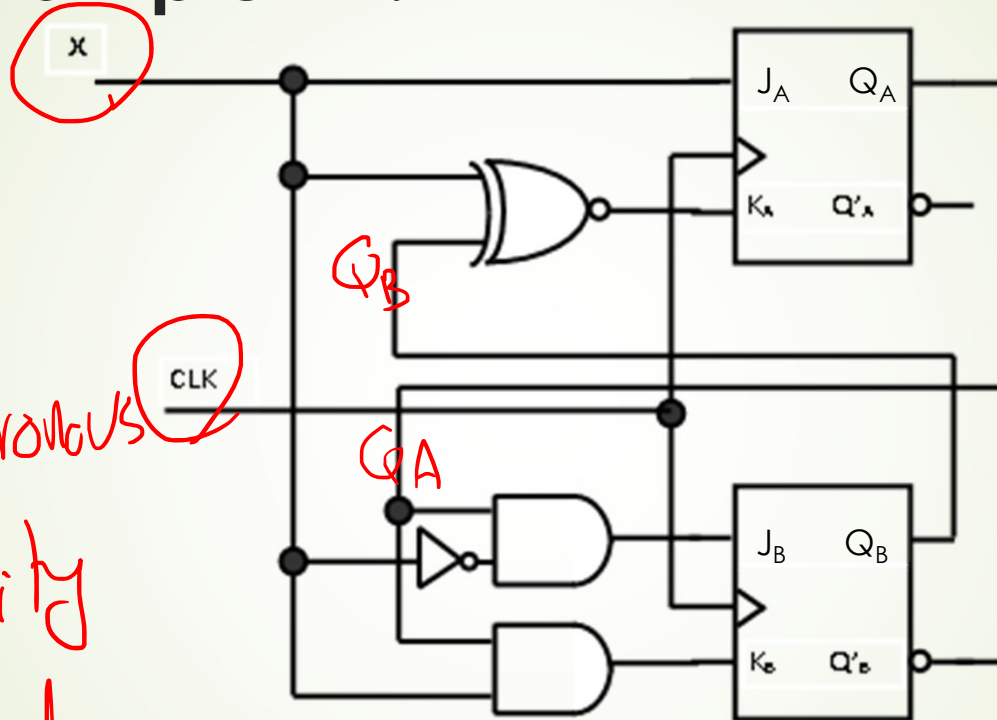

synchronous

Functionality

does not depend
on \uparrow or \downarrow CLK.

Step 1: Flip-flop input equations and output equation

$$J_A = X$$

$$K_A = \overline{Q_B \oplus X} = Q_B \odot X$$

$$J_B = Q_A X'$$

$$K_B = Q_A X$$

Step 2: Characteristic Table


J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Step 3: State Table

PS			F/F inputs				NS	
Q _A	Q _B	X	J _A	K _A	J _B	K _B	Q _A	Q _B
0	0	0	0	1	0	0	0	0
0	0	1	1	0	0	0	1	0
0	1	0	0	0	0	0	0	1
0	1	1	1	1	0	0	1	1
1	0	0	0	1	1	0	0	1
1	0	1	1	0	0	1	1	0
1	1	0	0	0	1	0	1	1
1	1	1	1	1	0	1	0	0


Step 4: State Diagram

Q_AQ_B
 0 0
 0 1
 1 0
 1 1

 

Example #2:

X: system input
Z: system output

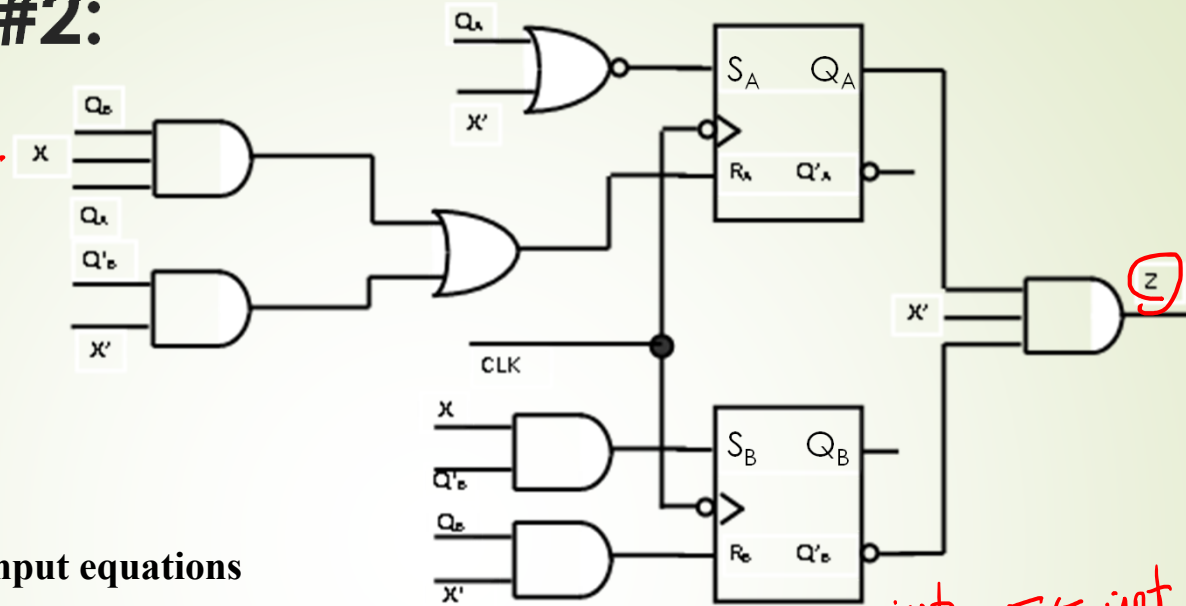

Step 1: Flip-flop input equations and output equation

$$S_A = (Q_A + X)' = Q'_A X$$

$$R_A = Q_A Q_B X + Q'_B X'$$

$$S_B = Q'_B X$$

$$R_B = Q_B X'$$

$$Z = Q_A Q'_B X'$$

Step 2: Characteristic Table

S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	--

ps	input	F/F input	NS	output					
QA	QB	X	SA	RA	SB	RB	QA	QB	Z
0	0	0							
:	:	:	using F/F input equations				using F/F input & chara. table	using equ.	
:	:	:							
:	:	:							
:	:	:							
1	1	1							

Problem 1

Analyze the following sequential circuits leading to a state diagram.

$$J_A = K_A = Q_B Q_C X + \overline{Q_B} \overline{Q_C} \overline{X} \quad \checkmark$$


$$J_B = K_B = X \oplus Q_C = \overline{Q_C} \oplus X$$

$$J_C = K_C = 1$$

$$Z = \overline{Q_B} Q_A \quad \overline{Q_B} Q_A$$


$Q_B + \overline{Q_A}$

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

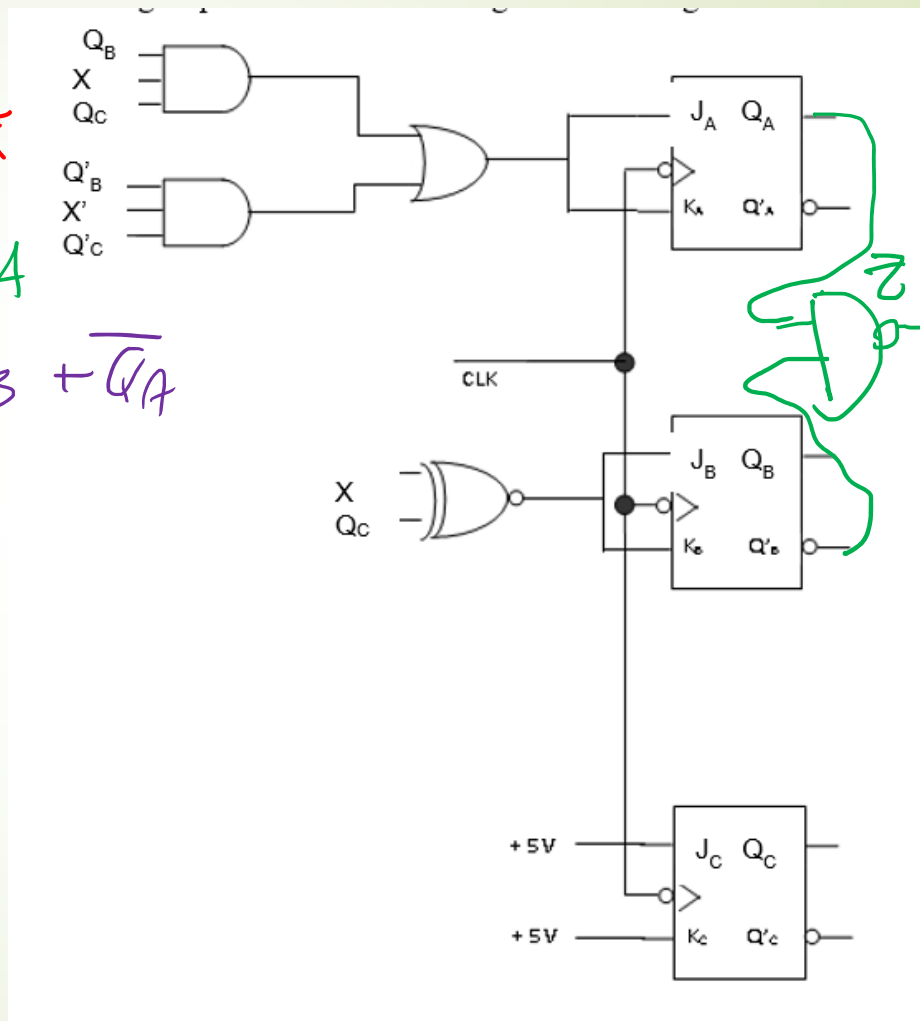



0-7
up/down
counter

 

Problem 2



Analyze the following sequential circuits leading to a state diagram.

1. $T_A = 1$; $T_B = Q_A$; $T_C = Q_A Q_B$

2. $T \mid Q(t+1)$
 $\begin{array}{c|c} 0 & Q(t) \\ 1 & \bar{Q}(t) \end{array}$

PS NS


Q_A	Q_B	Q_C	T_A	T_B	T_C	Q_A	Q_B	Q_C
0	0	0	1	0	0	1	0	0
0	0	1	1	0	0	1	0	1
0	1	0	1	0	0	1	1	0
0	1	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1	0
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	1	1	1	0	0	0

 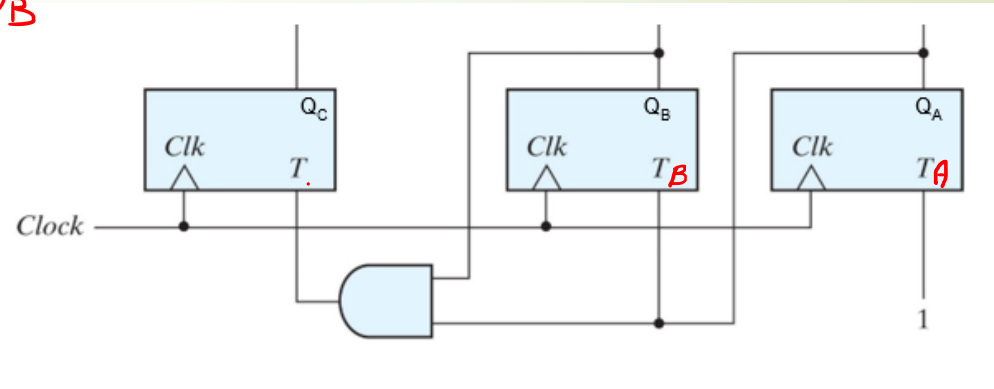

Problem 3

Analyze the following circuit leading to its state diagram.

\bar{Q}_A	Q_A	Q_B	X	FF inputs SUM D_A	inputs Cout D_B	NS Q_A	Q_B	output Z
1	0	0	0	1	0	1	0	1
1	0	0	1	0	1	0	1	0
1	0	1	0	0	1	0	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	0	0	1
1	1	0	1	1	0	1	0	0
1	1	1	0	1	0	1	0	0
1	1	1	1	0	1	0	1	0
0	0	0	0	0	1	0	0	1

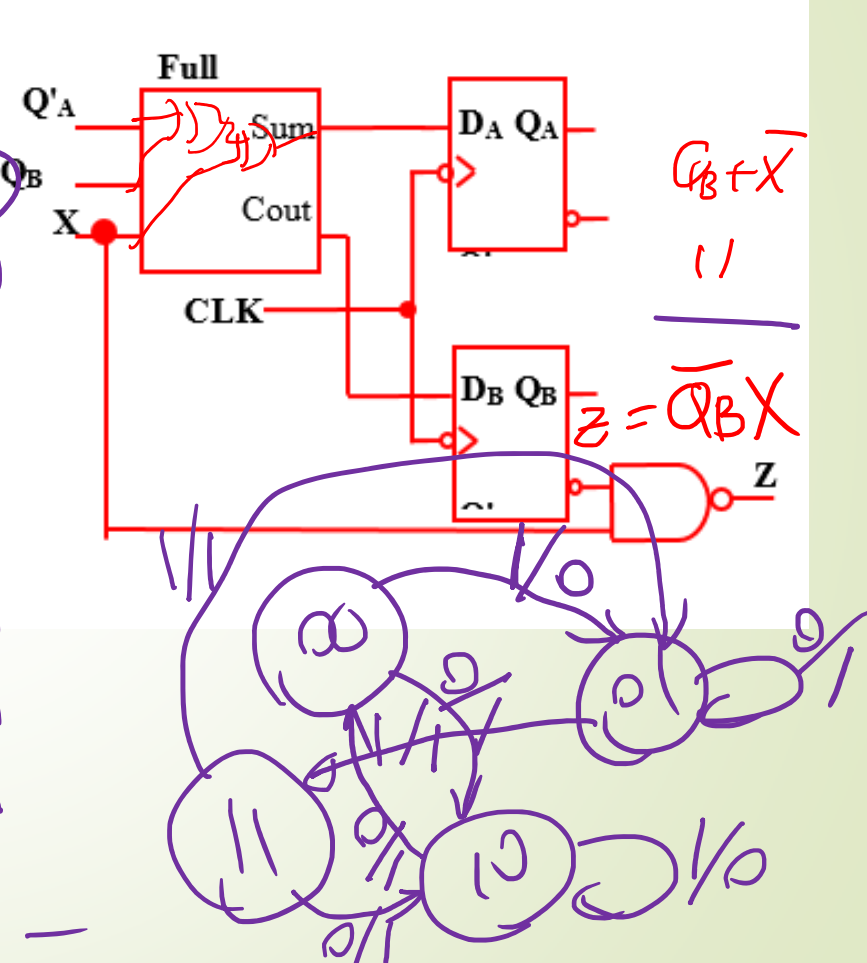

Data flow
assign → equation

behav.

describe ckt
@ (x, n, x)
case

