

EGC220

Class Notes

4/28/2023

Baback Izadi

Division of Engineering Programs

bai@enr.newpaltz.edu

Flip-Flop Excitation Tables

PRESENT STATE	NEXT STATE	S	R
Q(t)	Q(t+1)		
0	0	0	X
0	1	1	0
1	0	0	1
1	1	x	0



Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

PRESENT STATE	NEXT STATE	J	K
Q(t)	Q(t+1)		
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0



Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Moore Vs Mealy FSMs: different output generation

- Moore FSM:

 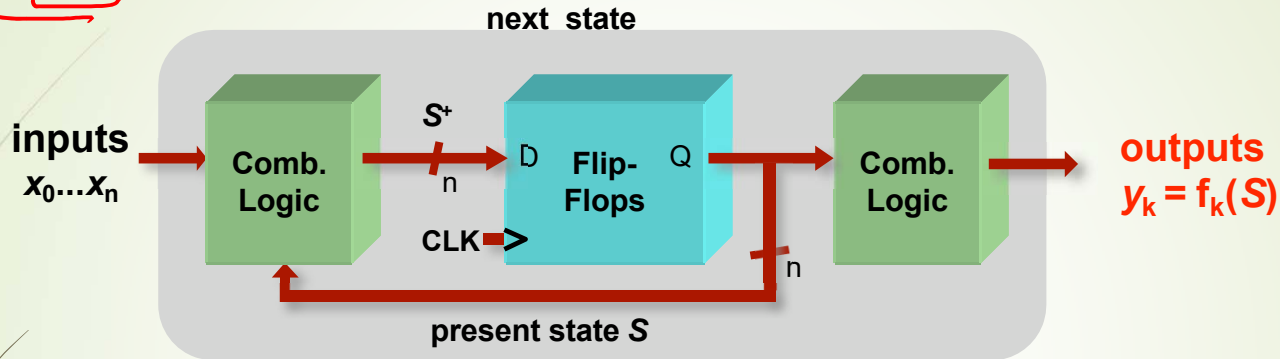

- Mealy FSM:

  

Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within always blocks, with subtly different behaviors.
- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
x = a | b;
```

1. Evaluate $a | b$, assign result to x

```
y = a ^ b ^ c;
```

2. Evaluate $a^b c$, assign result to y

```
z = b & ~c;
```

3. Evaluate $b \& (\sim c)$, assign result to z

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
x <= a | b;
```

1. Evaluate $a | b$ but defer assignment of x

```
y <= a ^ b ^ c;
```

2. Evaluate $a^b c$ but defer assignment of y


```
z <= b & ~c;
```

3. Evaluate $b \& (\sim c)$ but defer assignment of z

```
end
```

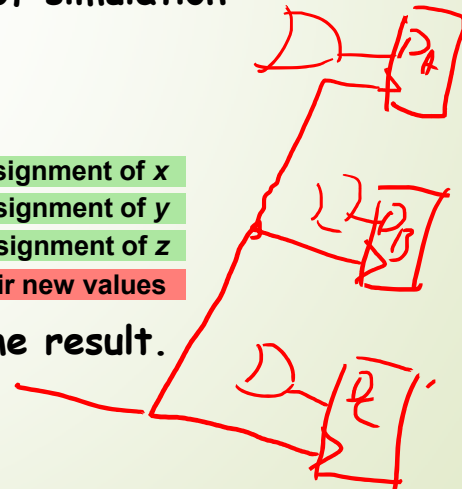
4. Assign x , y , and z with their new values

- Sometimes, as above, both produce the same result. Sometimes, not!



Finite State Machines Example

- State diagrams are representations of *Finite State Machines (FSM)*
- Mealy FSM
 - Output depends on input and state
 - Output is not synchronized with clock can have temporarily unstable output
- Moore FSM
 - Output depends only on state

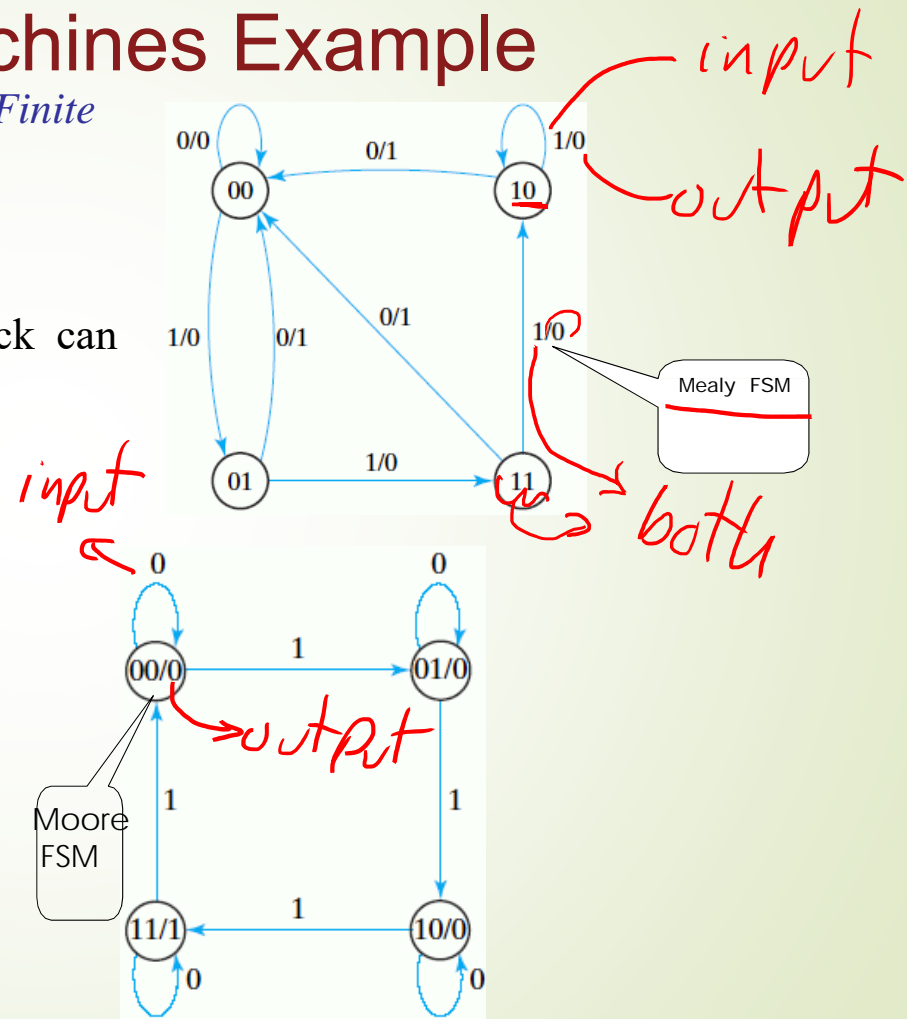


Problem 1

Using D flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume no overlapping.

10101 10101

1010
1011

 

1111100

S_N: nothing detected
 S₋₁: 1 is detected
 S₋₁₀: 10 "
 S₋₁₀₁: ✓

S _N	S ₋₁
S ₋₁	S ₋₁₀


PS			NS		Z
Q_A	Q_B	X	D_A	D_B	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	1	0

Q_B	X	0	1
0	0	1	0
1	1	0	0

$$D_A = \overline{Q_A} \overline{Q_B} + \overline{Q_A} X$$

$$D_B = \overline{Q_A} \overline{Q_B} X + \overline{Q_A} Q_B X$$

$$Z = \overline{Q_A} Q_B$$

 


Problem 2

Write a Verilog code for Problem 1

```
module seq3_detect_moore(x,clk, y);
// Moore machine for a sequence 101
input x, clk;
output y;
reg [1:0] state;

parameter S0=2'b00, S1=2'b10, S2=2'b11, S3=2'b01;

// Define the sequential block
always @(posedge clk)
case (state)
S0: if (x) state <= S1;
    elsestate <= S0;
S1: if (x) state <= S1;
    elsestate <= S2;
S2: if (x) state <= S3;
    else state <= S0;
S3: if (x) state <= S1;
    else state <= S0;
endcase
// Define output during s3
assign y = (state == S3);
endmodule
```

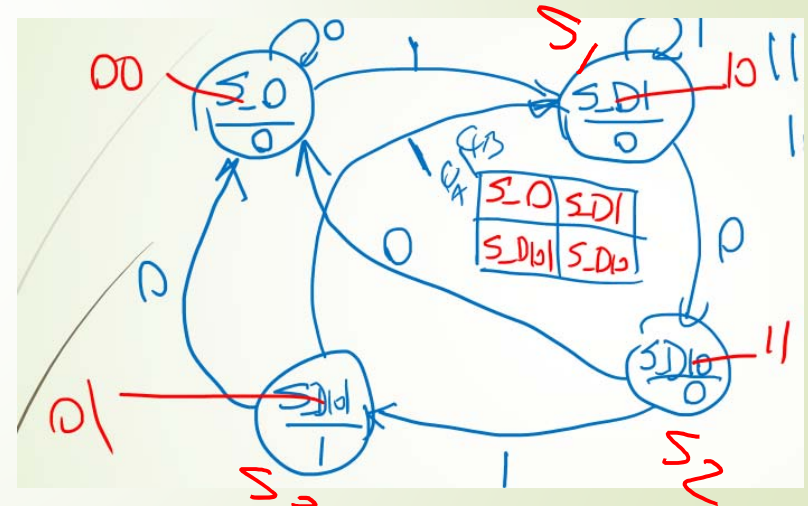


Problem 3

Using JK flip-flops, design a Mealy based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume no overlapping.

1110 101
100

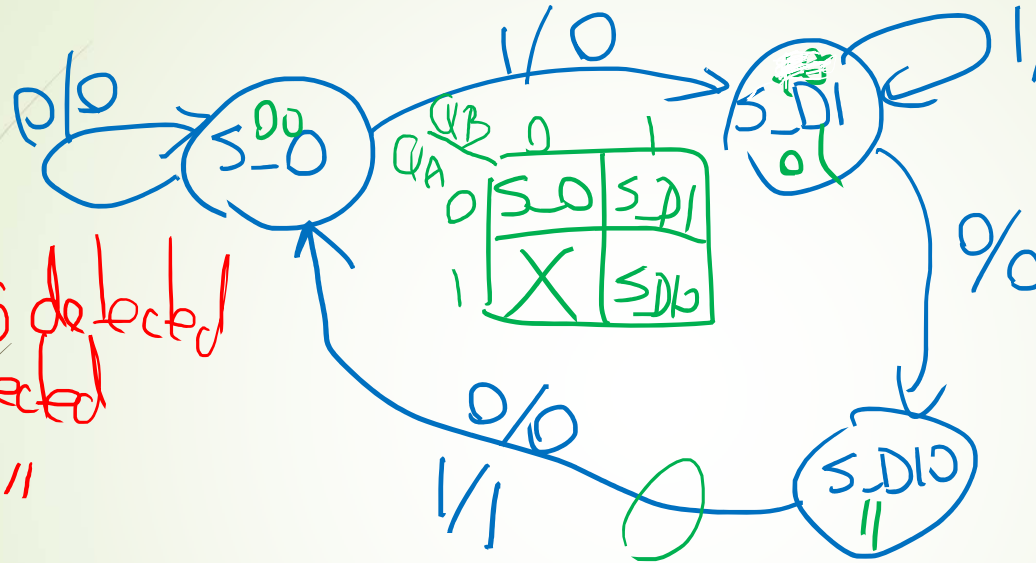S₀: Nothing detected
S₁: 1 detected
S₂: 10 11




	QA	QB
0	S ₀	S ₁
1	X	S ₂

PS	NS	QA	QB	X	J	K	Z
00	00	0	0	0	+	-	0
00	10	1	0	1	+	-	0
01	11	1	1	1	+	-	0
01	01	0	1	0	+	-	0
100	XX	X	X	X	X	X	X
101	XX	X	X	X	X	X	X
110	00	0	0	+	-	0	
111	00	0	0	+	-	1	

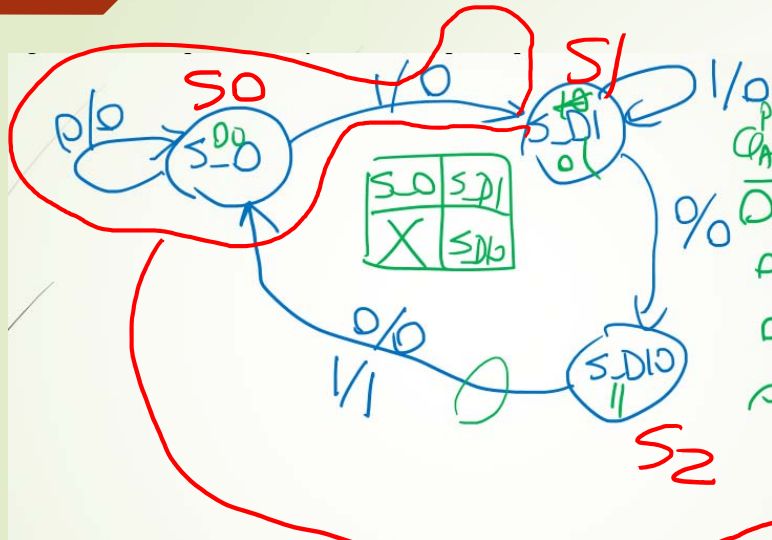Problem 4


Write a Verilog code for Problem 3. Use default flip-flop given by Verilog.



```
module seq3_detect_mealy(x,clk, y);  
  
// Mealy machine for a three-1s sequence detection  
input x, clk;  
  
output y; reg y;  
  
parameter S0=2'b00, S1=2'b01, S2=2'b11;  
  
// Next state and output combinational logic  
// Use blocking assignments "="  
always @(x or pstate)  
  
    case (pstate)  
        S0: if (x) begin nstate = S1; y = 0; end  
           else begin nstate = S0; y = 0; end  
        S1: if (x) begin nstate = S1; y = 0; end  
           else begin nstate = S2; y = 0; end  
        S2: if (x) begin nstate = S0; y = 1; end  
           else begin nstate = S0; y = 0; end  
    endcase  
  
// Sequential logic, use nonblocking assignments "<="   
    always @(posedge clk)  
        pstate <= nstate;  
  
endmodule
```

Problem 5

Using D flip-flops, design a Moore based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume overlapping.

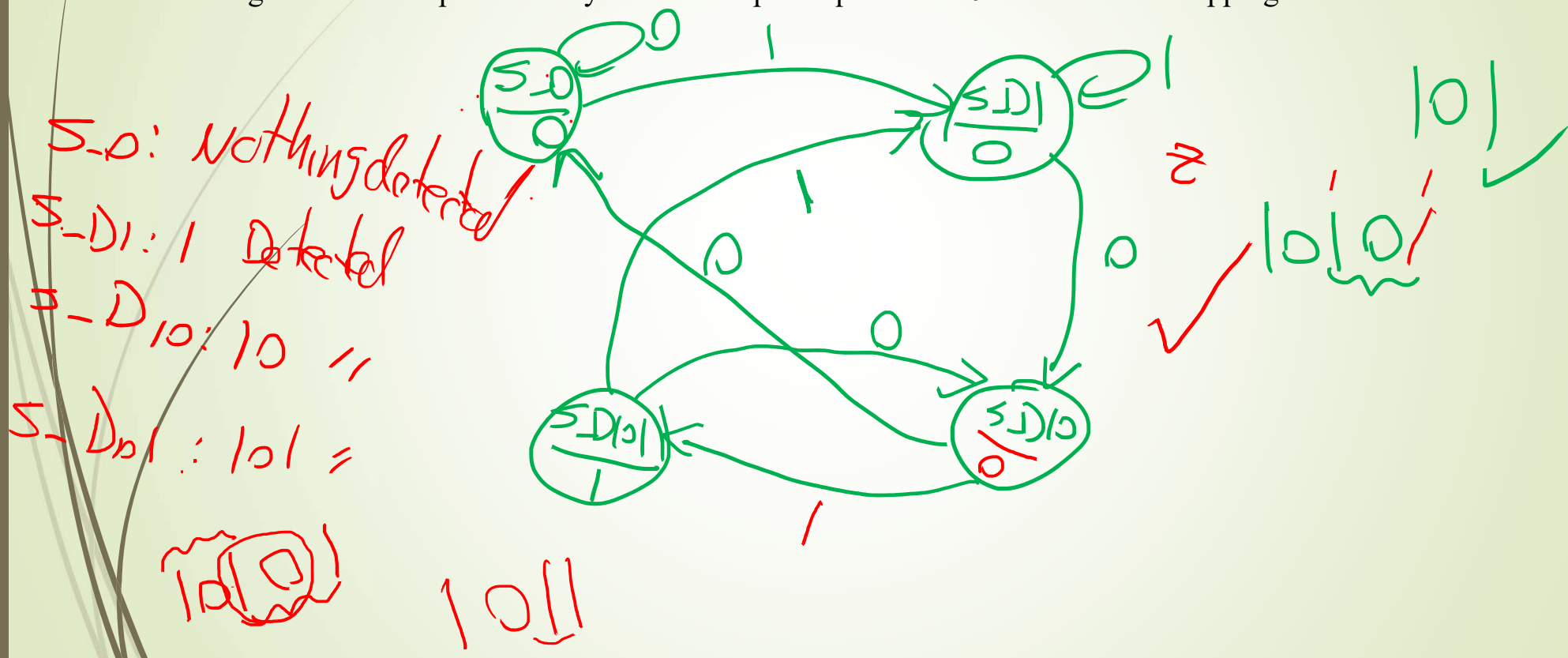

Problem 7

Using JK flip-flops, design a Mealy based sequence detector with one input and one output, which would generate an output of 1 only when the input sequence is 101. Assume overlapping.

