

EGC220 Class Notes 4/4/2023



Baback Izadi

Division of Engineering Programs

bai@engr.newpaltz.edu


1. Using Verilog, design an ALU with the following specification:

S	Function
0	A-B
1	A+B
2	A + 1
3	A - 1
4	A AND B
5	A OR B
6	A XOR B
7	A'


```
module alu(s, A, B, F);  
input [2:0] s;  
input [3:0] A, B;  
output [3:0] F;  
reg [3:0] F;  
always @(s or A or B)  
case (s)  
0: F = A - B;  
1: F = A + B;  
2: F = A + 1;  
3: F = A - 1;  
4: F = A & B;  
5: F = A | B;  
6: F = A ^ B;
```

```
7: F = ~ A;  
endcase  
endmodule
```


combinational circuits

 


sequential circuits

 


S-R Latch with NOR gates

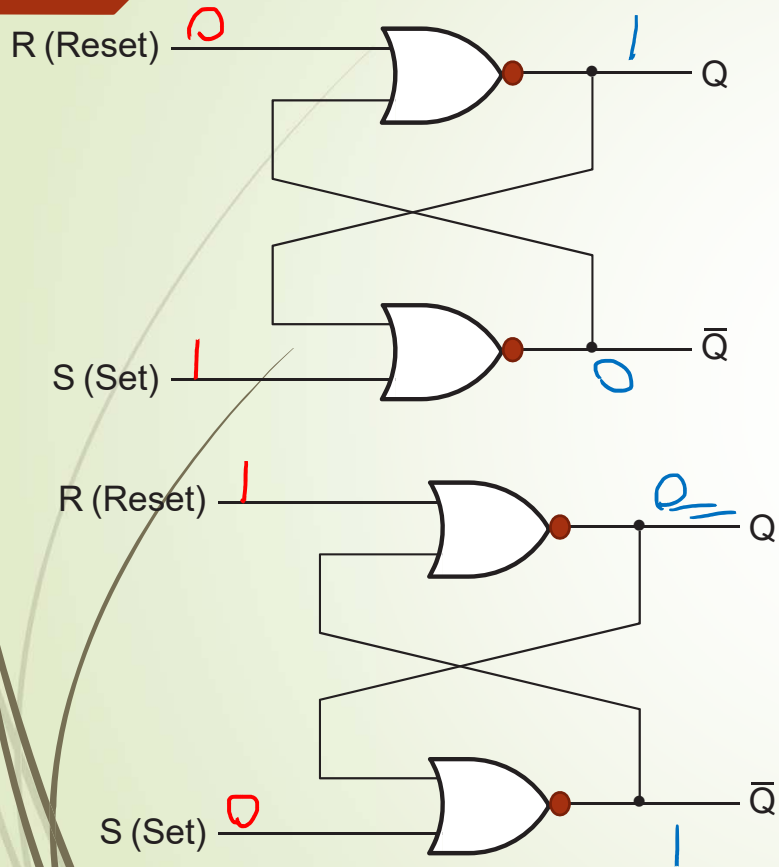


S	R	Q	Q̄	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

 

S	R	Q
0	0	Same as before
0	1	0
1	0	1
1	1	Not allowed!

 


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 


if one input is 1 output is 0

SR Latch

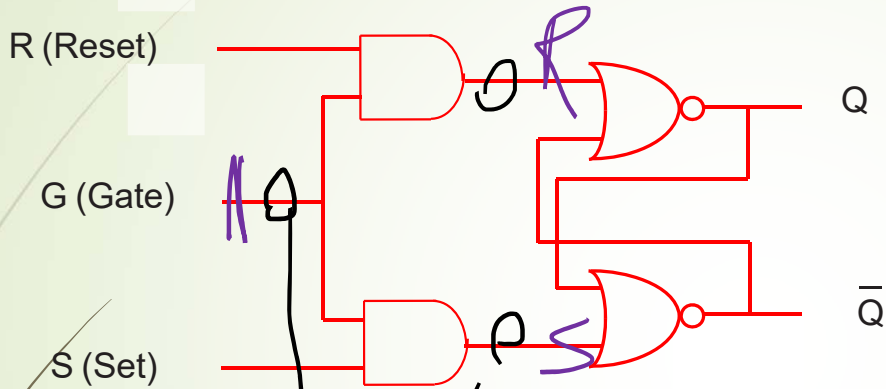

G	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

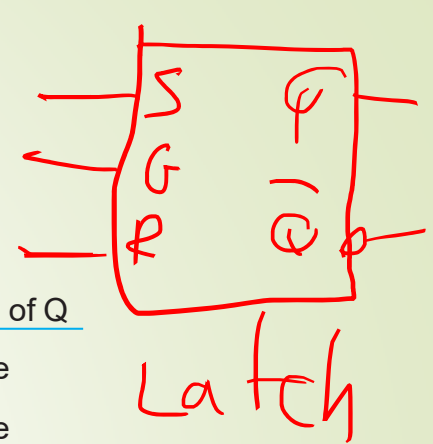


Clock

NO change



CLK

Not active

device is active

 


SR Latch

 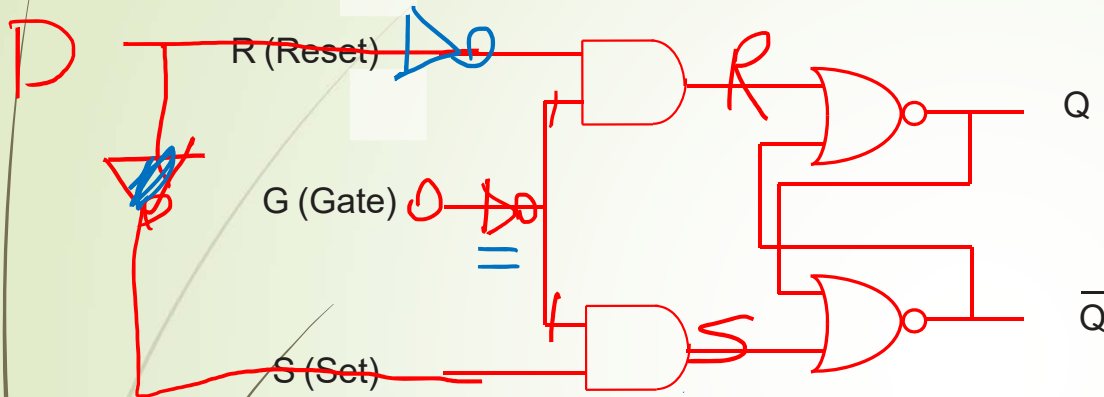

G	S	R	Next state of Q
1	X	X	No change
0	0	0	No change
0	0	1	Q = 0; Reset state
0	1	0	Q = 1; Set state
0	1	1	Undefined




D	S	R	Q
0	0	1	0
1	1	0	1

 

SR Latch with a Control Gate

Memory Device

D	S	R	Q
0	0	1	0
1	1	0	1

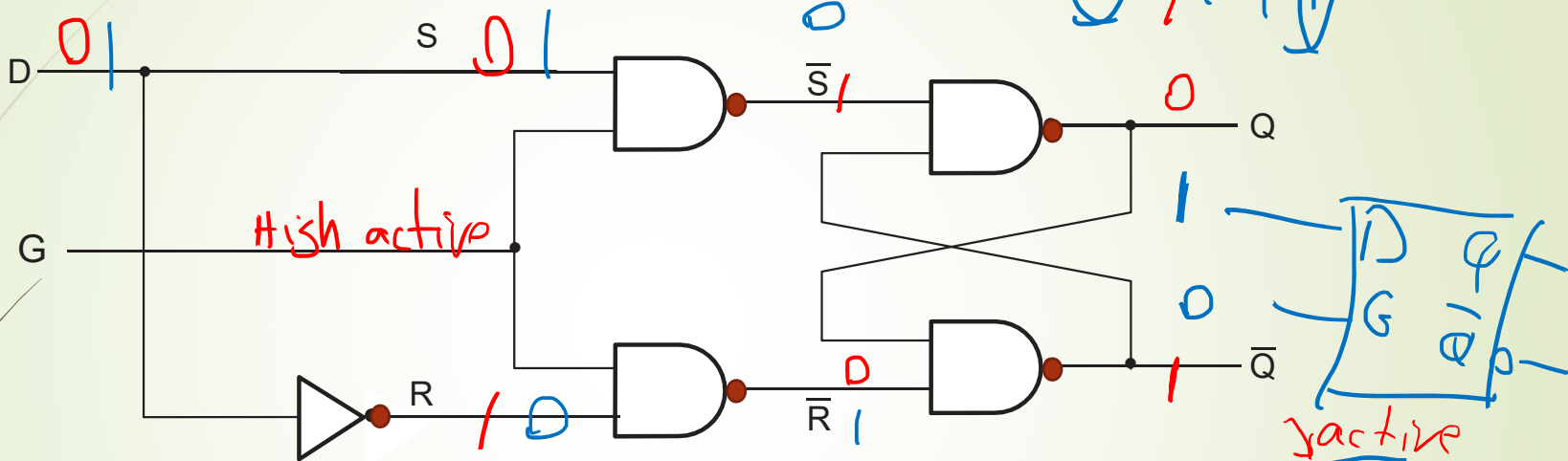


(a) Logic diagram

A	B
0	0
0	1
1	0
1	1


C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table

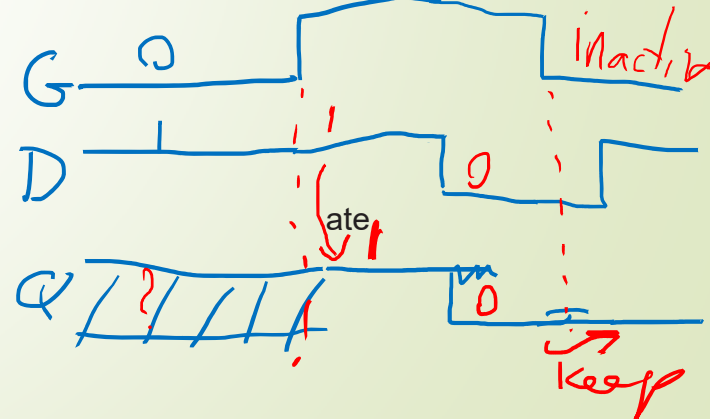


Problem 2

Complete the timing diagram if the following signals are applied as indicated.

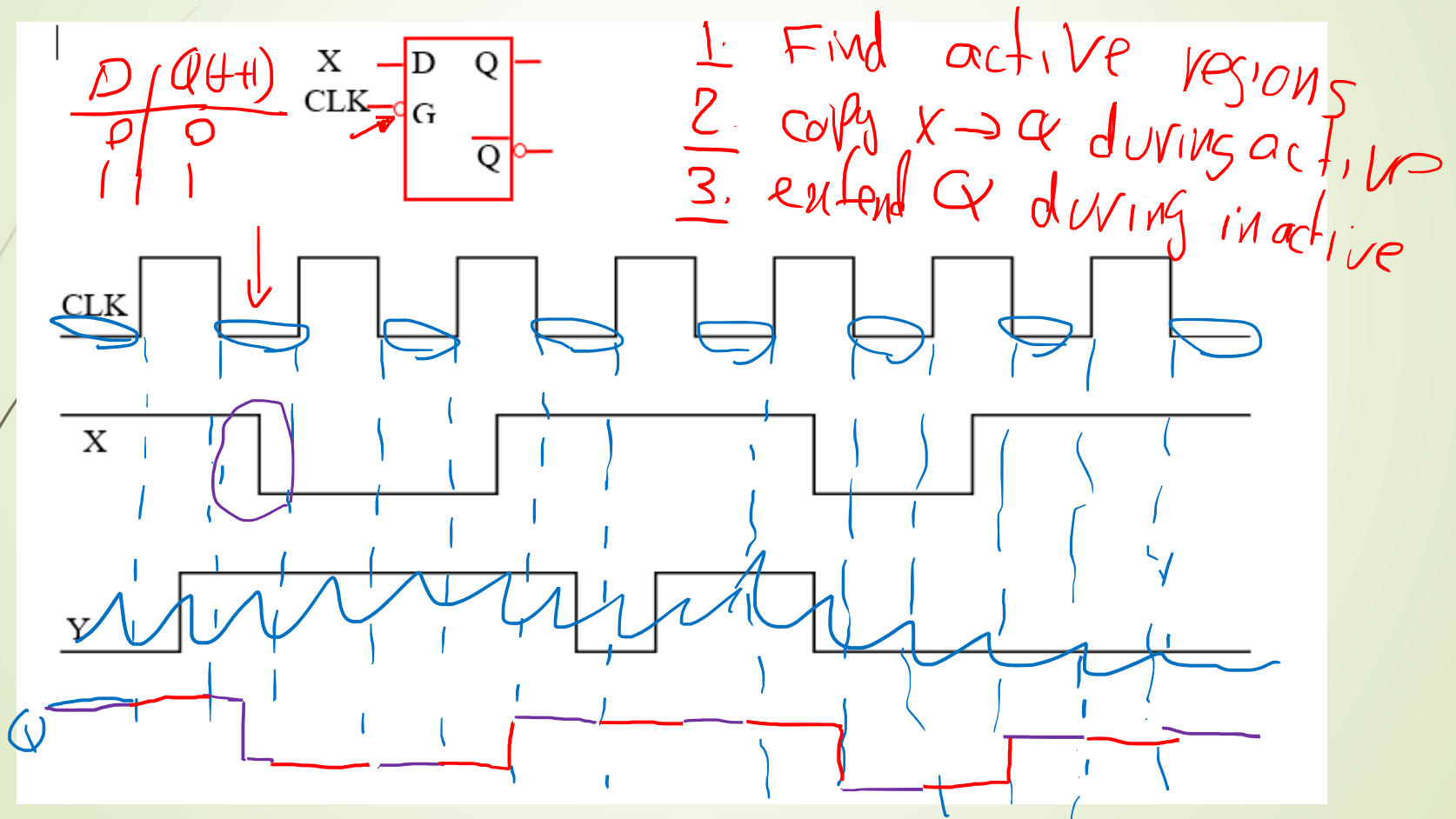

Problem 3

Complete the timing diagram if the following signals are applied as indicated.

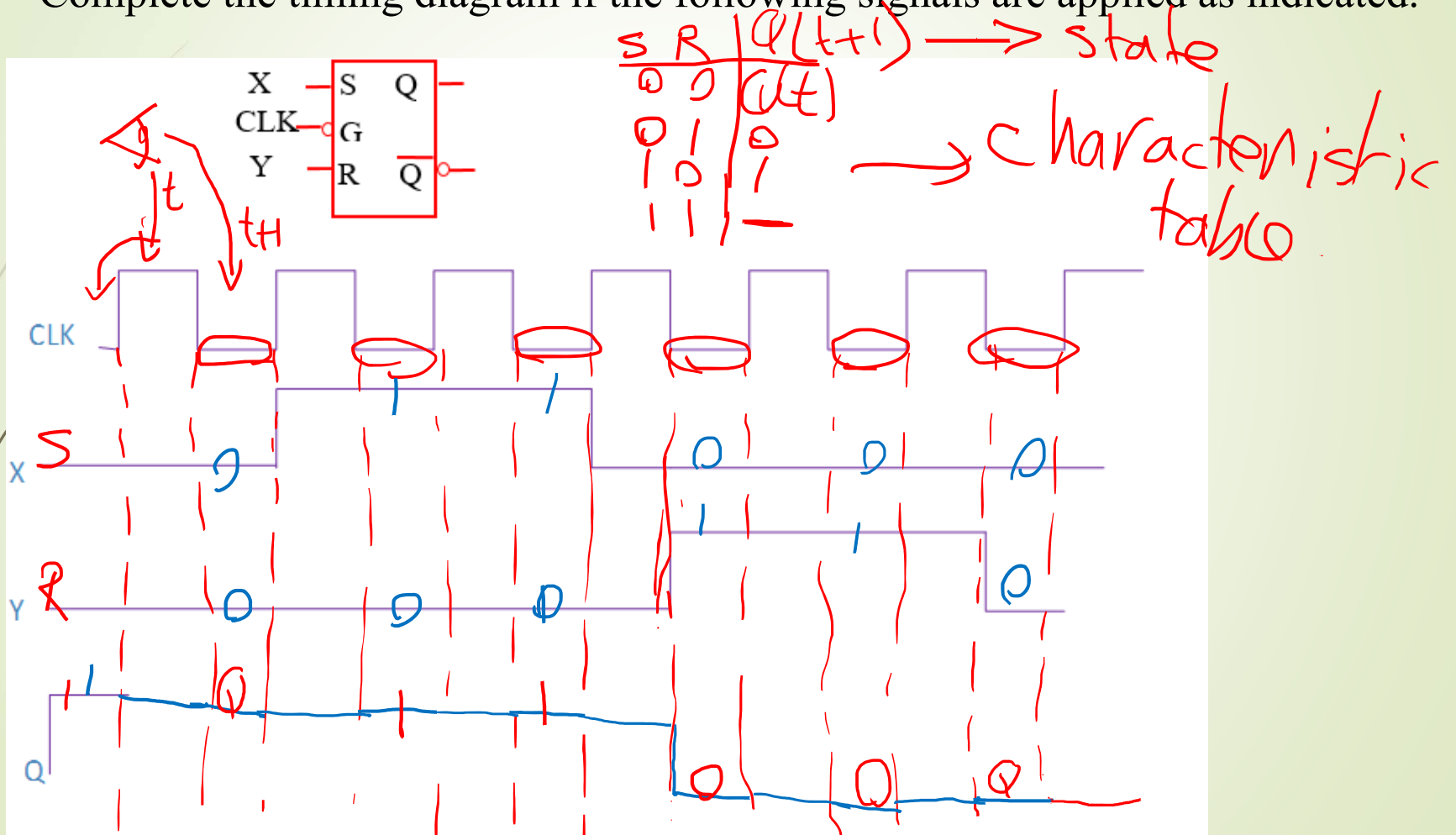

Problem 4

Complete the timing diagram if the following signals are applied as indicated.

