

EGC220 Class Notes 5/9/2023



Baback Izadi

Division of Engineering Programs


bai@enr.newpaltz.edu

Final:

Closed book and notes


- Number systems
 - Simplification using K-map
 - SOP, POS, Standard SOP and POS, Min. SOP and POS
 - Design of combinational circuits
 - Circuit conversion to all NAND or NOR gates
 - Multiplexers, Demultiplexers, Decoders, Encoders
 - Design of combinational circuits using PLD's
- Latch and flip flops characteristics and excitation tables, design of ripple counters
 - Analysis of sequential circuits
 - Design of sequential circuits
 - Design using Mealy and Moore model
 - Design of a sequence detector
 - Design of a shift register
 - Design of a controller

Decoder

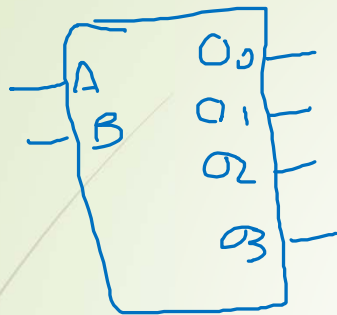

A	B	O_3	O_2	O_1	O_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Priority Encoder

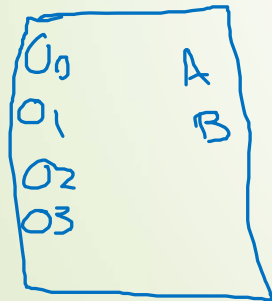

highest				lowest		A	B	V
O_3	O_2	O_1	O_0					
0	0	0	0	x	x	0	0	0
0	0	0	1	0	0	0	0	1
0	0	1	x	0	1	0	1	1
0	1	x	x	1	0	1	0	1
1	x	x	x	1	1	1	1	1

$$A = O_3 + O_2$$

$$B = O_3 + O_1$$

$$\bar{V} = \bar{O}_3 \bar{O}_2 \bar{O}_1 \bar{O}_0$$


$$V = O_3 + O_2 + O_1 + O_0$$

Full Adder


A	B	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$C_{out} = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$$

$$C_{in}(A \oplus B) + AB(C + C)$$

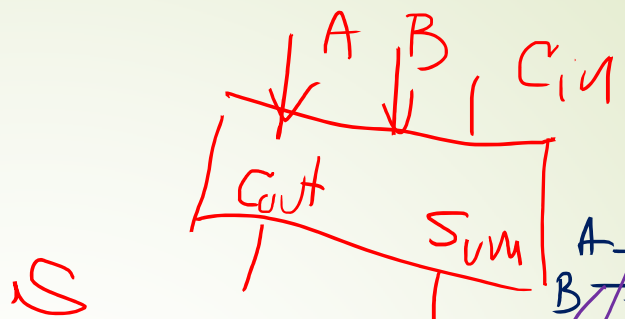

0	1	3	2
14	9	11	6

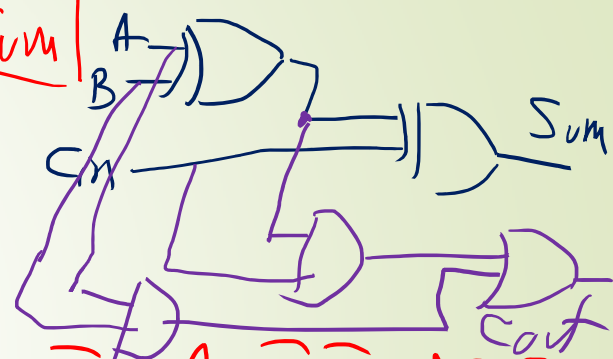

$$S = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$\bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$

$$\bar{A}(B \oplus C) + A(B \oplus C)$$

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + BC + AC$$

		1	
	1	1	1

8 bits

42.5

-42.5

Unsigned	Signed Mag	Signed 2's comp
01010101	01010101	01010101
01010101	11010101	10101010

5

64 32 16 8 4 2 1

0 1 0 1 0 1 0 1

-01010101

10101010

128 64 32 16 8 4 2 1

1 1 0 1 0 0 1 1

what domain

a. unsigned → 211

b. Signed Mag.

64 32 16 8 4 2 1

1 1 0 1 0 0 1 1

neg. -23

c. Signed 2's comp

1 0 1 0 1 0 1 0





-01010101

-45

E A

$\overbrace{x \ y \ z}^E \quad k_7 \ k_6 \ k_5 \ k_4 \ k_3 \ k_2 \ k_1 \ k_0$



0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

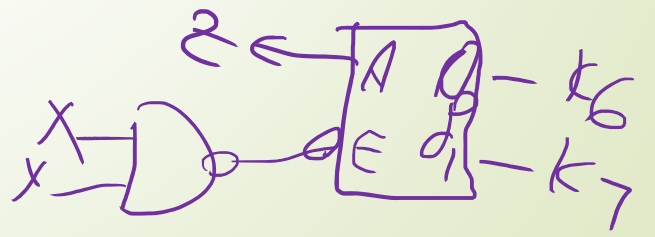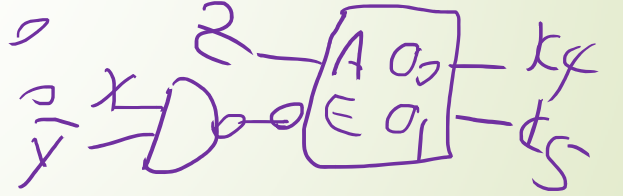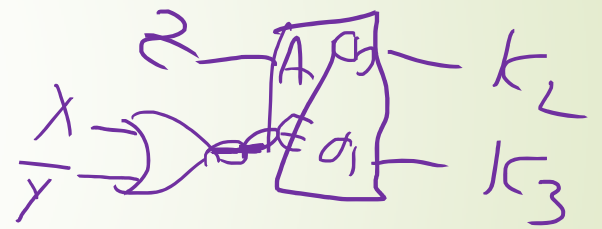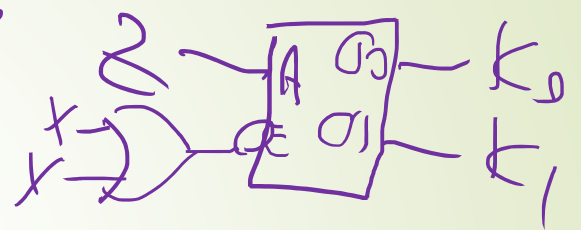


E	A	0	0
0	0	0	1
1	0	0	0

Make 8x1 out of 4x1

4x1 MUX

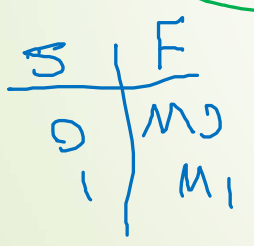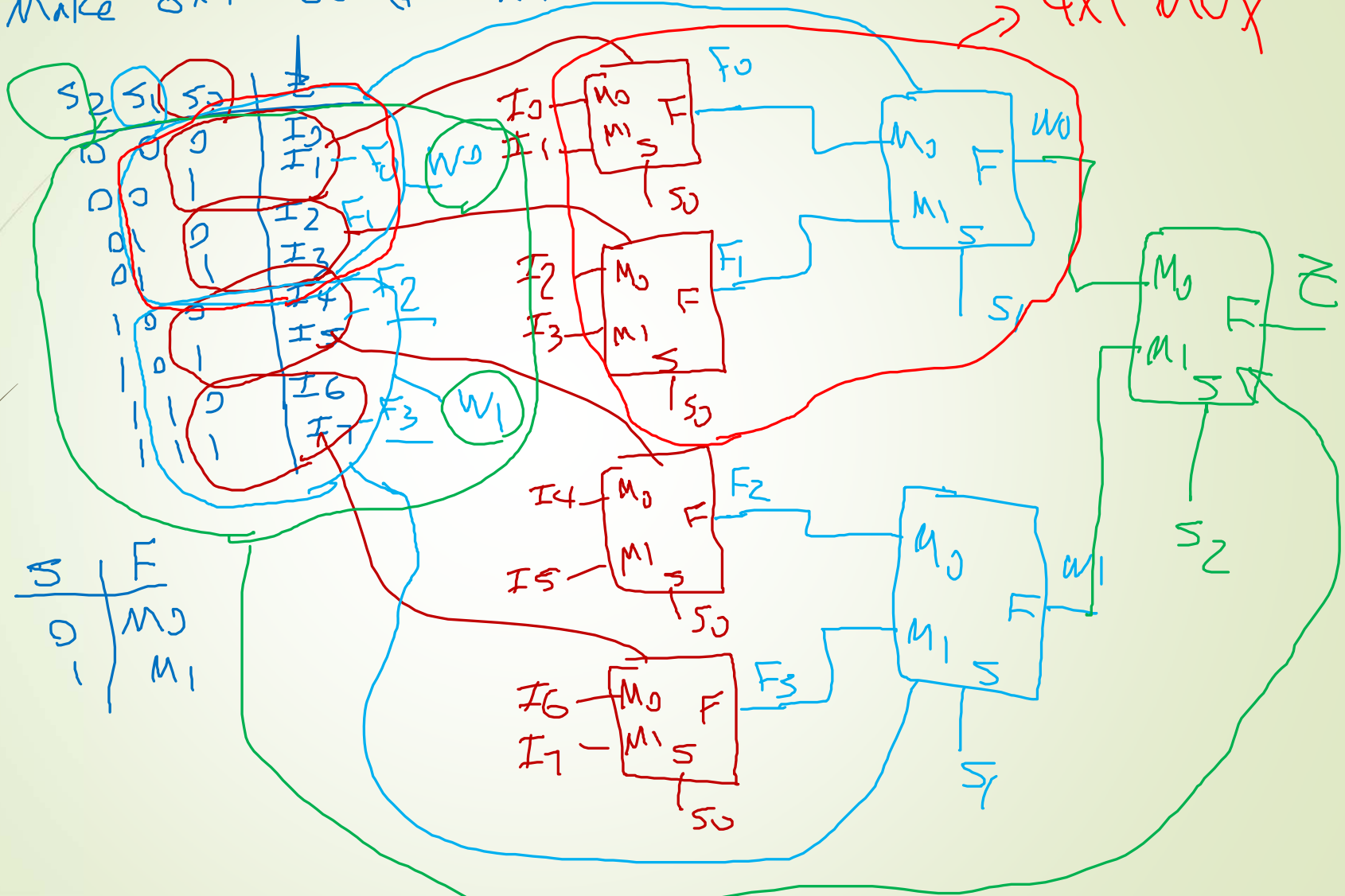

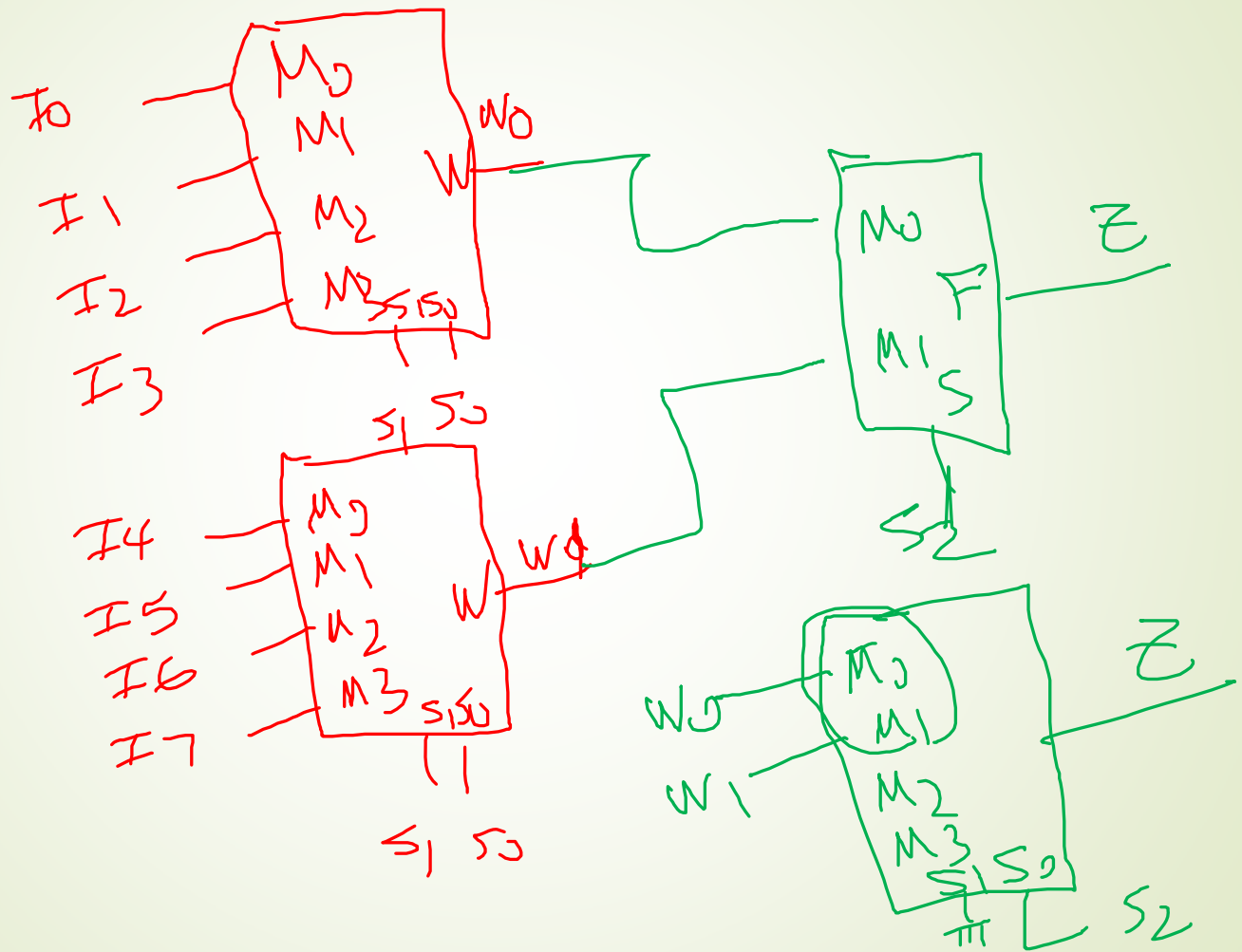


8x1 MUX



$$F = \sum m(4, 6, 9, 13, 15)$$





S_2	S_1	S_0	Z
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

8x1 MUX

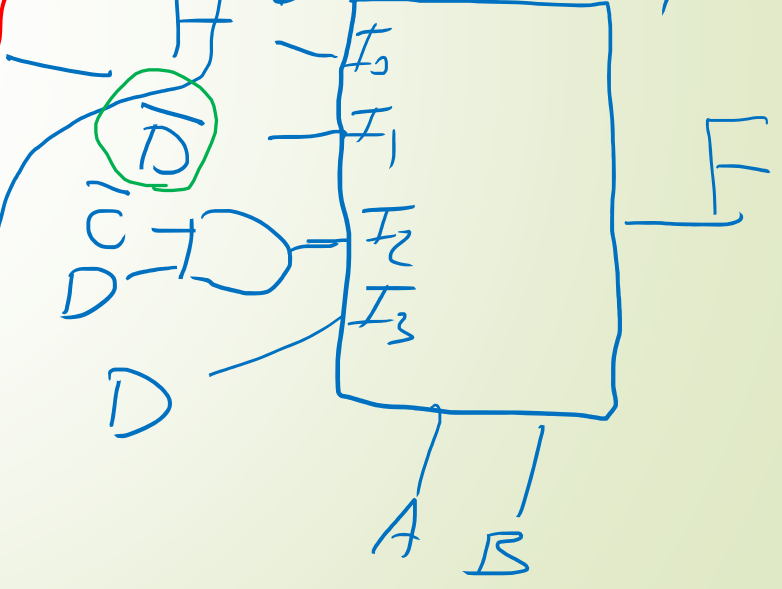

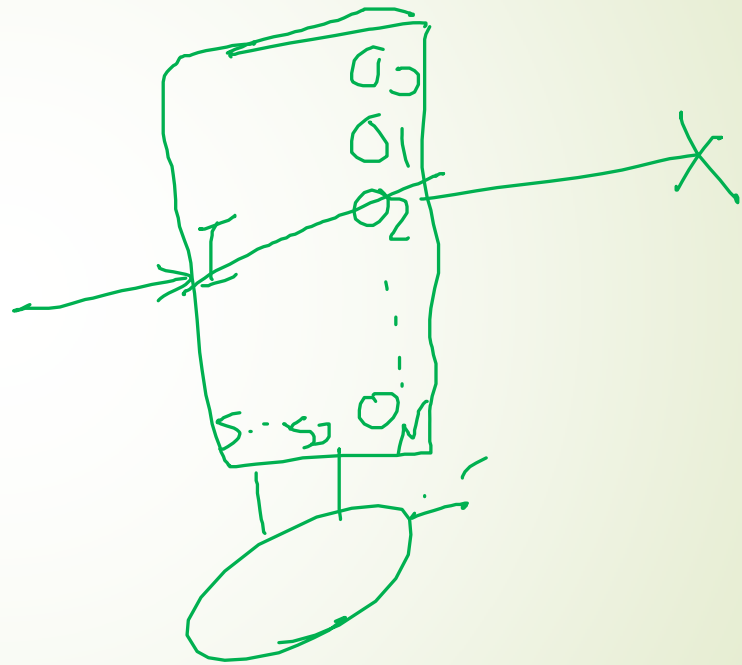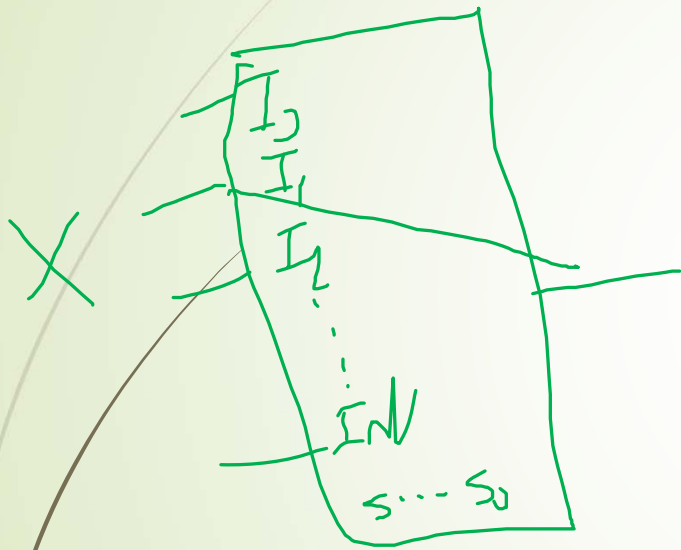

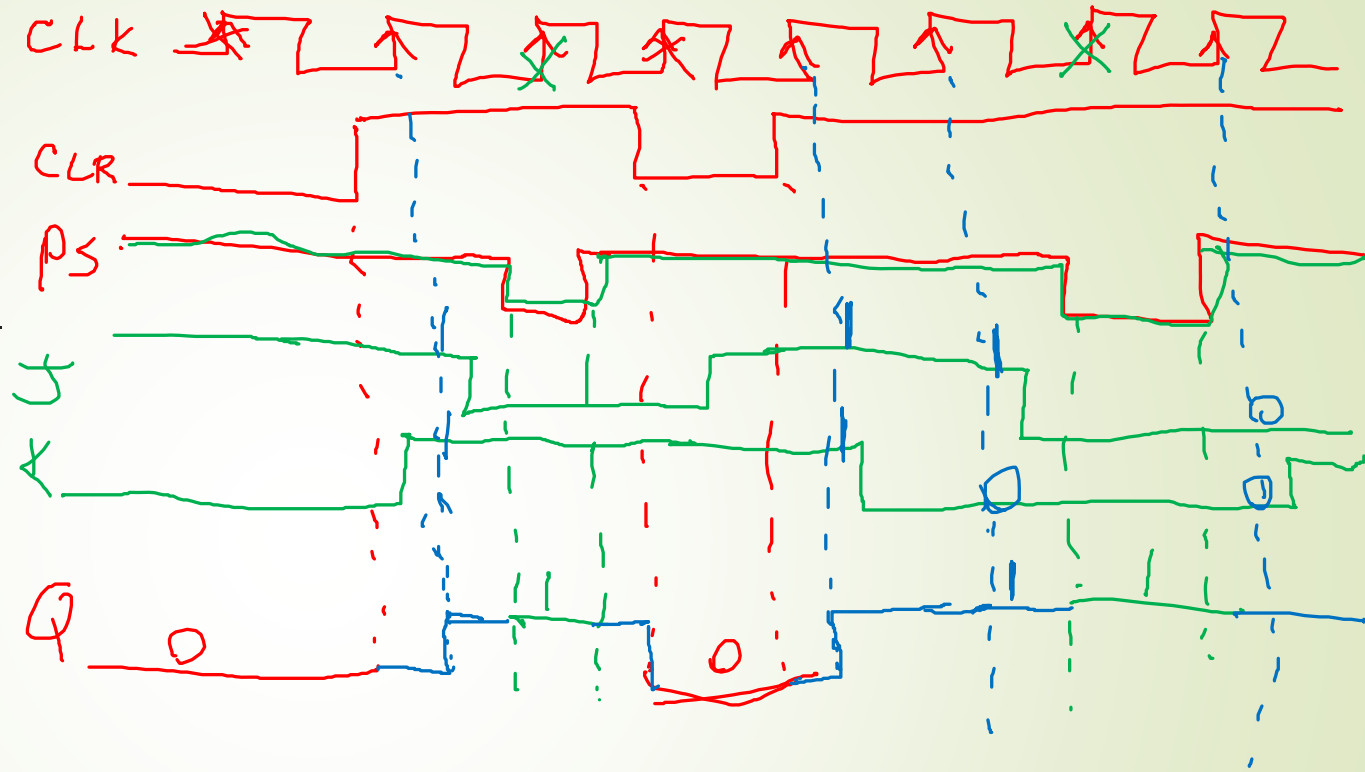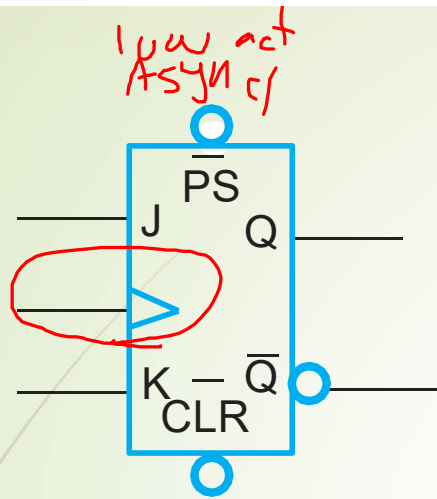

low
act.
ASYN

sequence

overlapping

Module


z

110|10|

10

11010

11100

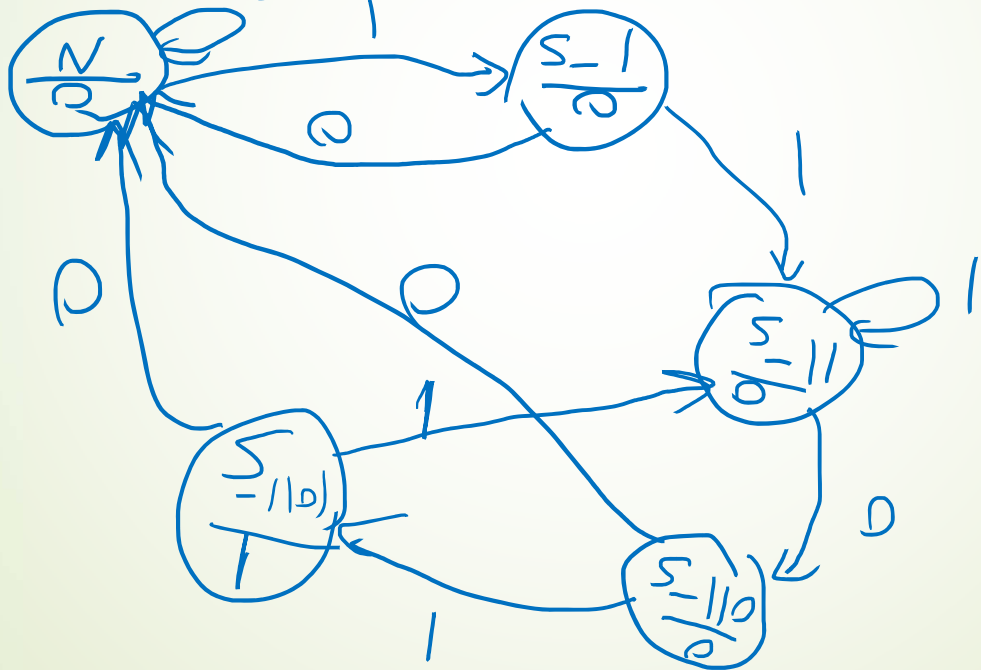

N = nothing
 S-1 : 1 detected
 S-11 : 11
 S-110 : 110
 S-110/1 : 1101

000
100
110
111
011
001

Problem 9

Using D flip flops, design a circuit to generate the following sequence.

0101 → 1100 → 0101 → 0011 → 1111 → 0001 →

Your design should be race free.

	0	01	11	1
0	A	B	C	
1	F	E	D	

ps NS

Q_A Q_B Q_C	D_A D_B D_C	Z_3 Z_2 Z_1 Z_0
0 0 0	0 0 /	0 1 0 /
0 0 1	0 1 /	1 1 0 0
0 1 0	X X X	X X X X
0 1 1	1 1 /	0 1 0 /
1 0 0	0 0 0	0 0 0 /
1 0 1	1 0 0	1 1 1 /
1 1 0	X X X	X X X X
1 1 1	1 0 1	0 0 1 /

$D_A = Q_B Q_C$
 $D_B = \overline{Q_A} Q_C$
 $D_C = \overline{Q_A} + Q_B$

$Z_3 = \overline{Q_C} + Q_C + \overline{Q_C}$
 $Z_2 = \overline{Q_A} + \overline{Q_B} + Q_C$
 $Z_1 = Q_A Q_C$
 $Z_0 = \overline{Q_A} + Q_B + \overline{Q_C}$

$D_A = Q_B + Q_A Q_C$

$$84 - 96 = -12$$

$$\begin{array}{r} 84 \\ 96 \\ -96 \\ \hline \end{array}$$

S	64	32	16	8	4	2	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	0	0
1	0	1	0	0	0	0	0

$$\begin{array}{r} 010100 \\ + 10100000 \\ \hline \end{array}$$

NEG.

$$\textcircled{1}1110100 \xrightarrow{2's}$$

$$\begin{array}{r} 8421 \\ -00001100 \\ \hline -12 \end{array}$$

unsigned subtraction

9.5
4.25

← 1001.10
- 0100.01

$$\begin{array}{r} 111 \\ 1001.10 \\ + 1011.11 \\ \hline 0101.01 \end{array}$$

$$\begin{array}{r} (23.5)_6 \\ * (34.3)_6 \\ \hline 1153 \\ 1432 \\ 1153 \\ \hline (1352.13)_6 \end{array}$$

$15 \div 6 = 2 \quad R=3$
 $11 \div 6 = 1 \quad R=5$
 $7 \div 6 = 1 \quad R=1$
 $20 \div 6 = 3 \quad R=2$
 $15 \div 6 = 2 \quad R=3$
 $10 \div 6 = 1 \quad R=4$
 $8 \div 6 = 1 \quad R=2$

EX=1