

EGC220 Practice Problems for Exam 3


1. Sequential Logic: Latches and Flip-flops

- (a) Draw a gate-level diagram of a D latch with low active gate input. Show and label all inputs and outputs.

(b). Draw a block diagram of the following devices and label all synchronous and asynchronous inputs. Moreover, write an appropriate characteristic table for each device.

 - i. D flip-flop
- ii. T flip-flop
- iii. JK flip-flop
- iv. SR flip-flop

(c). On the following graph, inputs CLK and D are shown. They are inputs to both a D latch and a D flip-flop. CLK goes into the Gate or Clock input. Write the output of the D latch as Q_{DL} on the graph. Then write the output of the D flip-flop as Q_{DFF} on the graph. Both outputs are initially 0 at the start of the graph, as shown.




2. Counters

(a). Design a ripple counter using J-K flip-flops, which counts 11 - 6.

(b). Design a ripple counter using D flip-flops, which counts 6 - 3.

 
(c). For the ripple counter in part b, show the output Q_0 , Q_1 and Q_2 in the grid below. Assume Q_0 to be the least significant bit and the initial count be 6.



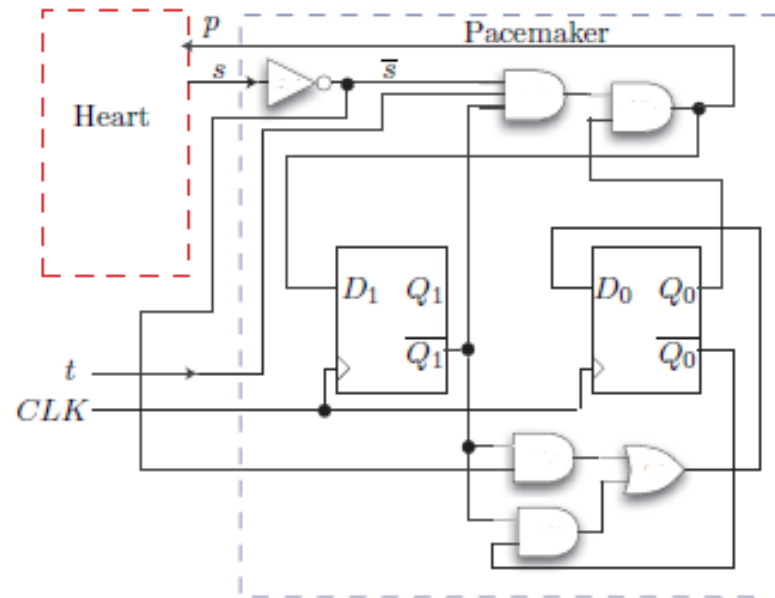3. Analysis of FSM Circuit Design

Below is a simplified block diagram of a heart pacemaker. The output p from the pacemaker pulses high if the heart does not contract within a certain time. The input s indicates whether the heart has contracted ($s = 1$) or not ($s = 0$). The input t comes from a timer, which counts for the expected time between contractions (approximately 1 second). When $t = 1$, the timer has counted up to 1 second, and the heart should have contracted. If the heart has not contracted within that time, the pacemaker sends a pulse $p = 1$. (There is also a timer reset control coming from the pacemaker, which we ignore for this problem.)

The inputs to the pacemaker circuit are s (from the heart) and t (from a timer - not shown). The output of the pacemaker circuit is p , which goes to the heart. Arrows indicate the inputs and output.



- Analyze the circuit leading to a state diagram.
- Is this a Mealy or a Moore machine? Why?