

## Problem 1

Design an  $8 \times 3$  priority encoder with inputs  $D_0 - D_7$ , and output X, Y, Z, V (valid).

## Problem 2

Design an  $8 \times 1$  Mux.

## Problem 3

Implement an  $8 \times 1$  Mux using  $2 \times 1$  Mux's.

## Problem 3

Implement an  $16 \times 1$  Mux using  $4 \times 1$  Mux's.

## Problem 4

Implement the following Boolean expression using an  $8 \times 1$  Mux.

$$F(A, B, C, D) = \sum m(4, 6, 7, 8, 12, 15)$$

## Problem 5

Repeat Problem 4 using a  $4 \times 1$  Mux and external gates.