 



Problem 1


On the following graph, inputs CLK and D are shown. They are inputs to both a D latch and a D flip-flop. CLK goes into the active high G input of the D latch and positive edge clock input of the D flip-flop. Show the output of the D latch as Q_{DL} on the graph and the output of the D flip-flop as Q_{DFF} on the graph. Both outputs are initially 0 at the start of the graph, as shown. Do the two outputs differ, and if so, why?



Problem 2

Complete the following timing diagram for a JK flip-flop with a low active preset (\overline{PS}) and clear (\overline{CLR}).

 

 

Problem 3

Using T flip-flops, design a ripple counter that counts 0 – 7 and repeats.

Problem 4

Show the waveform diagram for the counter in Problem 3.