

**Problem 1**

Using D flip-flops, design a counter with the following repeated binary sequence 1, 3, 5, 7. Assign the sequence as state values.

**Problem 2**

Using D flip-flops, design a counter with the following repeated binary sequence 1, 3, 5, 7. Assign the sequence as output values.

**Problem 3**

Using D flip-flops, design a counter with the following repeated binary sequence 1, 3, 5, 7 when input  $X = 1$  and the reverse sequence when  $X = 0$ . Assign the sequence as state values.