

First Name: _____ Last Name: _____

1. Find the complement of $F = XY + Z'$. Then show that $FF' = 0$ and $F + F' = 1$
2. For function $F = XY + XY' + Y'Z$
 - a. Truth table
 - b. Sum of min terms
 - c. Product of max terms
 - d. Standard sum of products
 - e. Standard product of sums
 - f. Minimum sum of products
 - g. Minimum products of sums
 - h. Gate implementation using all NAND gates
 - i. Gate implementation using all NOR gates.
3.
 - a. Using AND and OR gates, draw the logic diagrams for the following Boolean expressions without expanding or simplifying them.
 - i. $Y = (A' + B')C + B(A + C)$
 - ii. $(A + B')(C + D')$
 - b. Convert the above circuits to all NAND and all NOR gates without expanding or simplifying the functions.
4. For the following Boolean expression $F = X'Y' + Y'Z + XZ + XY + YZ'$, determine
 - a. Truth table
 - b. Sum of min terms
 - c. Product of max terms
 - d. Standard sum of products
 - e. Standard product of sums
 - f. Minimum sum of products
 - g. Minimum products of sums
 - h. Gate implementation using all NAND gates
 - i. Gate implementation using all NOR gates.