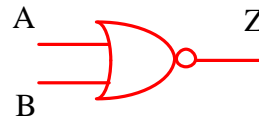






**NOR gate property:**

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0








**Cross coupled NOR gates:**

S	R	Q	M
0	0		
0	1		
1	0		
1	1		

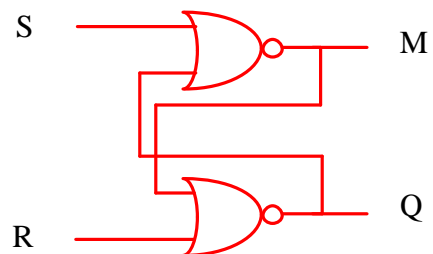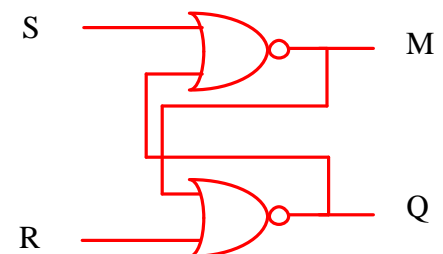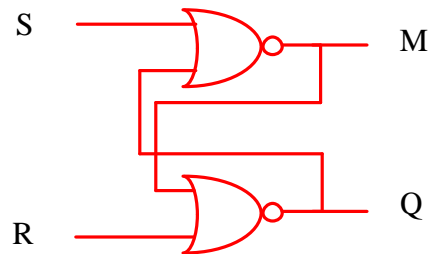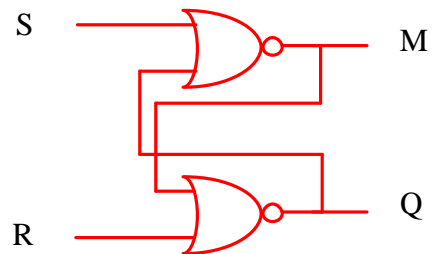



S	R	Q
0	0	
0	1	
1	0	
1	1	

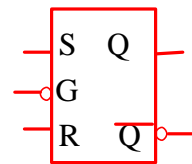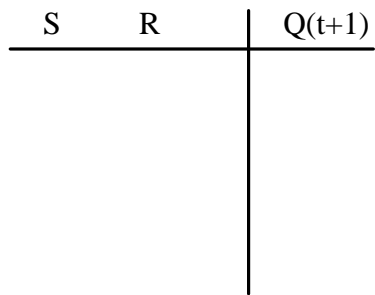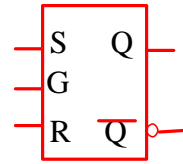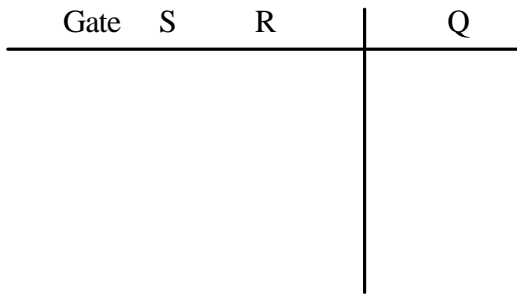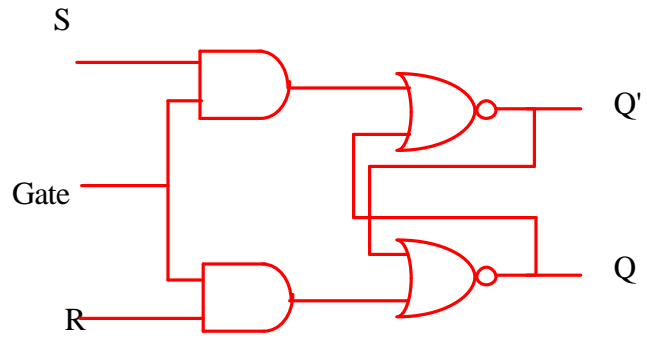A circuit diagram of a cross-coupled NOR gate latch. It has two input lines labeled 'S' and 'R' on the left. The output line is labeled 'Q' on the right. The top NOR gate has inputs 'S' and 'Q', and output 'Q'. The bottom NOR gate has inputs 'R' and 'Q', and output 'Q'.







**Flip flops:**



1. S-R flip-flop

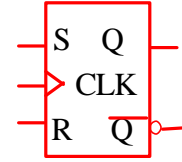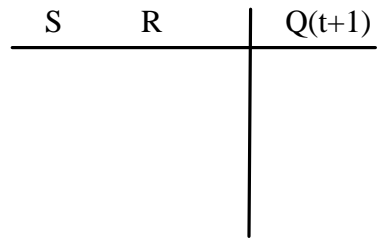

2. D flip-flop

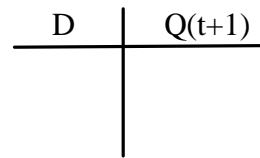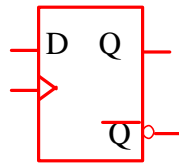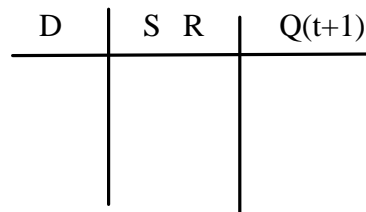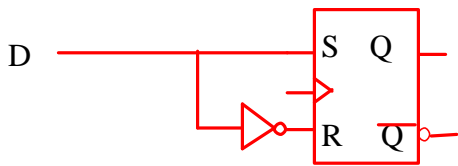

3. J K flip-flop

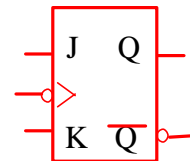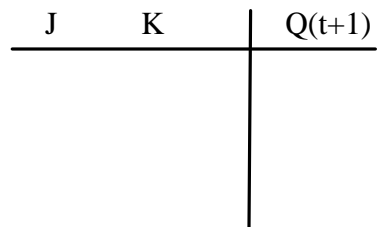

4. T flip-flop



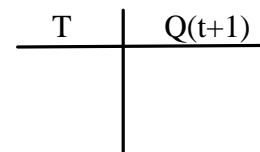
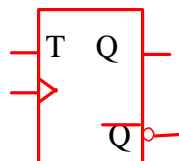
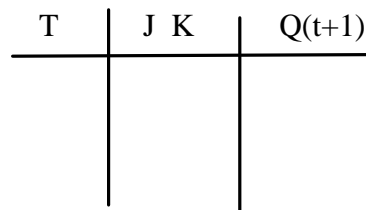


Figure 4-3 Synchronous Clocked Sequential Circuit

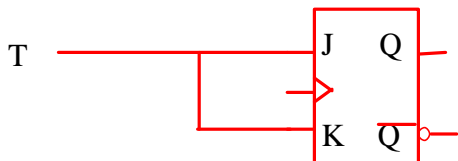

(a) Block diagram

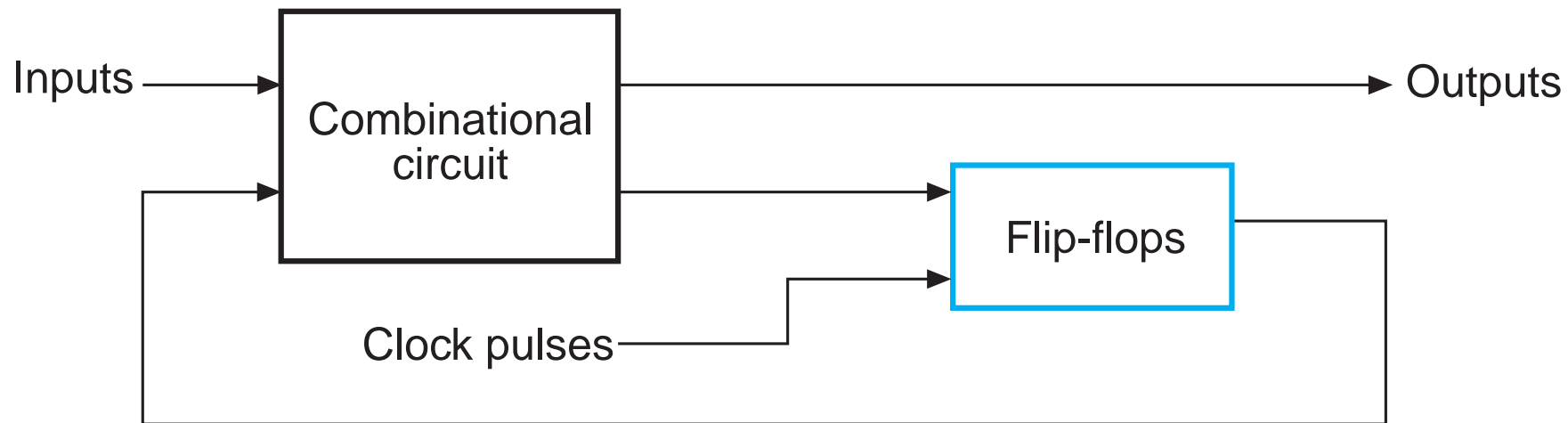

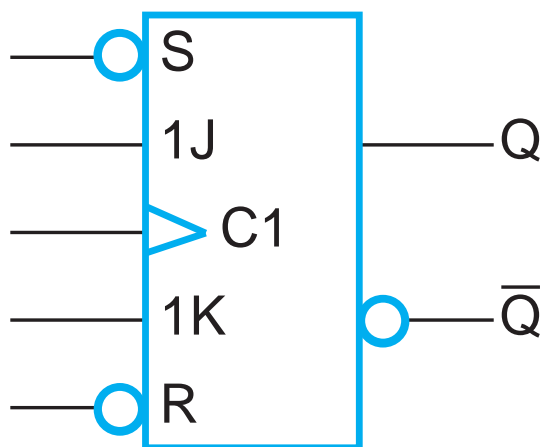
(b) Timing diagram of clock pulses

Table 4-1 Flip-Flop Characteristic Table

<b>(a) JK Flip-Flop</b>				<b>(b) SR Flip-Flop</b>			
<b>J</b>	<b>K</b>	<b><math>Q(t+1)</math></b>	<b>Operation</b>	<b>S</b>	<b>R</b>	<b><math>Q(t+1)</math></b>	<b>Operation</b>
0	0	$Q(t)$	No change	0	0	$Q(t)$	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	$\overline{Q}(t)$	Complement	1	1	?	Undefined

<b>(c) D Flip-Flop</b>			<b>(d) T Flip-Flop</b>		
<b>D</b>	<b><math>Q(t+1)</math></b>	<b>Operation</b>	<b>T</b>	<b><math>Q(t+1)</math></b>	<b>Operation</b>
0	0	Reset	0	$Q(t)$	No change
1	1	Set	1	$\overline{Q}(t)$	Complement

Figure 4-16 *JK* Flip-Flop with Direct Set and Reset


(a) Graphic symbols

S	R	C	J	K	Q	$\bar{Q}$
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	Undefined	
1	1	↑	0	0	No change	
1	1	↑	0	1	0	1
1	1	↑	1	0	1	0
1	1	↑	1	1	Complement	

(b) Function table

**Analysis Procedure:**

1. Obtain flip-flop input equations
2. Write down characteristic table of each type of flip-flop in use
3. Develop state table
4. Obtain state diagram

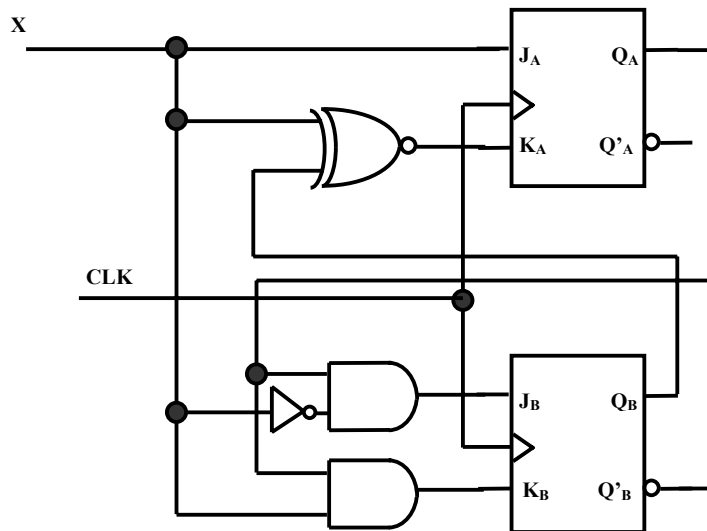□ **Example #1:****Step 1: Flip-flop input equations and output equation**

$$J_A = X$$

$$K_A = Q_B \oplus X = Q_B \odot X$$

$$J_B = Q_A X'$$


$$K_B = Q_A X$$

**Step 2: Characteristic Table**

J K	Q(t+1)
0 0	Q(t)
0 1	0
1 0	1
1 1	Q'(t)


**Step 3: State Table**

PS Q <sub>A</sub> Q <sub>B</sub> X	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	NS Q <sub>A</sub> Q <sub>B</sub>
000	0	1	0	0	00
001	1	0	0	0	10
010	0	0	0	0	01
011	1	1	0	0	11
100	0	1	1	0	01
101	1	0	0	1	10
110	0	0	1	0	11
111	1	1	0	1	00

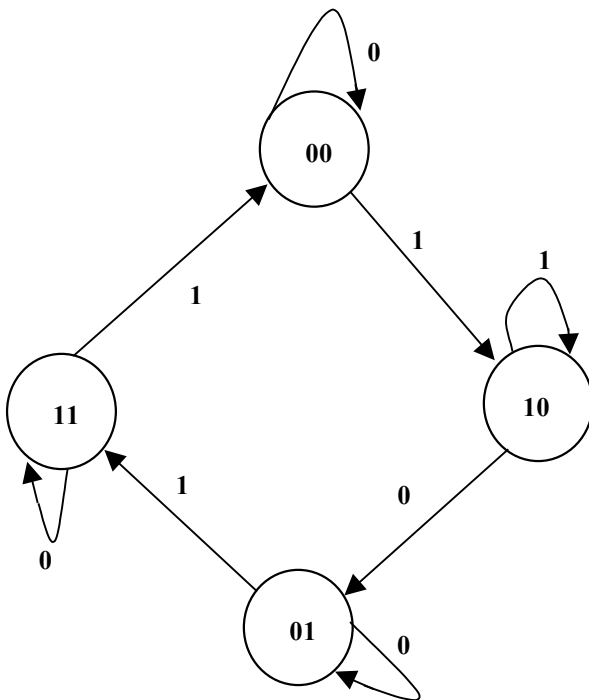**Step 4: State Diagram**



□ **Example #2:**

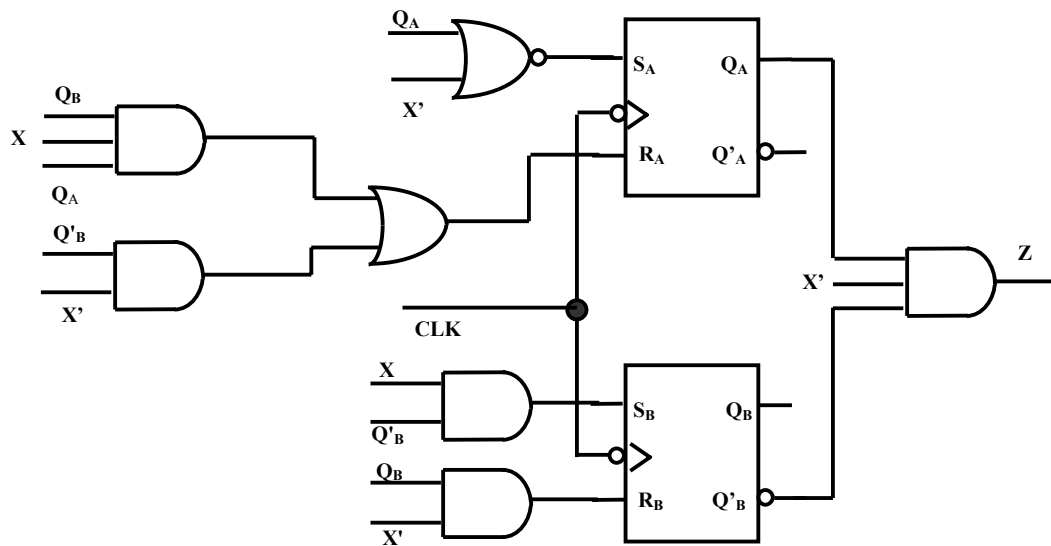

**Step 1: Flip-flop input equations and output equation**

$$S_A = (Q_A + X)' = Q'_A X$$

$$R_A = Q_A Q_B X + Q'_B X'$$

$$S_B = Q'_B X$$

$$R_B = Q_B X'$$

$$Z = Q_A Q'_B X'$$

**Step 2: Characteristic Table**

S	R	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	-

**Step 3: State Table**

PS Q <sub>A</sub> Q <sub>B</sub> X	S <sub>A</sub>	R <sub>A</sub>	S <sub>B</sub>	R <sub>B</sub>	NS Q <sub>A</sub> Q <sub>B</sub>	Z
000	0	1	0	0	00	0
001	1	0	1	0	11	0
010	0	0	0	1	00	0
011	1	0	0	0	11	0
100	0	1	0	0	00	1
101	0	0	1	0	11	0
110	0	0	0	1	10	0
111	0	1	0	0	01	0

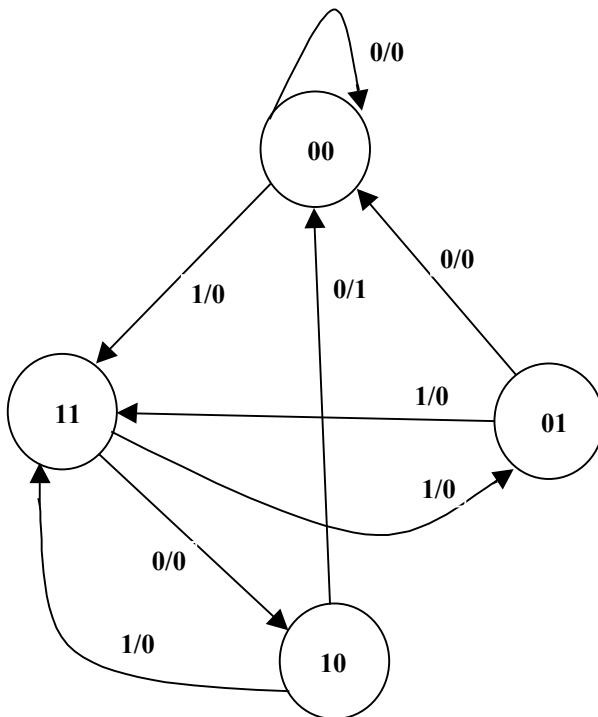
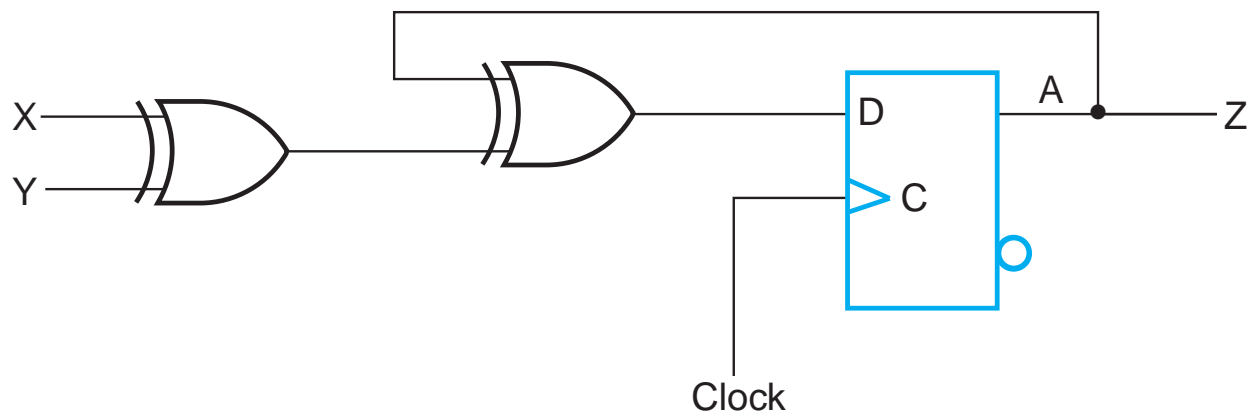
**Step 4: State Diagram**


Figure 4-19 Logic Diagram and State Table for  $D_A = A \oplus X \oplus Y$ 

(a)

Present state	Inputs		Next state	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

(b) State table

□ **Example #3:**

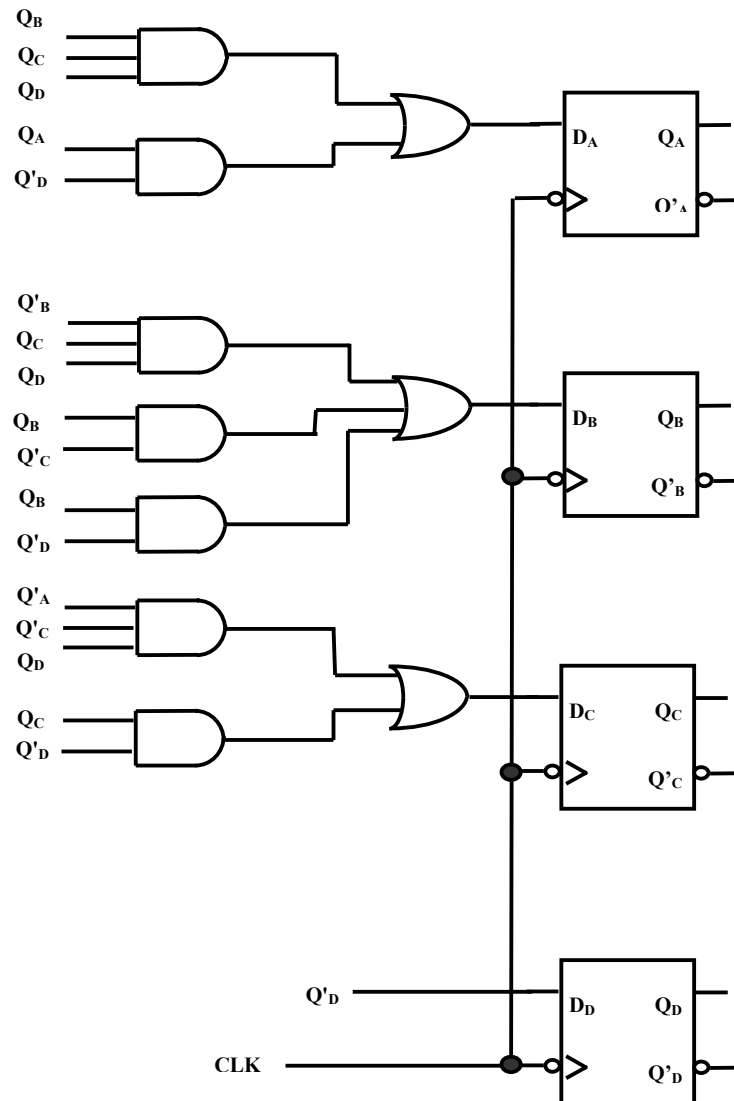

**Step 1: Flip-flop input equations**

$$D_A = Q_B Q_C Q_D + Q_A Q_D'$$

$$D_B = Q_B' Q_C Q_D + Q_B Q_C' + Q_B Q_D'$$

$$D_C = Q_A' Q_C' Q_D + Q_C Q_D'$$

$$D_D = Q_D'$$

**Step 2: Characteristic Table**

<b>D</b>	<b>Q(t+1)</b>
<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>

**Step 3: State Table**

<b>PS</b> <b>Q<sub>A</sub>Q<sub>B</sub>Q<sub>C</sub>Q<sub>D</sub></b>	<b>D<sub>A</sub></b>	<b>D<sub>B</sub></b>	<b>D<sub>C</sub></b>	<b>D<sub>D</sub></b>	<b>NS</b> <b>Q<sub>A</sub>Q<sub>B</sub>Q<sub>C</sub>Q<sub>D</sub></b>
<b>0 0 0 0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0 0 0 1</b>
<b>0 0 0 1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0 0 1 0</b>
<b>0 0 1 0</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0 0 1 1</b>
<b>0 0 1 1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0 1 0 0</b>
<b>0 1 0 0</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>0 1 0 1</b>
<b>0 1 0 1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>0 1 1 0</b>
<b>0 1 1 0</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>0 1 1 1</b>
<b>0 1 1 1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1 0 0 0</b>
<b>1 0 0 0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1 0 0 1</b>
<b>1 0 0 1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0 0 0 0</b>
<b>1 0 1 0</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1 0 1 1</b>
<b>1 0 1 1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0 1 0 0</b>
<b>1 1 0 0</b>	<b>1</b>	<b>1</b>	<b>0</b>	<b>1</b>	<b>1 1 0 1</b>
<b>1 1 0 1</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0 1 0 0</b>
<b>1 1 1 0</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	<b>1 1 1 1</b>
<b>1 1 1 1</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1 0 0 0</b>

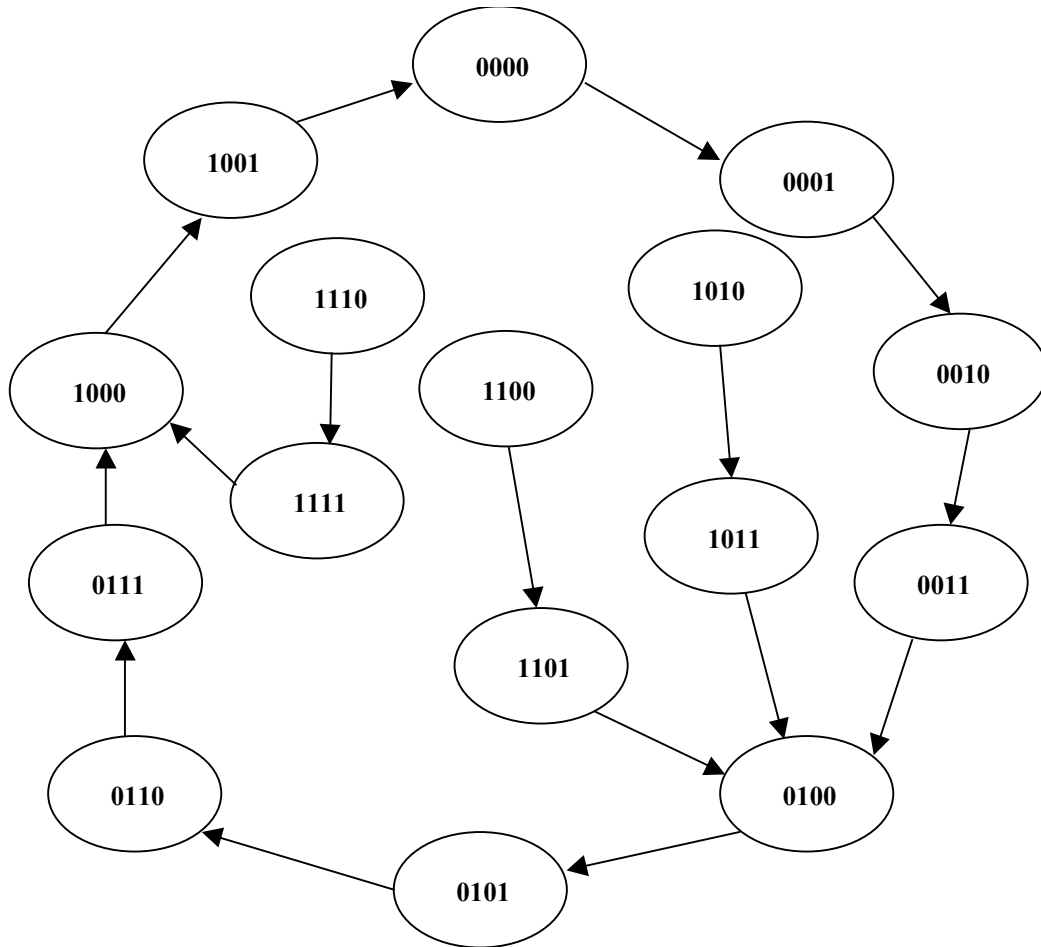
**Step 4: State Diagram**

Table 4-10 Flip-Flop Excitation Table

(a) <i>JK</i> Flip-Flop				(b) <i>SR</i> Flip-Flop			
$Q(t)$	$Q(t+1)$	J	K	$Q(t)$	$Q(t+1)$	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0


(c) <i>D</i> Flip-Flop			(d) <i>T</i> Flip-Flop		
$Q(t)$	$Q(t+1)$	D	$Q(t)$	$Q(t+1)$	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

□ **DESIGN PROCEDURE**

1. Word description.
2. State diagram.
3. Assign binary values.
4. Decide on type of flip flops.
5. Excitation table for the flip flop.
6. State table.
7. Generate simplified logic equations for flip flop inputs and system outputs.
8. Draw logic diagram.

- **Example #1: Using D flip-flops, design a 0 to 9 synchronous counter.**

**State diagram**

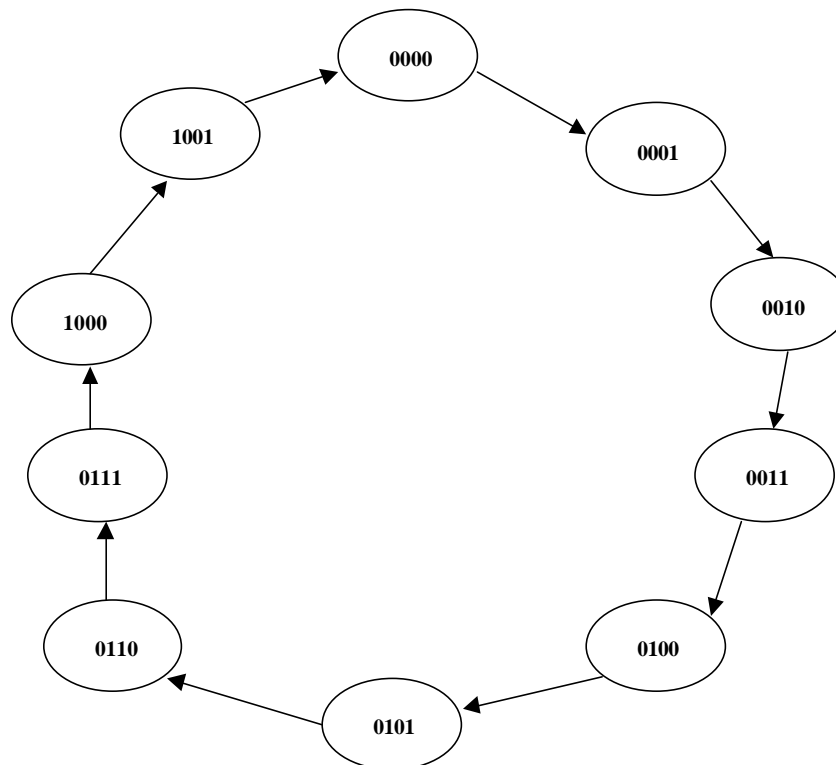




- **D Flip-Flop Excitation Table**

<b>Q(t)</b>	<b>Q(t+1)</b>	<b>D</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>


- **State Table**

<b>PRESENT STATE</b>	<b>NEXT STATE</b>				
<b>Q<sub>A</sub>Q<sub>B</sub>Q<sub>C</sub>Q<sub>D</sub></b>	<b>Q<sub>A</sub>Q<sub>B</sub>Q<sub>C</sub>Q<sub>D</sub></b>	<b>D<sub>A</sub></b>	<b>D<sub>B</sub></b>	<b>D<sub>C</sub></b>	<b>D<sub>D</sub></b>
<b>0000</b>	<b>0001</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>0001</b>	<b>0010</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>0</b>
<b>0010</b>	<b>0011</b>	<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>
<b>0011</b>	<b>0100</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>0100</b>	<b>0101</b>	<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>
<b>0101</b>	<b>0110</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>
<b>0110</b>	<b>0111</b>	<b>0</b>	<b>1</b>	<b>1</b>	<b>1</b>
<b>0111</b>	<b>1000</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1000</b>	<b>1001</b>	<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>
<b>1001</b>	<b>0000</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1010</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1011</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1100</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1101</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1110</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>
<b>1111</b>	<b>XXXX</b>	<b>X</b>	<b>X</b>	<b>X</b>	<b>X</b>

• **Karnaugh Map**

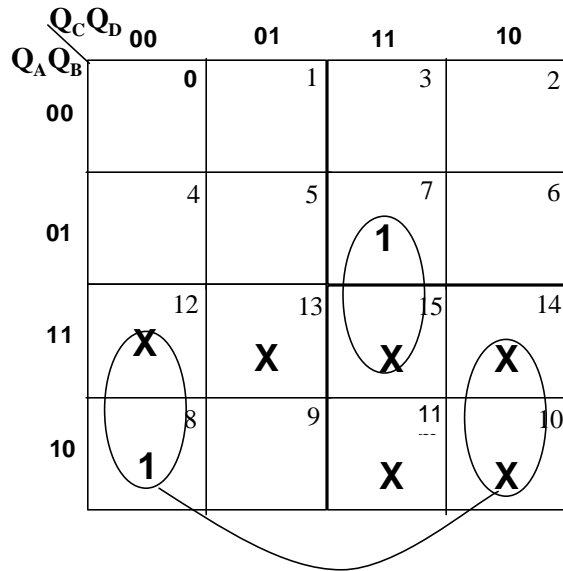

•  $D_A = Q_B Q_C Q_D + Q_A Q_D'$

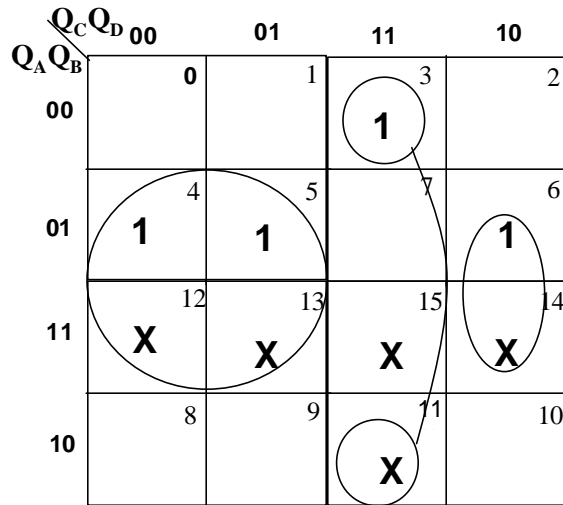

•  $D_B = Q_B' Q_C Q_D + Q_B Q_C' + Q_B Q_D'$

$Q_A Q_B$		$Q_C Q_D$			
		00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

		1		1
		1		1
X	X	X	X	X
			X	X

·  $D_C = Q_A' Q_C' Q_D + Q_C Q_D'$


$Q_A Q_B$		$Q_C Q_D$			
		00	01	11	10
00	0	1	3	2	
01	4	5	7	6	
11	12	13	15	14	
10	8	9	11	10	

1			1
1			1
X	X	X	X
1		X	X


·  $D_D = Q_D'$

- **Circuit**

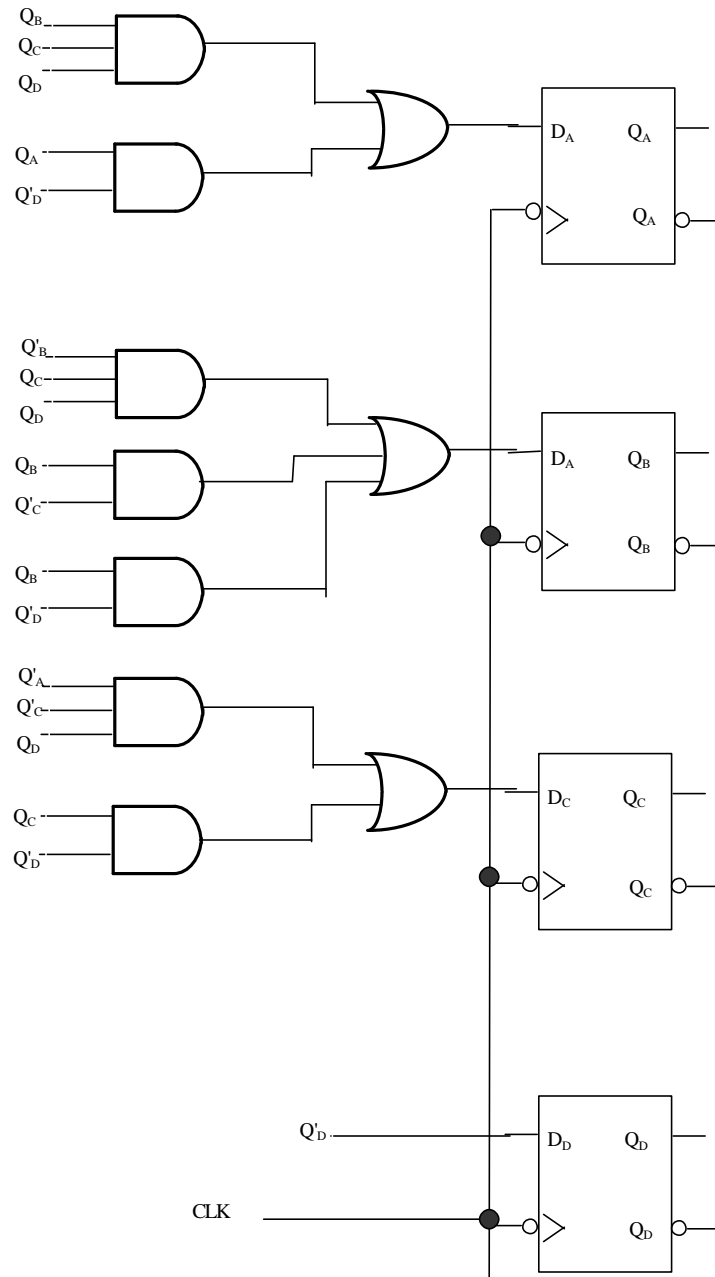

□ Example #2:

1. State diagram

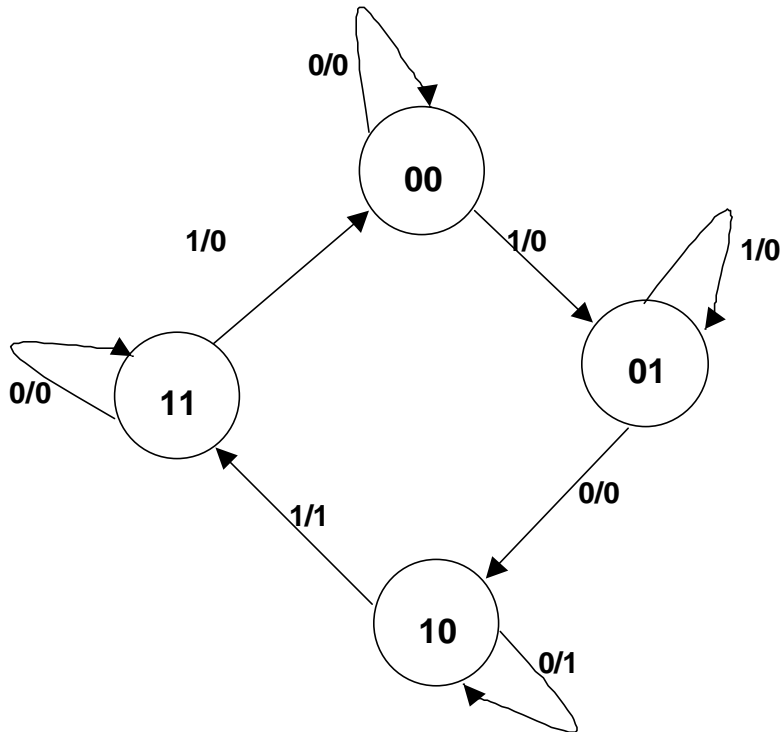

2. Use JK flip flops

3. Flip flop Excitation Table

PRESENT STATE	NEXT STATE	J	K
Q(t)	Q(t+1)		
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

#### 4. State Table

PRESENT STATE	INPUT	NEXT STATE	FLIP-FLOP INPUTS				OUTPUT
			$Q_A Q_B$	$J_A$	$K_A$	$J_B$	
00	0	00	0	X	0	X	0
00	1	01	0	X	1	X	0
01	0	10	1	X	X	1	0
01	1	01	0	X	X	0	0
10	0	10	X	0	0	X	1
10	1	11	X	0	1	X	1
11	0	11	X	0	X	0	0
11	1	00	X	1	X	1	0

#### 5. Karnaugh Map

$Q_B \ X$	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$ (1)
1	X	X	X	$m_6$ (X)
$Q_A$	$m_4$	$m_5$	$m_7$	$m_6$

$$J_A = Q_B X'$$

$Q_B \ X$	00	01	11	10
0	X	X	$m_3$ (X)	X
1			$m_7$ (1)	
$Q_A$	$m_4$	$m_5$	$m_7$	$m_6$

$$K_A = Q_B X$$

$Q_B \backslash X$	00	01	11	10
$Q_A \backslash 0$	$m_0$	1 $m_1$	X $m_3$	X $m_2$
$Q_A \backslash 1$	$m_4$	1 $m_5$	X $m_7$	X $m_6$

·  $J_B = X$


$Q_B \backslash X$	00	01	11	10
$Q_A \backslash 0$	X $m_0$	X $m_1$		1 $m_2$
$Q_A \backslash 1$	X $m_4$	X $m_5$	1 $m_7$	

·  $K_B = Q_A X' + Q_A' X = Q_A \oplus X$

$Q_B \backslash X$	00	01	11	10
$Q_A \backslash 0$	$m_0$	$m_1$	$m_3$	$m_2$
$Q_A \backslash 1$	1 $m_4$	1 $m_5$	$m_7$	$m_6$

·  $Z = Q_A Q'_B$


## 6. Schematic

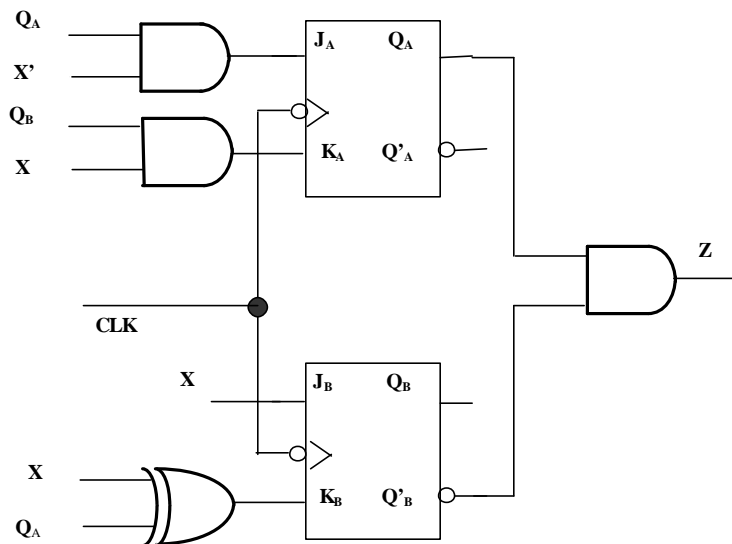

□ **Example #3:**

**Using JK flip-flops, design an up/down synchronous counter as specified below. The counter counts up if input X is 1 and it counts down when X is 0.**

• **State Diagram**

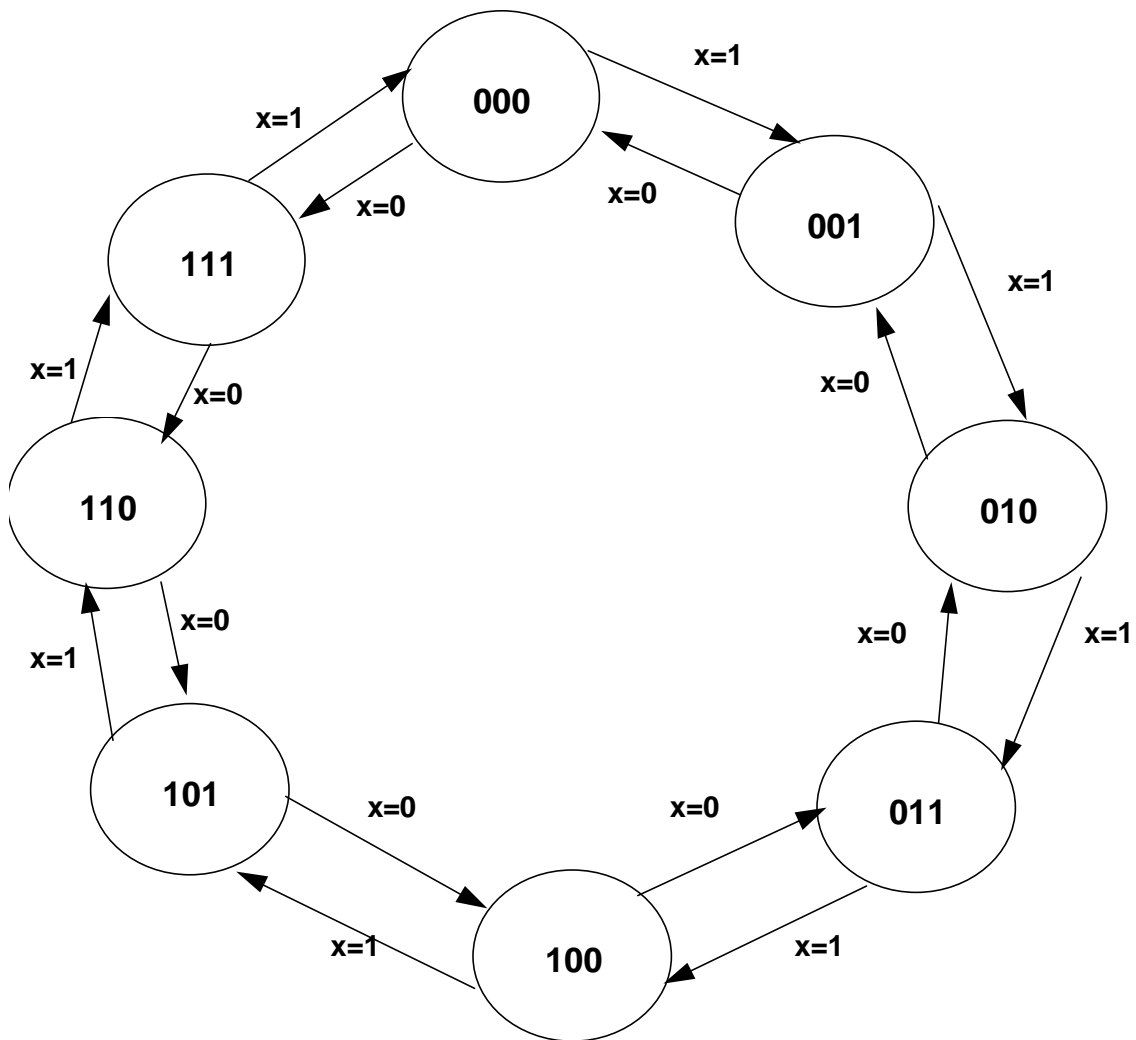

- **Use JK flip flops**



- Flip flop Excitation Table

PRESENT STATE	NEXT STATE		
Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

- State Table

PRESENT STATE	INPUT	NEXT STATE						
Q <sub>A</sub> Q <sub>B</sub> Q <sub>C</sub>	X	Q <sub>A</sub> Q <sub>B</sub> Q <sub>C</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
000	0	111	1	X	1	X	1	X
000	1	001	0	X	0	X	1	X
001	0	000	0	X	0	X	X	1
001	1	010	0	X	1	X	X	1
010	0	001	0	X	X	1	1	X
010	1	011	0	X	X	0	1	X
011	0	010	0	X	X	0	X	1
011	1	100	1	X	X	1	X	1
100	0	011	X	1	1	X	1	X
100	1	101	X	0	0	X	1	X
101	0	100	X	0	0	X	X	1
101	1	110	X	0	1	X	X	1
110	0	101	X	0	X	1	1	X
110	1	111	X	0	X	0	1	X
111	0	110	X	0	X	0	X	1
111	1	000	X	1	X	1	X	1

## Karnaugh Map

$Q_A \backslash Q_B$	$Q_C X$ 00	01	11	10
00	1 $m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	1 $m_7$	$m_6$
11	X $m_{12}$	X $m_{13}$	X $m_{15}$	X $m_{14}$
10	X $m_8$	X $m_9$	X $m_{11}$	X $m_{10}$

$$J_A = Q'_B Q'_C X' + Q_B Q_C X$$

$Q_A \backslash Q_B$	$Q_C X$ 00	01	11	10
00	X $m_0$	X $m_1$	X $m_3$	X $m_2$
01	X $m_4$	X $m_5$	X $m_7$	X $m_6$
11	$m_{12}$	$m_{13}$	1 $m_{15}$	$m_{14}$
10	1 $m_8$	$m_9$	$m_{11}$	$m_{10}$

$$K_A = Q'_B Q'_C X' + Q_B Q_C X$$

$Q_A \backslash Q_B$	$Q_C X$ 00	01	11	10
00	1 $m_7$	$m_1$	1 $m_3$	$m_2$
01	X $m_4$	X $m_5$	X $m_7$	X $m_6$
11	X $m_2$	X $m_{13}$	X $m_5$	X $m_{14}$
10	1 $m_6$	$m_9$	1 $m_{11}$	$m_{10}$

·  $J_B = Q'_C X' + Q_C X = Q_C \odot X$

$Q_A \backslash Q_B$	$Q_C X$ 00	01	11	10
00	X $m_7$	X $m_1$	X $m_3$	X $m_2$
01	1 $m_4$	$m_5$	1 $m_7$	$m_6$
11	1 $m_2$	$m_{13}$	1 $m_5$	$m_{14}$
10	X $m_6$	X $m_9$	X $m_{11}$	X $m_{10}$

·  $K_B = Q'_C X' + Q_C X = Q_C \odot X$

·  $J_C = 1$

·  $K_C = 1$

- Schematic

