

## EGC221: Digital Logic Lab

### Experiment #7 Arithmetic Logic Unit (ALU) Schematic Implementation

Student's Name:	Reg. no.:
Student's Name:	Reg. no.:
Semester: Spring 2017	Date: 04 April 2017

#### Assessment:

Assessment Point	Weight	Grade
Methodology and correctness of results		
Discussion of results		
Participation		
<b>Assessment Points' Grade:</b>		

#### Comments:


**Experiment #7:****Arithmetic Logic Unit****Objectives:**

The objective of this lab is:

1. To design a 4-bit ALU
2. To implement the ALU on an (Altera) FPGA Development Board
3. To verify the operation of the ALU through simulation
4. To experimentally check the operation of the ALU

This lab is different from the other assignments in the sense that it is a design project which gives you more freedom to come up with your own solutions. The following write-up serves as a guideline to help you design the lab. However, if you find more efficient or more elegant ways to implement parts of the ALU, go ahead. Just make sure you justify your design and explain it clearly in the lab report write-up.

**Pre-lab assignment:****a. Problem Statement:**

An Arithmetic and Logic Unit (ALU) is a combinational circuit that performs arithmetic and logic micro-operations on a pair of n-bit operands (e.g., A[3:0] and B[3:0]). The operations performed by an ALU are controlled by a set of function-select inputs. In this lab you will design a 4-bit ALU with 3 function-select inputs: Selects: S0, S1, and Mode: M. The functions performed by the ALU are specified in Table 1.

Logic				
M	S1	S0	FUNCTION	OPERATION (bit wise)
0	0	0	$A \cdot B$	AND
0	0	1	$A + B$	OR
0	1	0	$A \oplus B$	XOR
0	1	1	$A'$	NOT
Arithmetic				
M	S1	S0	FUNCTION	OPERATION
1	0	0	$A + B$	Addition
1	0	1	$A - B$	Subtract
1	1	0	$A + 1$	Increment
1	1	1	$A - 1$	Decrement





This design methodology creates separate 4-bit units for each function. This method would utilize the 4-bit adder/subtractor that you have created in a previous lab, leaving you with some modifications (for increment and decrement) as well as some new designs (for your logic functions.) The 8 functions would then be selected with a 4-bit wide, 8:1 MUX, therefore directing the desired function to the (4-bit) output.

---

**Note: This lab is worth 20 points****Hand-in**

You have to hand in a lab report that contains the following:

1. Course Title, Lab number and title, your name(s) and date (You can use the cover sheet provided with this handout.)
2. Theory of topic (ALU)
3. Section on the Pre-lab explaining the detailed design of each macro and its simulation waveform.
4. Conclusion and overall discussion.

The lab report is an important part of the laboratory. Write it carefully, be clear and well organized. It is the only way to convey that you did a great job in the lab. It is necessary that you use computer tools (MS Word, Visio, Altera, etc.) to document the entire lab report.