

EGC221

Class Notes

3/29/2023

Baback Izadi

Division of Engineering Programs
bai@engr.newpaltz.edu

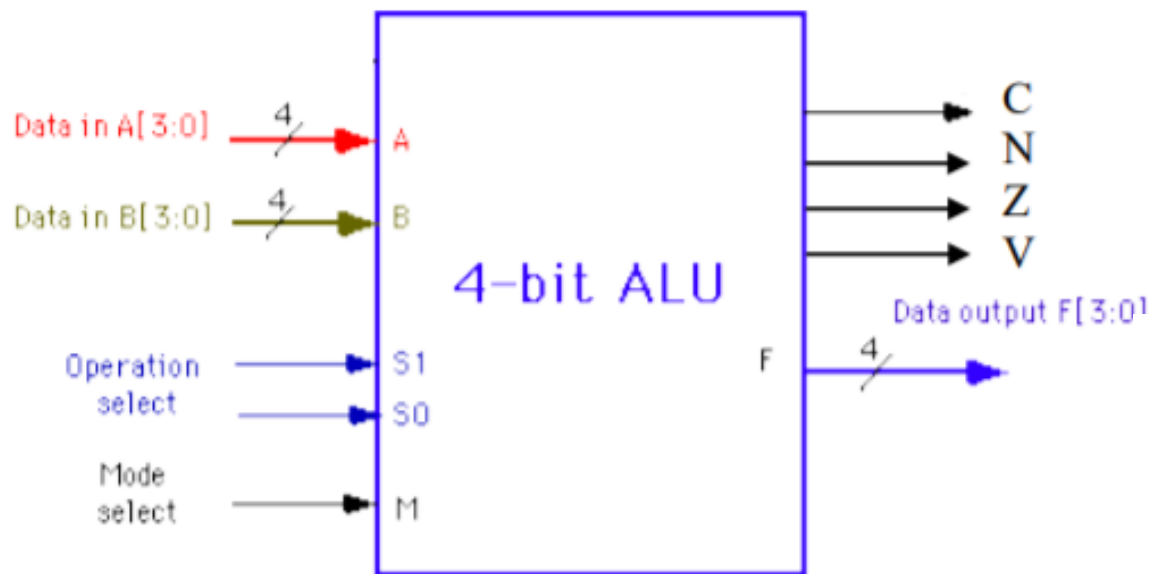


Figure 1: Block diagram of the 4-bit ALU.

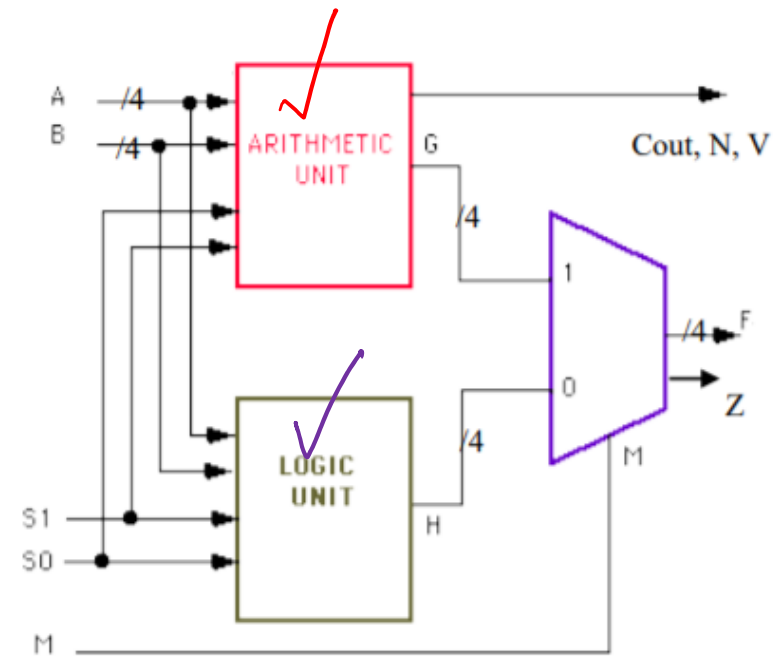


Figure 2: Block diagram of the ALU

ALU using basic chips

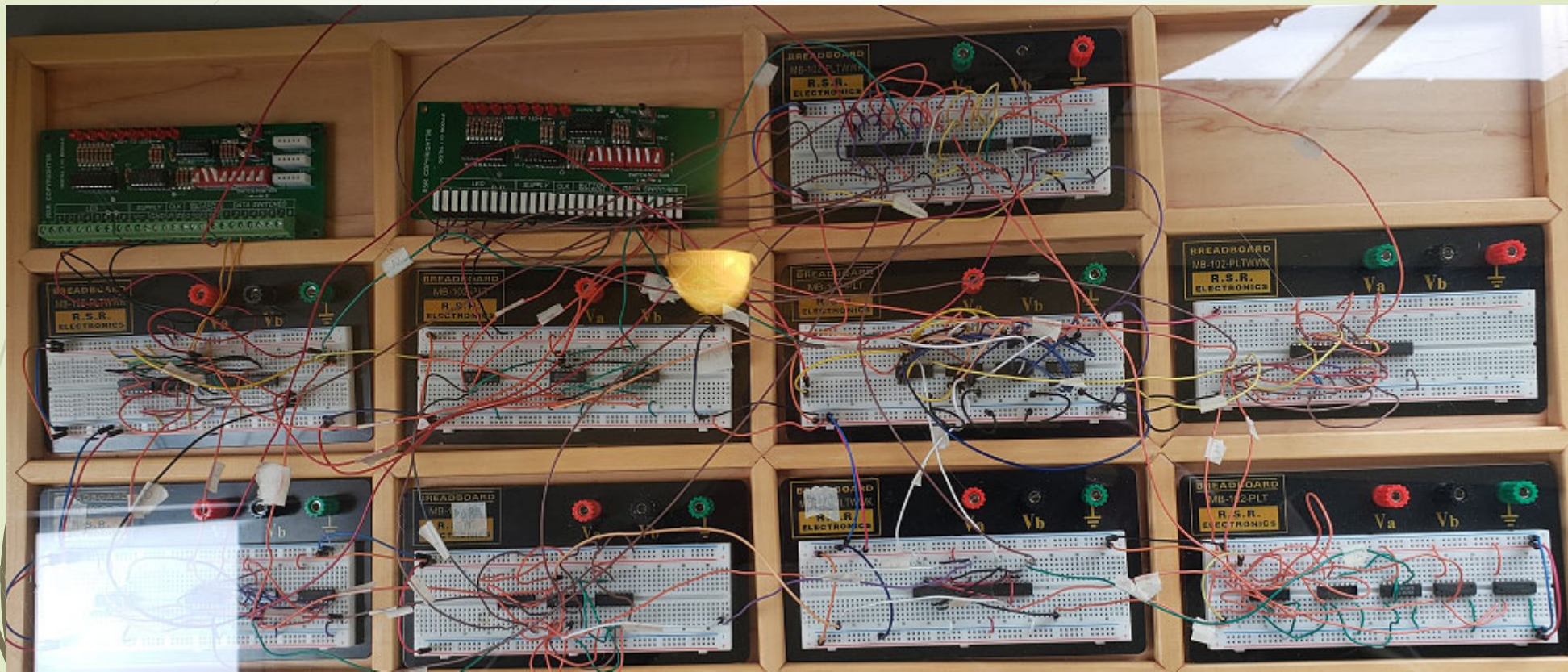


Table 1: Functions of ALU


Logic

M	S1	S0	FUNCTION	OPERATION (bit wise)
0	0	0	$A \cdot B$	AND
0	0	1	$A + B$	OR
0	1	0	$A \oplus B$	XOR
0	1	1	A'	NOT

Arithmetic

M	S1	S0	FUNCTION	OPERATION
1	0	0	$A + B$	Addition
1	0	1	$A - B$	Subtract
1	1	0	$A + 1$	Increment
1	1	1	$A - 1$	Decrement

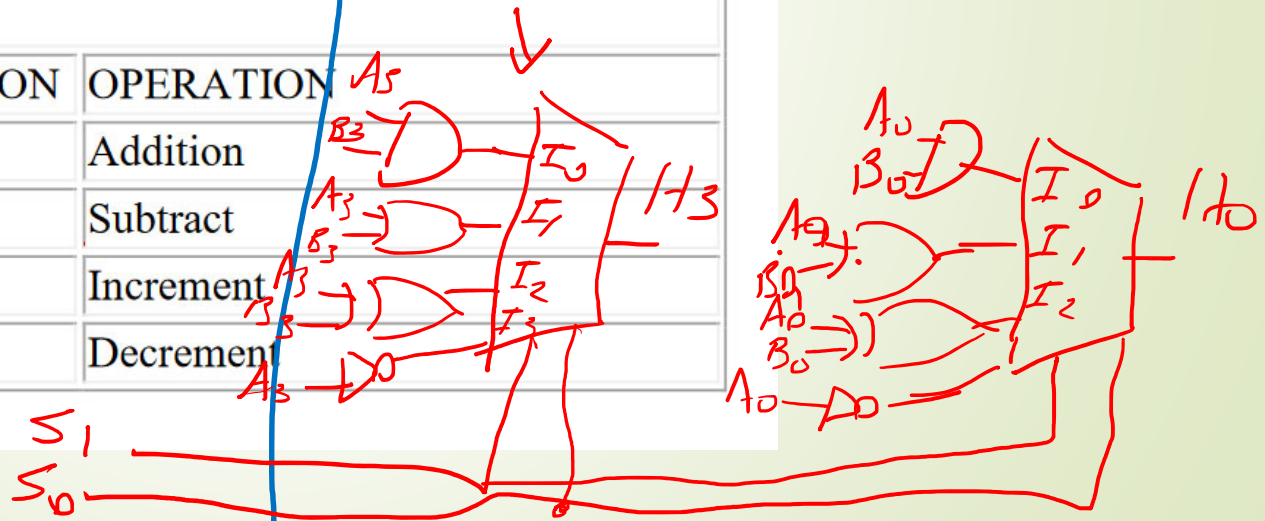$A_3 \cdot B_3$ $A_2 \cdot B_2$ $A_1 \cdot B_1$ $A_0 \cdot B_0$
 $A_3 + B_3$ $A_2 + B_2$ $A_1 + B_1$ $A_0 + B_0$
 $A_3 \oplus B_3$ $A_2 \oplus B_2$ $A_1 \oplus B_1$ $A_0 \oplus B_0$
 $\overline{A_3}$ $\overline{A_2}$ $\overline{A_1}$ $\overline{A_0}$



$M = 1$
 $A - 1$
 $A + 1$
 $A - B$
 $A + B$

1
 1
 0
 0

5, 50


Cout

sign

1 0 0 0 1

→


1 1 1 1

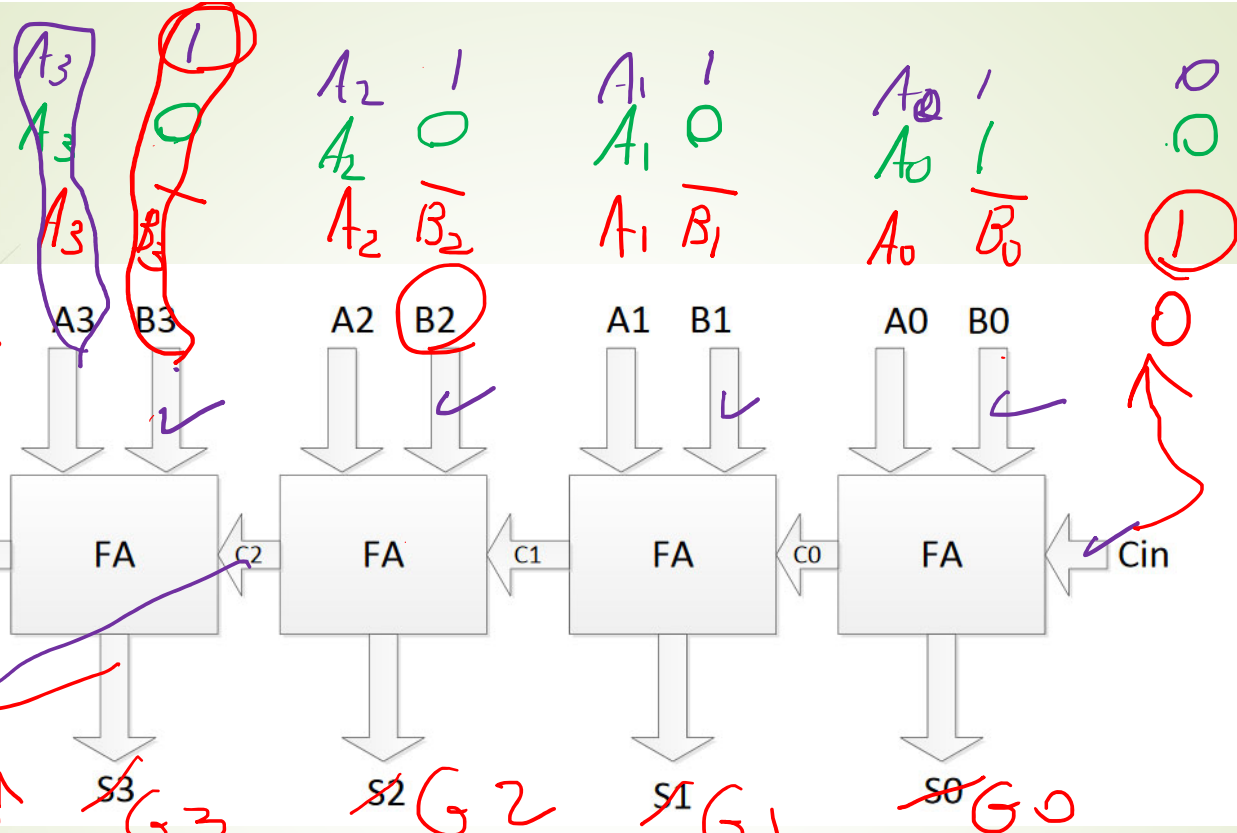

5, 50


MUX

S, S0	I0	I1	I2	I3
0 0	0	1	0	1
0 1	0	1	0	1
1 0	0	1	0	1
1 1	0	1	0	1

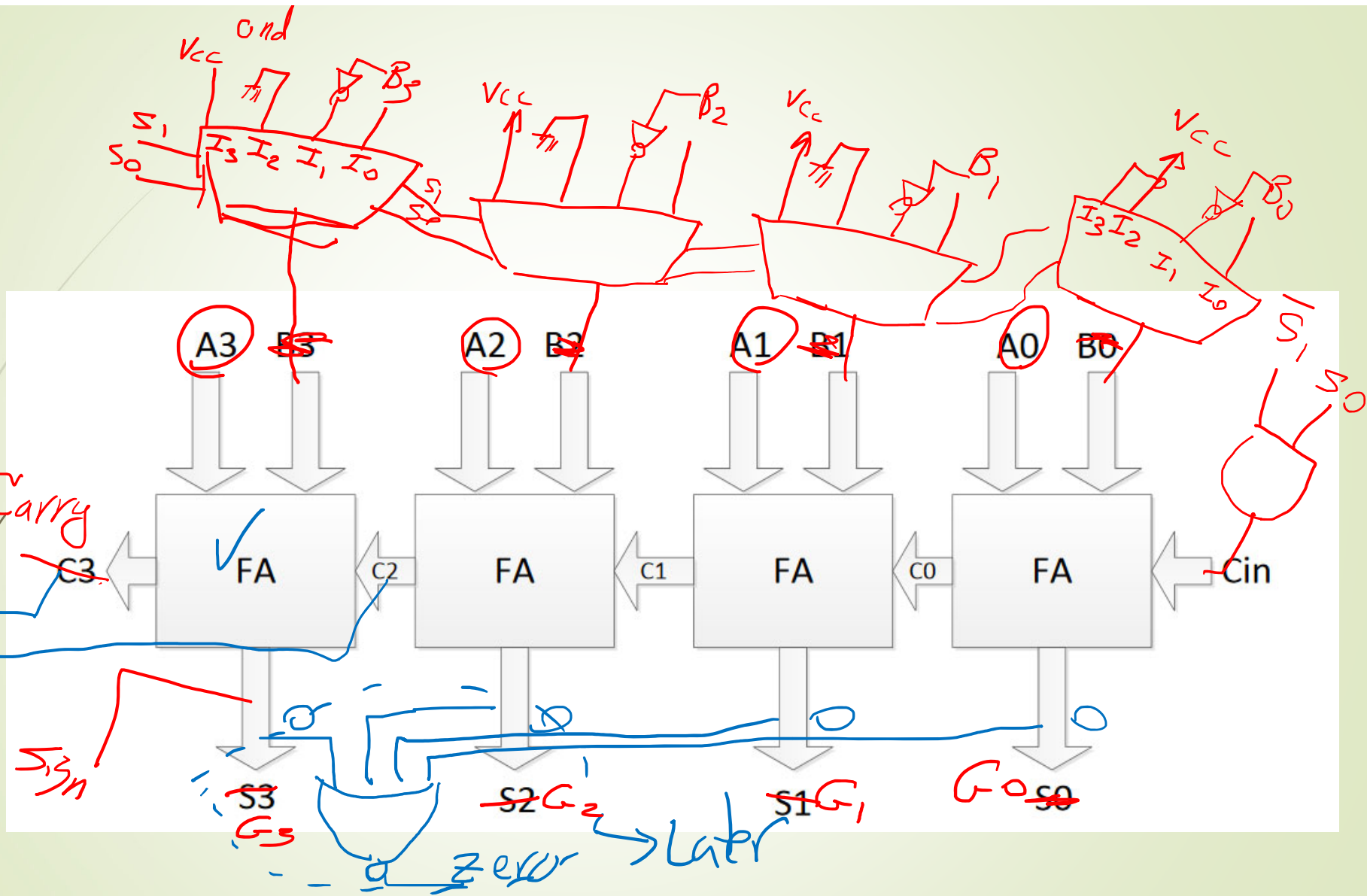


0110

OR

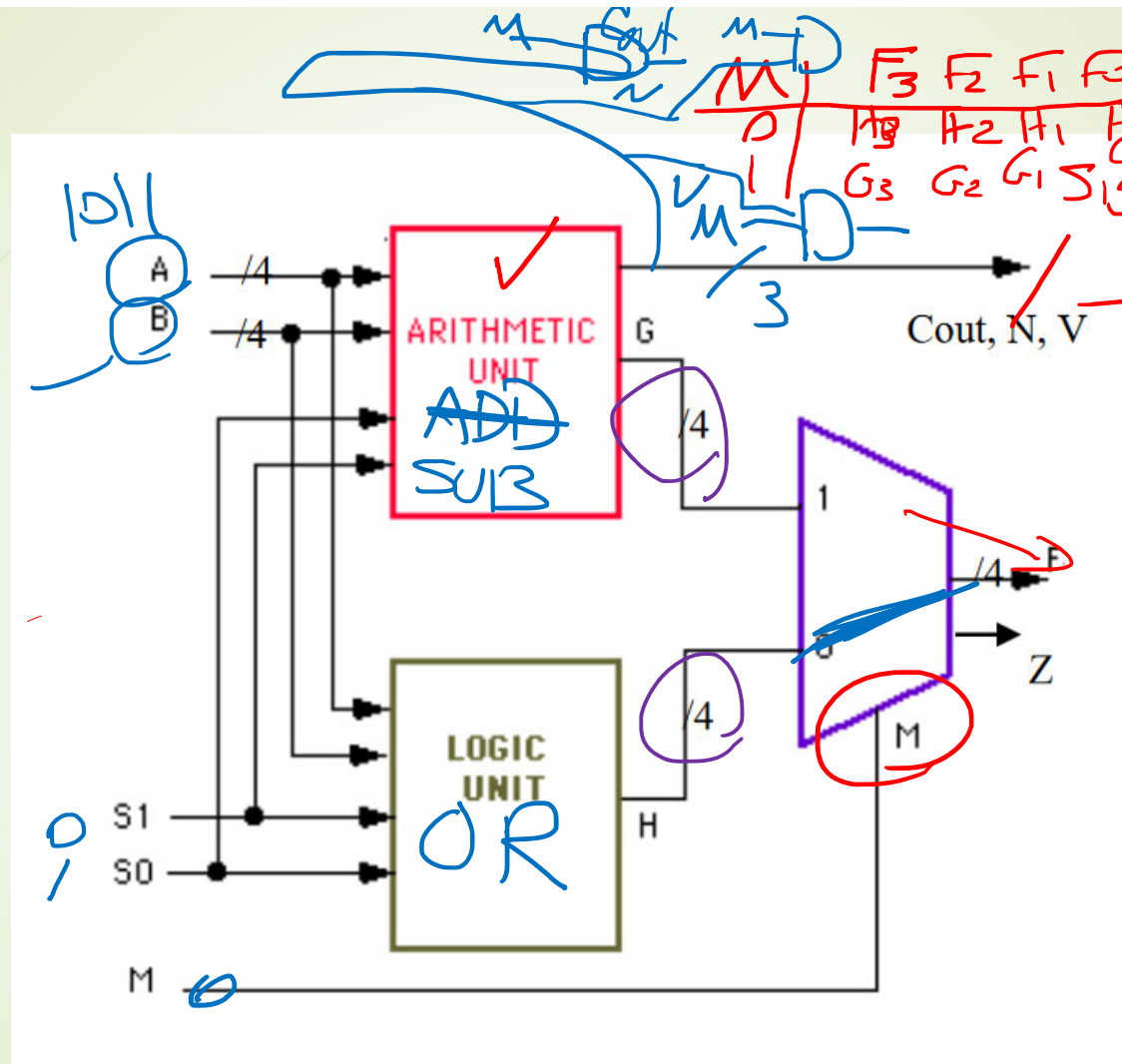

M	F ₃	F ₂	F ₁	F ₀
0	H ₃	H ₂	H ₁	H ₀
1	G ₃	G ₂	G ₁	G ₀

S	V
0	I ₀
1	I ₁

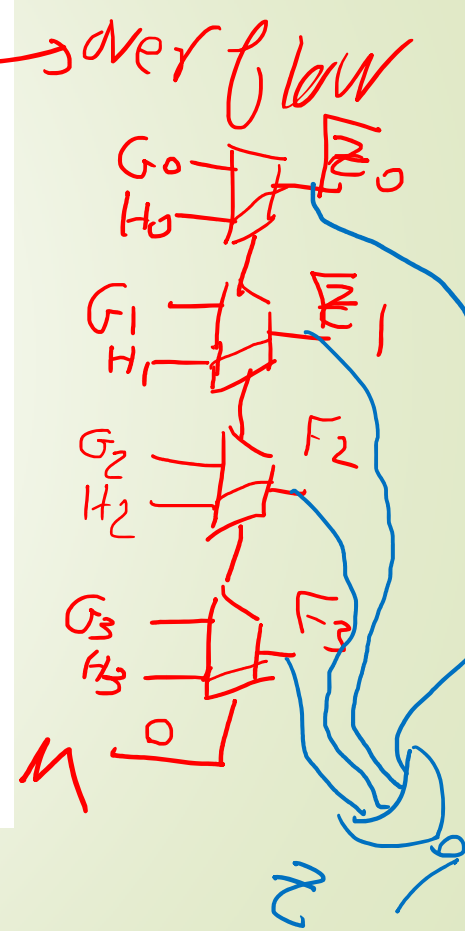

Lab report

- This lab report is worth 20 points (twice as a regular lab report)
- You are required to write a detailed report.
 - Start with the truth table, equation, and circuit of a full adder.
 - Take that step by step to build the arithmetic circuit.
 - Show why you used multiplexers: need to show function tables and discuss why and how Mux's did the job.
 - You need to do this at every level.
- Resulting simulation at every level need to be clearly illustrated and discussed.
 - Don't give me many undocumented simulations. Make sure grid size is 1 microsecond and window size is 16 microseconds. You should present two simulations for each arithmetic and logic operations.