

# EGC221

## Class Notes

### 4/19/2023



**Baback Izadi**

Division of Engineering Programs

[bai@engr.newpaltz.edu](mailto:bai@engr.newpaltz.edu)

 


Figure 1: Block diagram of the 4-bit ALU.

 


Figure 2: Block diagram of the ALU


Table 1: Functions of ALU

Logic

<del>S2</del>	S1	S0	FUNCTION	OPERATION (bit wise)
0	0	0	$A \cdot B$	AND
0	0	1	$A + B$	OR
0	1	0	$A \oplus B$	XOR
0	1	1	$A'$	NOT

Arithmetic

<del>S2</del>	S1	S0	FUNCTION	OPERATION
1	0	0	$A + B$	Addition
1	0	1	$A - B$	Subtract
1	1	0	$A + 1$	Increment
1	1	1	$A - 1$	Decrement

 


# Design of an ALU using Case Statement

$f(F == 0)$   
 $z = 1;$   
 $\text{else}$   
 $z = 0;$

$Z = (F == 4'b0);$

S	Function
0	A AND B
1	A OR B
2	A XOR B
3	$A'$
4	$A+B$
5	$A-B$
6	$A+1$
7	$A-1$

sign =  $F(3)$ ;  $\{C\} \{F\} = A+B$

 

```
// 74381 ALU
module alu(s, A, B, F);
input [2:0] s;
input [3:0] A, B;
output [3:0] F;
reg [3:0] F;
always @ (s or A or B)
case (s)
    0: F = A & B;
    1: F = A | B;
    2: F = A ^ B;
    3: F = ~A;
    4: F = A + B;
    5: F = A - B;
    6: F = A + 4'b0001;
    7: F = A + 4'b1111;
endcase
endmodule
```

Red annotations on the right side of the code include:  
 $A(3)A(2)A(1)A(0)$   
 $B(3)B(2)B(1)B(0)$   
 $+ \quad$   
 $CY \quad F(3)F(2)F(1)F(0)$   
 $CY, F$   
begin  
 $F = A \& B;$   
 $CY = 0;$   
 $sign = 0;$   
 $Z = 0;$   
end

4: begin

$$\{ \underline{C}Y, F \} = A + B ;$$

$$temp[3:0] = A[2:0] + B[2:0] ;$$

$$sign = F(3) ;$$

$$\overline{if}(F == 0)$$


$$z = 1 ;$$

else

$$z = 0 ;$$

$$V = temp[3] \wedge CY ;$$

end

 

```
// 74381 ALU
module VALU(s, A, B, F);
input [2:0] s;
input [3:0] A, B;
output [3:0] F;
reg [3:0] F;
always @(s or A or B)
case (s)
0: F = 4'b0000;
1: F = B - A;
2: F = A - B;
3: F = A + B;
4: F = A ^ B;
5: F = A | B;
6: F = A & B;
7: F = 4'b1111;
endcase
endmodule
```

## . Concatenation and Replication in Verilog

- ▶ The concatenation operator "{ , }" combines (concatenates) the bits of two or more data objects. The objects may be scalar (single bit) or vectored (multiple bit). Multiple concatenations may be performed with a constant prefix and is known as replication.

```
module Concatenation (A, B, Y);
    input [2:0] A, B;
    output [14:0] Y;
    parameter C=3'b011;
    reg [14:0] Y;
    always @(A or B)
    begin
        Y={A, B, {2{C}}, 3'b110};
    end
endmodule
```

# BIT-WISE Operations in verilog



```
module Bitwise (A, B, Y);
    input [6:0] A;
    input [5:0] B;
    output [6:0] Y;
    reg [6:0] Y;
    always @(A or B)
    begin
        Y[0]=A[0]&B[0]; //binary AND
        Y[1]=A[1] | B[1]; //binary OR
        Y[2]=!(A[2]&B[2]); //negated AND
        Y[3]=!(A[3] | B[3]); //negated OR
        Y[4]=A[4]^B[4]; //binary XOR
        Y[5]=A[5]~^B[5]; //binary XNOR
        Y[6]=!A[6]; //unary negation
    end
endmodule
```



```
module ALU8bit( Opcode, Operand1, Operand2,
Result, flagC, flagZ); input [2:0] Opcode;
input [7:0] Operand1, Operand2;
output reg [15:0] Result = 16'b0;
output reg flagC = 1'b0, flagZ = 1'b0;
parameter [2:0] ADD = 3'b000, SUB = 3'b001, MUL =
3'b010, AND = 3'b011, OR = 3'b100, NAND = 3'b101,
NOR = 3'b110, XOR = 3'b111;
always @ (Opcode or Operand1 or Operand2)
begin
case (Opcode)
ADD: begin
Result = Operand1 + Operand2;
flagC = Result[8];
flagZ = (Result == 16'b0);
end
SUB: begin
Result = Operand1 - Operand2;
flagC = Result[8];
flagZ = (Result == 16'b0);
end
MUL: begin
Result = Operand1 * Operand2;
flagZ = (Result == 16'b0);
end
```

```
AND: begin
Result = Operand1 & Operand2;
flagZ = (Result == 16'b0);
end
OR: begin
Result = Operand1 | Operand2;
flagZ = (Result == 16'b0);
end
NAND: begin
Result = ~(Operand1 & Operand2);
flagZ = (Result == 16'b0);
end
NOR: begin
Result = ~(Operand1 | Operand2);
flagZ = (Result == 16'b0);
end
XOR: begin
Result = Operand1 ^ Operand2;
flagZ = (Result == 16'b0);
end
default: begin
Result = 16'b0;
flagC = 1'b0; flagZ = 1'b0;
end
endcase
end
endmodule
```