

EGC221

Class Notes

4/26/2023



Baback Izadi

Division of Engineering Programs

bai@engr.newpaltz.edu

Verilog – D Flip-flop

```
module D-flipflop (D, Clk, Q);
```

```
    input D, Clk;
```


```
    output Q; reg Q;
```

```
    always @(posedge Clk)
```

```
        Q = D;
```



```
Endmodule
```

D
CLK

 


Finite State Machines (FSM)

  - State diagrams are representations of Finite State Machines (FSM)
- Mealy FSM
 - Output depends on input and state
 - Output is not synchronized with clock
 - can have temporarily unstable output
- Moore FSM
 - Output depends only on state




Finite State Machines

 - Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**



Example: Light Switch

- State transition diagram

 

PS	Q	Button	NS	Q & D	Light
0	0	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	1
1	1	1	0	1	1



$$D = Q'B + QB'$$

$$\text{Light} = Q$$

Note: B = Button


BUTTON

CLK

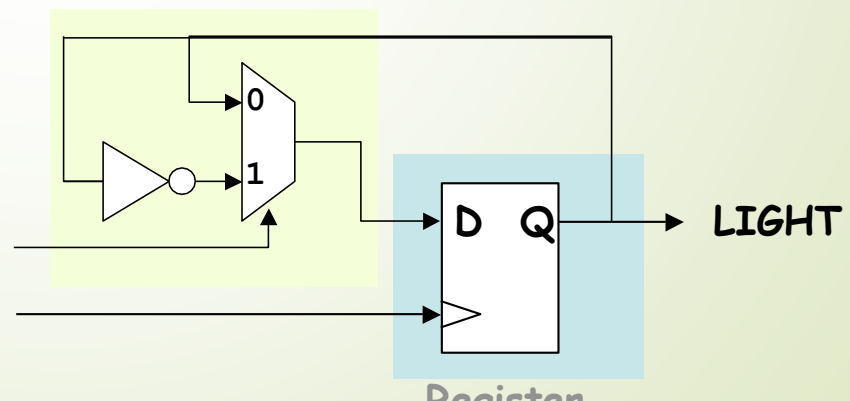 


Example: Light Switch

- State transition diagram

 


- Logic diagram

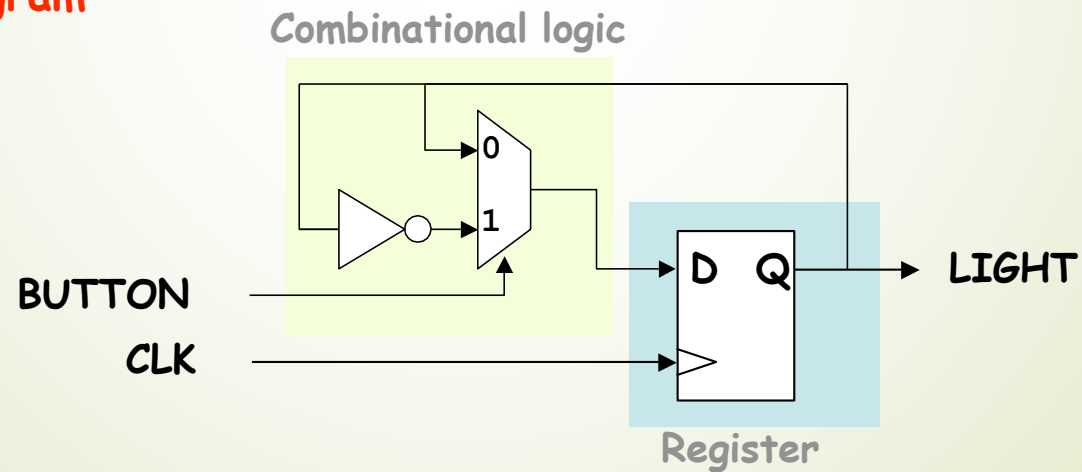


CLOCKED CIRCUIT FOR ON/OFF BUTTON
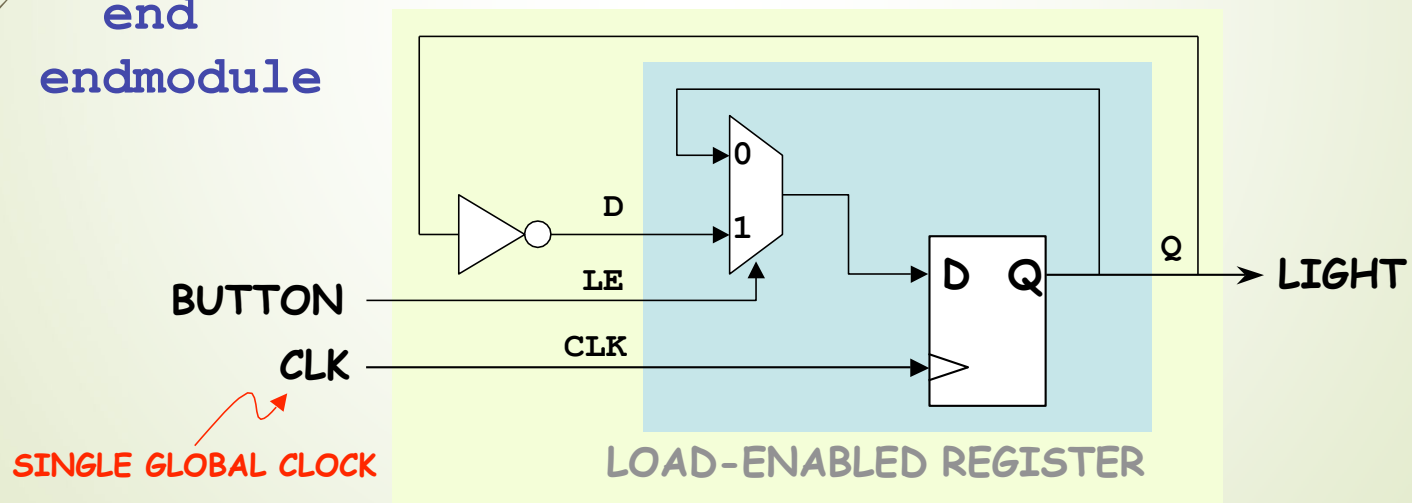
```
module onoff(clk,button,light);  
  input clk,button;  
  output light; reg light;  
  always @ (posedge clk) begin  
    if (button) light <= ~light;  
  end  
endmodule
```



Example: 4-bit Counter

• Logic diagram

 

• Verilog

4-bit counter

```
module counter(clk, count);
```

```
input clk;
```

```
output [3:0] count;
```

```
reg [3:0] count;
```

```
always @ (posedge clk) begin
```


```
count <= count+1;
```

```
End
```

```
endmodule
```

→ count(3) count(2) count(1) count(0)

• Logic diagram

 

• Verilog

```
# 4-bit counter with enable
module counter(clk,enb,count) ;
  input  clk,enb;
  output [3:0] count;
  reg [3:0] count;

  always @ (posedge clk) begin
    count <= enb ? count+1 : count;
  end
endmodule
```

Could I use the following instead?
if (enb) count <= count+1;


else

count = count;



example. 4-bit counter

• Logic diagram

 

• Verilog


```
# 4-bit counter with enable and synchronous clear
module counter(clk,enb,clr,count);
    input clk,enb,clr;
    output [3:0] count;
    reg [3:0] count;

    always @ (posedge clk) begin
        count <= clr ? 4'b0 : (enb ? count+1 : count);
    end
endmodule
```

4-bit Shift Register with Reset

```
module srg_4_r_v (CLK, RESET, SI, Q, SO);  
  input CLK, RESET, SI;  
  output [3:0] Q;  
  output SO;  
  reg [3:0] Q;  
  assign SO = Q[3];  
  always@(posedge CLK or posedge RESET) begin  
    if (RESET)  
      Q <= 4'b0000;  
    else  
      Q <= {Q[2:0], SI};  
    end  
  endmodule
```

1st Asynchronous input

 


4-bit Binary Counter with Reset


```
module count_4_r_v (CLK, RESET, EN, Q, CO);  
  input CLK, RESET, EN;  
  output [3:0] Q;  
  output CO;  
  reg [3:0] Q;  
  assign CO = (count == 4'b1111 && EN == 1'b1) ? 1 : 0;  
  always@(posedge CLK or posedge RESET)  
  begin  
    if (RESET)  
      Q <= 4'b0000;  
    else if (EN)  
      Q <= Q + 4'b0001;  
    end  
endmodule
```

You are to design a 4-bit counter with the following inputs and functionality:

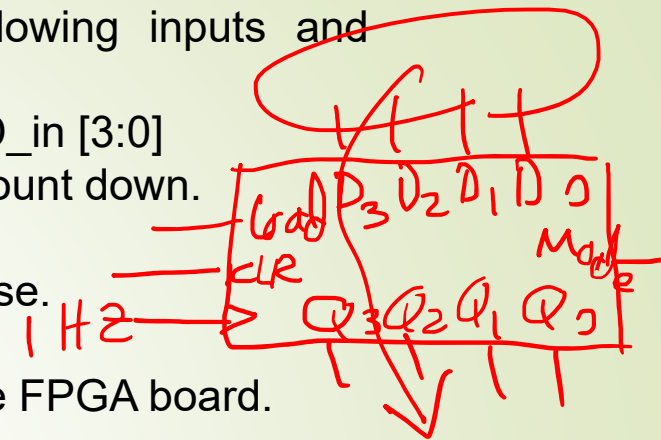- Load (ld): if activated, count will be loaded from D_in [3:0]
- Mode: if 0, counter counts up. Otherwise, it will count down.
- Clear (clr): If activated, count will be 0
- Clock 1 Hz is generated from the previous exercise.



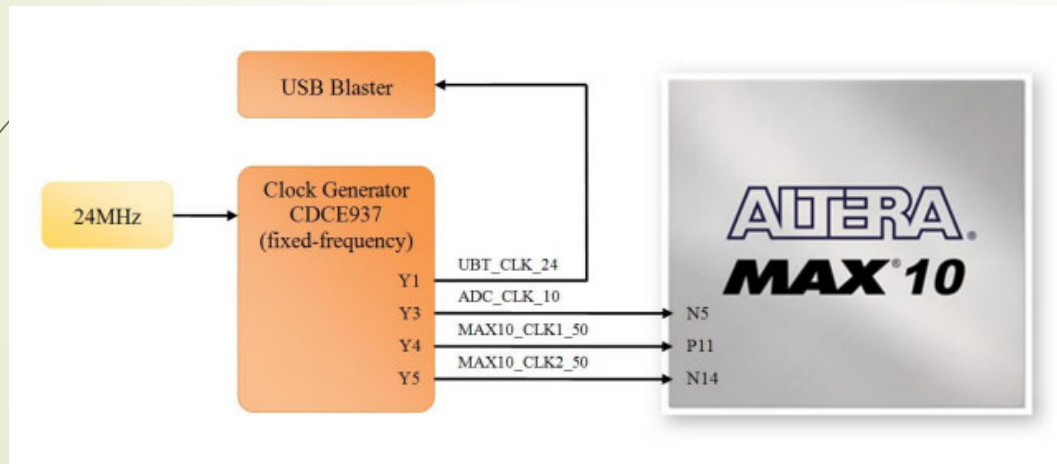Complete the following code and implement it on the FPGA board.



ld = 1
Q3...Q0 ← D3...D0

Signal Name	FPGA Pin No.	Description
ADC_CLK_50	PIN_N5	10 MHz clock input for ADC (Bank 3B)
MAX10_CLK1_50	PIN_P11	50 MHz clock input (Bank 3B)
MAX10_CLK2_50	PIN_N14	50 MHz clock input (Bank 3B)

Device family

Family:
MAX 10 (DA/DF/DC/SA/SC)

Device:
All

Target device

☐ Auto device selected by the Fitter

☒ Specific device selected in 'Available devices' list

☐ Other: n/a

Show in 'Available devices' list

Package:
Any

Pin count:
Any


Core speed grade:
Any

Name filter:

☒ Show advanced devices

Available devices:

Name	Core Voltage	LEs	Total I/Os	GPIOs	Memory Bits	Embedded multiplier
10M50DAF484C7G	1.2V	49760	360	360	1677312	288

 

Signal Name	FPGA Pin No.	Description
KEY0	PIN_B8	Push-button[0]
KEY1	PIN_A7	Push-button[1]

Board	Device Name
DE10-Lite	MAX 10: 10M50DAF484C7G


Pin Assignment

Signal Name	FPGA Pin No.	Description
SW0	PIN_C10	Slide Switch[0]
SW1	PIN_C11	Slide Switch[1]
SW2	PIN_D12	Slide Switch[2]
SW3	PIN_C12	Slide Switch[3]
SW4	PIN_A12	Slide Switch[4]
SW5	PIN_B12	Slide Switch[5]
SW6	PIN_A13	Slide Switch[6]
SW7	PIN_A14	Slide Switch[7]
SW8	PIN_B14	Slide Switch[8]
SW9	PIN_F15	Slide Switch[9]

Signal Name	FPGA Pin No.	Description
LEDR0	PIN_A8	LED [0]
LEDR1	PIN_A9	LED [1]
LEDR2	PIN_A10	LED [2]
LEDR3	PIN_B10	LED [3]
LEDR4	PIN_D13	LED [4]
LEDR5	PIN_C13	LED [5]
LEDR6	PIN_E14	LED [6]
LEDR7	PIN_D14	LED [7]
LEDR8	PIN_A11	LED [8]
LEDR9	PIN_B11	LED [9]

 Exercise 1: Divide-by-N Circuit:

Design, simulate, and build a Divide-by-N circuit that will divide the on board clock from 50 MHz down to ~1 Hz. The basic principle is as follows:



//The goal of this always procedural block is to generate 1Hz clock from a
//50MHz clock that is used in the Altera FPGA board.

module Divide_by_50M_counter(clr,clk,clk_1Hz);

input clr,clk;

output clk_1Hz;

reg clk_1Hz =1'b0;

integer counter_50M =0; ←

always @(posedge clk, posedge clr)

begin

if (clr)

counter_50M <=0;

else if (counter_50M <25000000)

begin

counter_50M <= counter_50M + 1;

end

else if (counter_50M ==25000000)

begin

clk_1Hz <= !clk_1Hz;

counter_50M <=0;


end

end

endmodule

25,000,000

→ output

 


```
module up_down_counter(mode,clr,ld,D_in,clk,count,clk_1Hz);
```

```
input mode,clr,ld,clk;
```

```
input [3:0] D_in;
```

```
output clk_1Hz;
```

```
output [3:0] count;
```

```
reg [3:0] count;
```

```
reg clk_1Hz = 1'b0;
```

```
integer counter_50M = 0;
```

} From Prev. Slide

```
//If "ld =1" we load the external data through D_in[3:0], if mode is active  
// it will be counting up and if mode is inactive it will count down.
```

```
always @(posedge clk_1Hz, posedge clr)
```

begin

```
. if (clr)
```

```
count <= 0;
```

```
else if (ld)
```

```
count <= D_in[3:0];
```

```
.
```

```
endmodule
```

→ {0 up
1 down} → Q = P → 4 inputs → output

load
if (mode)
count ← count - 1;