

EGC221

Class Notes


11/20/2018



Baback Izadi
Division of Engineering Programs
bai@engr.newpaltz.edu



Verilog – D Flip-flop
 
```
module D-flipflop (D, Clk, Q);  
  
    input D, Clk;  
    output Q;    reg Q;  
  
    always @(posedge Clk)  
        Q = D;  
  
Endmodule
```




Finite State Machines (FSM)

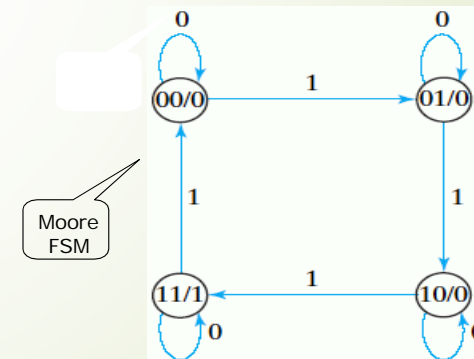 - State diagrams are representations of Finite State Machines (FSM)
- Mealy FSM
 - Output depends on input and state
 - Output is not synchronized with clock
 - can have temporarily unstable output
- Moore FSM
 - Output depends only on state




Finite State Machines

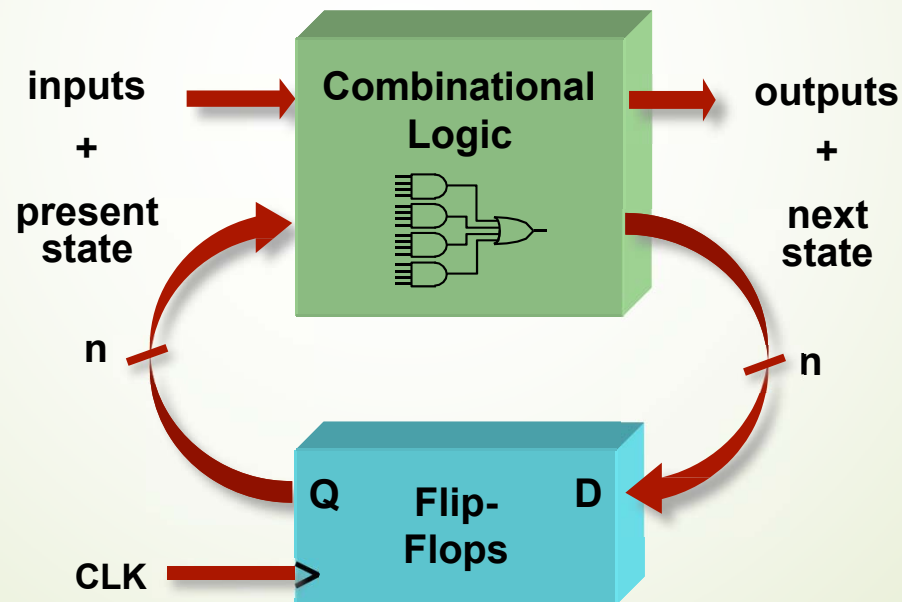- **Finite State Machines (FSMs)** are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**




Example: Light Switch

- State transition diagram

 


PS	Q	Button	NS	Q & D	Light
0	0	0	0	0	0
0	1	1	1	0	0
1	0	1	1	1	1
1	1	1	0	1	1

 

$$D = Q'B + QB'$$


$$\text{Light} = Q$$

Note: B = Button **BUTTON**
CLK

 


Example: Light Switch

- State transition diagram

 


- Logic diagram

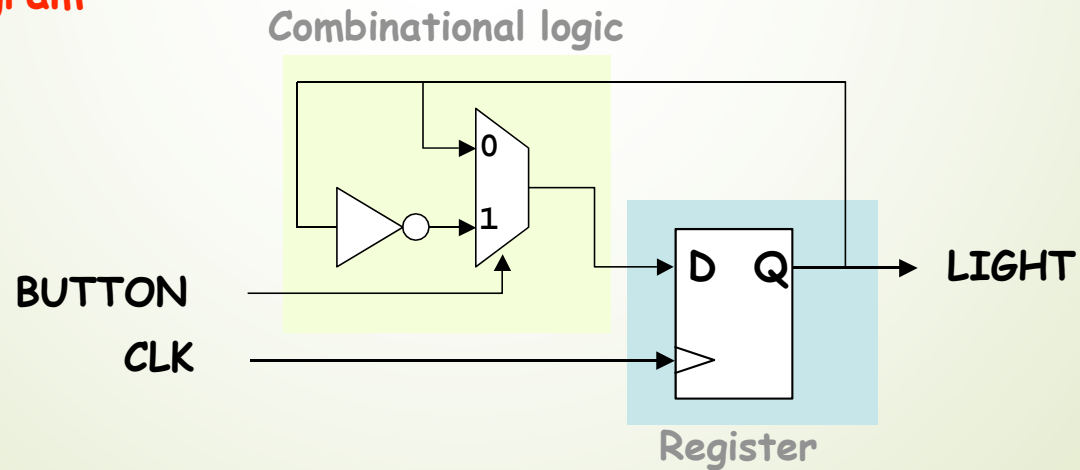


CLOCKED CIRCUIT FOR ON/OFF BUTTON
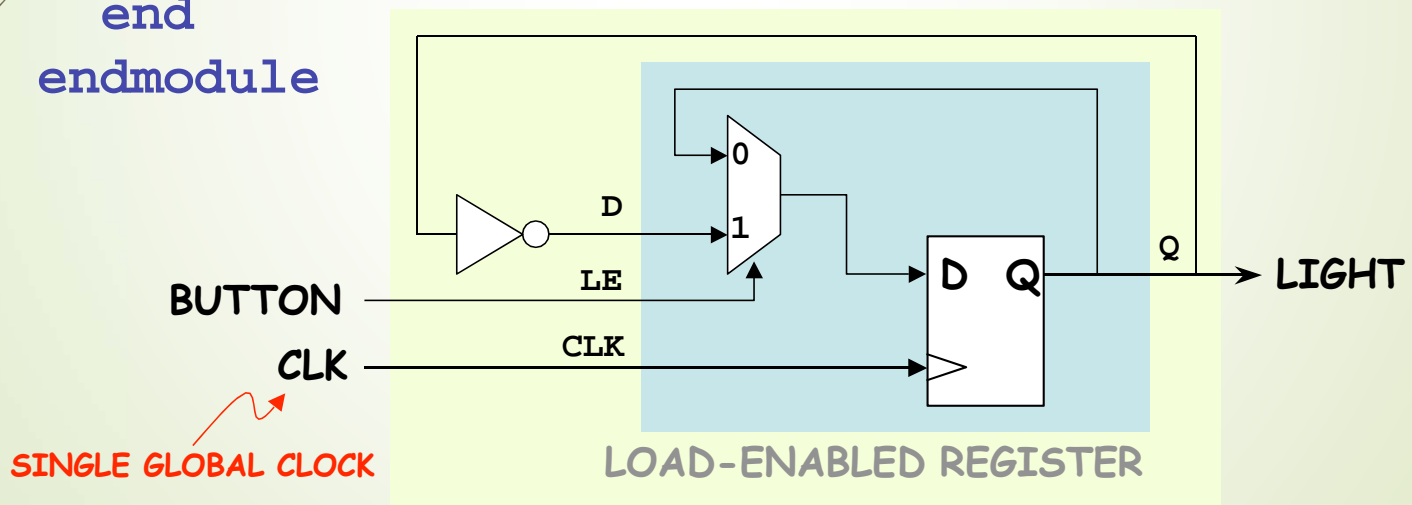
```
module onoff(clk,button,light);  
  input clk,button;  
  output light; reg light;  
  always @ (posedge clk) begin  
    if (button) light <= ~light;  
  end  
endmodule
```



Example: 4-bit Counter

- Logic diagram

 


- Verilog

```
# 4-bit counter
module counter(clk, count);
  input clk;
  output [3:0] count;
  reg [3:0] count;

  always @ (posedge clk) begin
    count <= count+1;
  end
endmodule
```


• Logic diagram

 

• Verilog

```
# 4-bit counter with enable
module counter(clk,enb,count);
  input  clk,enb;
  output [3:0] count;
  reg [3:0] count;

  always @ (posedge clk) begin
    count <= enb ? count+1 : count;
  end
endmodule
```


Could I use the following instead?
if (enb) count <= count+1;

else



example. 4-bit counter

• Logic diagram

 

• Verilog

```
# 4-bit counter with enable and synchronous clear
module counter(clk,enb,clr,count);
  input clk,enb,clr;
  output [3:0] count;
  reg [3:0] count;

  always @ (posedge clk) begin
    count <= clr ? 4'b0 : (enb ? count+1 : count);
  end
endmodule
```

4-BIT SHIFT REGISTER WITH RESET

```
module srg_4_r_v (CLK, RESET, SI, Q,SO);
input CLK, RESET, SI;
output [3:0] Q;
output SO;
reg [3:0] Q;
assign SO = Q[3];
always@(posedge CLK or posedge RESET) begin
    if (RESET)
        Q <= 4'b0000;
    else
        Q <= {Q[2:0], SI};
    end
endmodule
```

4-bit Binary Counter with Reset

```
module count_4_r_v (CLK, RESET, EN, Q, CO);
input CLK, RESET, EN;
output [3:0] Q;
output CO;
reg [3:0] Q;
assign CO = (count == 4'b1111 && EN == 1'b1) ? 1 : 0;
always@(posedge CLK or posedge RESET)
begin
if (RESET)
Q <= 4'b0000;
else if (EN)
Q <= Q + 4'b0001;
end
endmodule
```

//The goal of this always procedural block is to generate 1Hz clock from a //50MHz clock that is used in the Altera FPGA board.

```
module Divide_by_50M_counter(clr,clk,clk_1Hz);
```

```
input clr,clk;
```

```
output clk_1Hz;
```

```
reg clk_1Hz =1'b0;
```

```
integer counter_50M =0;
```

```
always @(posedge clk, posedge clr)
```

```
begin
```

```
  if (clr)
```

```
    counter_50M <=0;
```

```
  else if (counter_50M <25000000)
```

```
    begin
```

```
      counter_50M <= counter_50M + 1;
```

```
    end
```

```
  else if (counter_50M ==25000000)
```

```
    begin
```


```
      clk_1Hz <= !clk_1Hz;
```

```
      counter_50M <=0;
```


```
    end
```

```
end
```

```
endmodule
```

 

```
module up_down_counter(mode,clr,ld,D_in,clk,count,clk_1Hz);
input mode,clr,ld,clk;
input [3:0] D_in;
output clk_1Hz;
output [3:0] count;
reg [3:0] count;
reg clk_1Hz =1'b0;
integer counter_50M =0;
//The goal of this always procedural block is to generate 1Hz clock from a
//50MHz clock that is used in the Xilinx Nexus FPGA board.
always @(posedge clk)
begin
if (clr)
counter_50M =0;
else if (counter_50M <25000000)
begin
counter_50M = counter_50M + 1;
end
else if (counter_50M ==25000000)
begin
clk_1Hz <= !clk_1Hz;
counter_50M =0;
end
end
end
```



//If "ld =1" we load the external data through D_in[3:0], if mode is active
// it will be counting up and if mode is inactive it will count down.

```
always @(posedge clk_1Hz, posedge clr)
  if(clr)
    count <= 0 ;
  else if(ld)
    count <= D_in ;
  else if (mode)
    count <= 0 ;
  else
    count <= 0 ;
```