

EGC220

Class Notes

9/13/2018


Baback Izadi

Division of Engineering Programs
bai@engr.newpaltz.edu

```

module fig2_5 (L, D, X, A);
  input D, X, A;
  output L;
  wire X_n, t2;
  not (X_n, X);
  and (t2, D, X_n);
  or (L, t2, A);
endmodule

```

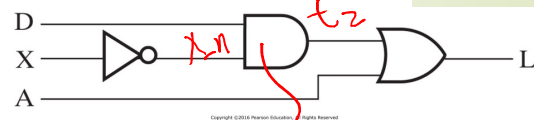

Copyright ©2016 Pearson Education, All Rights Reserved

1. Perform the following operations in binary. Assume signed 2's complement notation.

a. $54 + 72$

		5	64	32	16	8	4	2	1
+54	0	0	1	1	0	1	1	0	
+72	0	1	0	0	1	0	0	0	
<hr/>									
+126	0	1	1	1	1	1	1	0	

b. $54 - 72$

54	0	0	1	1	0	1	1	0	
-72	1	0	1	1	1	0	0	0	
<hr/>									
-18	1	0	1	0	1	1	0	0	

c. $72 - 54$

+72	0	1	0	0	1	0	0	0	
-54	1	1	0	0	1	0	1	0	
<hr/>									
+18	0	0	0	1	0	0	1	0	

$\rightarrow C = 1$

1. Perform the following operations in binary. Assume signed 2's complement notation.

$(-72) - (-54)$

		5	64	32	16	8	4	2	1
+72	0	1	0	0	1	0	0	0	
-72	1	0	1	1	1	0	0	0	
54	0	0	1	1	0	1	1	0	
-54	1	1	0	0	1	0	1	0	
$-(-54)$	0	0	1	1	0	1	1	0	

-72	1	0	1	1	1	0	0	0	
$-(-54)$	0	0	1	1	0	1	1	0	
<hr/>									
	1	1	0	1	1	1	0		

$\rightarrow -00010010$
 -18

1. Decide the following ASCII code

1000010 1101001 1101100 1101100 1000111 1100001 1110100 1100101 1110011

B i l l G a t e s

TABLE 1-5
American Standard Code for Information Interchange (ASCII)

B ₄ B ₃ B ₂ B ₁	B ₇ B ₆ B ₅							
	000	001	010	011	100	101	110	111
0000	NULL	DLE	SP	0	@	P	`	p
0001	SOH	DC1	!	1	A	Q	a	q
0010	STX	DC2	"	2	B	R	b	r
0011	ETX	DC3	#	3	C	S	c	s
0100	EOT	DC4	\$	4	D	T	d	t
0101	ENQ	NAK	%	5	E	U	e	u
0110	ACK	SYN	&	6	F	V	f	v
0111	BEL	ETB	'	7	G	W	g	w
1000	BS	CAN	(8	H	X	h	x
1001	HT	EM)	9	I	Y	i	y
1010	LF	SUB	*	:	J	Z	j	z
1011	VT	ESC	+	;	K	[k	{
1100	FF	FS	,	<	L	\	l	
1101	CR	GS	-	=	M]	m	}
1110	SO	RS	.	>	N	^	n	~
1111	SI	US	/	?	O	_	o	DEL

1. Convert 134₁₀ to BCD code

0001 0011 0100 = 134₁₀


1. By means of truth table and waveform determine the outputs of the circuit

ABCD | X
0000 | 0

a.




b.

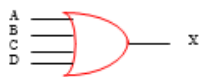

= A + B + C + D

ABC | ABC
000 | 0
001 | 0
010 | 0
011 | 0
100 | 0
101 | 0
110 | 0
111 | 0

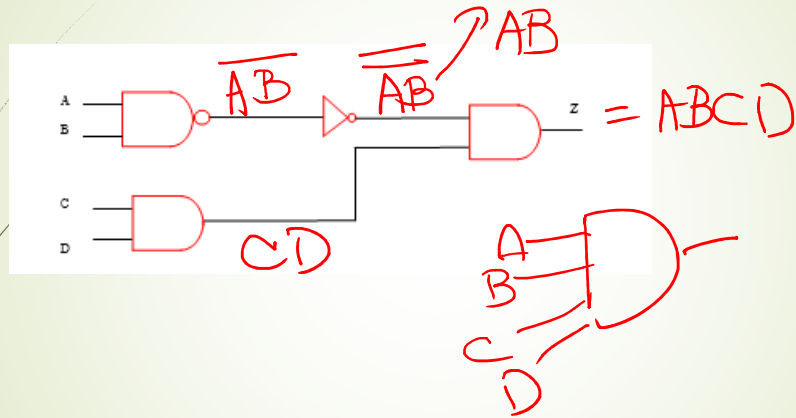1. Write the Boolean expression of the following circuit:



1. Draw the logic circuit realization of the following Boolean expression as stated. Do not simplify!

$$Y = f(A, B, C) = \overline{(A + B)(\overline{B} + C)}$$

