

How-to Easily Design an Adder Using VHDL

Preface

We are going to take a look at designing a simple unsigned adder circuit in VHDL through different coding styles. By doing so, this will get you familiar with designing by different methods and, hopefully, show you to look for the easy solution before attempting to code anything.

The specific circuit we are going to model in this how-to is a 4-bit unsigned adder. In the first pass of the design, we will build a 1-bit full adder (or (3,2) counter) slice that will be used to build the full 4-bit adder. In the second pass of the design, we are going to build the circuit using the IEEE std_logic unsigned package, a much more code efficient and scalable design.

This how-to assumes you have some knowledge of VHDL and understand concepts such as entities, architectures, and signals.

1-Bit Full Adder

As you know, a 1-bit full adder is characterized by the following equations:

$$\begin{aligned} \text{sum} &= x \text{ xor } y \text{ xor } \text{cin} \\ \text{cout} &= (x \text{ and } y) \text{ or } (x \text{ and } \text{cin}) \text{ or } (y \text{ and } \text{cin}) \end{aligned}$$

where x, y, and cin are the two inputs and the carry in, respectively while sum and cout are the sum and carry out. A pictorial representation of the component is listed in figure 1.

 


Figure 1 - 1-Bit Full Adder Component

The VHDL code for the above component (downloadable file [add_1_bit.vhd](#)) is as follows:

```
library IEEE;
use IEEE.std_logic_1164.all;

entity add_1_bit is
  port (
    x: in std_logic;
    y: in std_logic;
    cin: in std_logic;
    sum: out std_logic;
    cout: out std_logic
  );
end add_1_bit;

architecture rtl of add_1_bit is
begin
  sum <= x xor y xor cin;
  cout <= (x and y) or (x and cin) or (y and cin);
end rtl;
```

As you can see, we are using the standard IEEE libraries, which include `std_logic`, in order to create components that can be synthesized easily to hardware. Using signal types such as `bit` may not synthesize or produce unpredictable results. Always use the `std_logic_1164` library!

This is a pretty standard component. In the entity declaration, `x`, `y`, and `cin` are declared as inputs of type `std_logic`. The outputs are `sum` and `cout` of type `std_logic`. In the architecture section, we define the outputs `sum` and `cout` to be concurrent statements based directly off the inputs. Nothing special about this component, I'm sure you have already seen a version of this model.

4-Bit Unsigned Adder using 1-Bit Full Adder Component

Now we are going to make four copies of the above component to make our 4-bit unsigned adder component, thus producing a ripple-carry adder. This is done through instantiating four copies of the above 1-bit adder component in VHDL. Figure 2 illustrates the connections of this component.

 


Figure 2 - 4-Bit Unsigned Adder

The inputs to the component are the 4-bit unsigned numbers, `x` and `y`, and the carry in that includes `cin` and the internal ripple carries between each 1-bit block. The 4-bit output `sum` and `cout` are shown as outputs of the systems. Listed below is the VHDL code for the component (downloadable [add_4_bits.vhd](#)).

```
library IEEE;
use IEEE.std_logic_1164.all;

entity add_4_bits is
  port (
    x: in std_logic_vector(3 downto 0);
    y: in std_logic_vector(3 downto 0);
    cin: in std_logic;
    sum: out std_logic_vector(3 downto 0);
    cout: out std_logic
  );
end add_4_bits;

architecture rtl of add_4_bits is
  component add_1_bit
  port (
    x: in std_logic;
    y: in std_logic;
    cin: in std_logic;
    sum: out std_logic;
    cout: out std_logic
  );
end component;
```

```

signal i_carry: std_logic_vector(2 downto 0);
begin
cell_1: add_1_bit
  port map (x(0), y(0), cin, sum(0), i_carry(0));

cell_2: add_1_bit
  port map (x(1), y(1), i_carry(0), sum(1), i_carry(1));

cell_3: add_1_bit
  port map (x(2), y(2), i_carry(1), sum(2), i_carry(2));

cell_4: add_1_bit
  port map (x(3), y(3), i_carry(2), sum(3), cout);
end rtl;

```

You can see that we define the component `add_1_bit` in the architecture declaration section of the code. Four versions of this component are then declared in the body section of the code, with all of the appropriate "glue" between each component. As this point, you must be asking, "isn't there an easy way to do this?". From my perspective, this is a lot of code for just a 4-bit unsigned adder; the point to VHDL is to make it easier to perform operations such as the above. Let's take a look at an easier way.

4-Bit Unsigned Adder Using `std_logic_unsigned`

Using the same entity as above, look at the code below and notice how much and where it has been shortened.

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;

entity add is
  generic (width: integer:=4);
  port (
    x: in std_logic_vector((width-1) downto 0);
    y: in std_logic_vector((width-1) downto 0);
    cin: in std_logic;
    sum: out std_logic_vector((width - 1) downto 0);
    cout: out std_logic
  );
end add;

architecture rtl of add is
  signal i_sum: std_logic_vector(width downto 0);
  constant i_cin_ext: std_logic_vector(width downto 1) := (others => '0');
begin
  i_sum <= ('0' & x) + ('0' & y) + (i_cin_ext & cin);
  sum <= i_sum((width-1) downto 0);
  cout <= i_sum(width);
end rtl;

```

The first thing you will notice, at the top of the code, is the reference to the `std_logic_unsigned` package, used for unsigned `std_logic` arithmetic operations. This package contains a procedure called "+" which we use as an addition within the body of the architecture. This "+" takes three unsigned `std_logic_vectors` and adds them, returning a result.

The other should be the use of a generic. A generic lets us produce code that can be changed by the passed parameter. In our case, we let the generic `width` be the bit width of the two numerands, thus making the code scalable to any width of signals.

For this specific example, we take `x` and `y`, concatenate a '0' to the beginning (unsigned logic). For `cin`, we concatenate a vector one less than the generic constant. These are all added with "+" and assigned to the result `i_sum`. We then split `i_sum` into the sum and the carry out. This can be done a number of ways but this is one of them and, as you can see, is much simpler than the previous example. Additionally, with the use of the generic `width`, the component becomes much more reusable, a quality always desired by designers.

4-Bit Simple ALU

Using the same entity as above, look at the code below and notice how easily one can put together an ALU.

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
use ieee.std_logic_arith.all;
-----
entity ALU is
  generic (width: integer:=4);
  port(
    A:      in std_logic_vector((width-1) downto 0);
    B:      in std_logic_vector((width-1) downto 0);
    Sel:    in std_logic_vector(1 downto 0);
    Res:    out std_logic_vector((width-1) downto 0)
  );
end ALU;
-----
architecture behv of ALU is
begin
  process(A,B,Sel)
  begin
    -- use case statement to achieve
    -- different operations of ALU
    case Sel is
      when "00" =>
        Res <= A + B;
      when "01" =>
        Res <= A + (not B) + 1;
      when "10" =>
        Res <= A and B;
      when "11" =>
        Res <= A or B;
      when others =>
        Res <= "XX";
    end case;
  end process;
end behv;
```

Now, you can expand the model to include full ALU. Moreover, you can see how you can access individual bits to generate needed flags.