

# EGC442

## Class Notes

### 3/10/2023

**Baback Izadi**

Division of Engineering Programs

[bai@enr.newpaltz.edu](mailto:bai@enr.newpaltz.edu)



# Test 1

Average	82.5
Median	85.5
MAX	92.0
Minimum	67.0

Consider a rising clock edge that causes 3000 to be written into the PC.

- 1) The 3000 waits at the instruction memory input for the next rising clock edge, at which time the instruction at address 3000 is read out.  
 True  
 False
- 2) After the address 3000 is read into the PC, the 3000 only propagates to the adder.  
 True  
 False
- 3) The 3000 waits at the adder input for the next rising clock edge.  
 True  
 False
- 4) 3001 will be waiting at the PC's input to be written on the next instruction fetch cycle.  
 True  
 False

**Correct**

Because the instruction memory only reads, the instruction memory is like combinational logic. So the read begins as soon as the new address arrives, without waiting for a rising clock edge.



**Correct**

When the 3000 is written into the PC, the 3000 propagates simultaneously to both the instruction memory and the adder.



**Correct**

The adder is combinational logic, so the 3000 enters the adder logic without waiting for a rising clock edge.



**Correct**

The adder adds 4, not 1, because each MIPS word is 4 bytes.



1) The register file always outputs the two registers' values for the two input read addresses.

- True  
 False

2) The register file writes to one register on every rising clock edge.

- True  
 False

3) The design can read from two registers and write to one register during the same clock cycle.

- True  
 False

4) The programmer must take care not to create a program that writes to a register during the same cycle that the same register is read.

- True  
 False

**Correct**

The register file does not wait for a rising clock edge, nor any special control signals, to output those two registers' values.



**Correct**

The write only occurs if the RegWrite input is 1.



**Correct**

Because the design is edge triggered, the read values will be waiting at register inputs to be written on the next rising clock edge.



**Correct**

Instructions like `add $s1, $s1, $s0` (read `$s1` and `$s0`, add values, and write the result to `$s1`) are common. Because the design is edge triggered, the reads will occur, then the add, and the result will be waiting and ready to be written on the next rising clock edge.



Consider the MIPS datapath above. Find the error in each of the following statements.

- 1) An R-type instruction like add uses three datapath units: the register file, the ALU and the data memory.
  
- 2) In addition to the register file and ALU, a load or store instruction also involves the sign extension, data memory and shift left units.
  
- 3) The branch datapath uses the sign extension, shift by 2 and data memory units.
  
- 4) During a load instruction, the mux to the data memory's right would pass the top bottom input.
  
- 5) The mux at the upper right either passes PC + 1 (the normal case), or passes a target address from the instruction (for jumps or branches).

**Correct**

Such an instruction reads register values, operates using the ALU, and writes a result back to a register. The data memory is not involved (no load or store is occurring).

**Correct**

The shifter is used by branch instructions, but is not needed by load or store instructions.

**Correct**


The data memory is not involved in a jump instruction.

**Correct**

The mux's top input comes from the data memory. During a load, the data read from data memory gets loaded into a register in the register file.



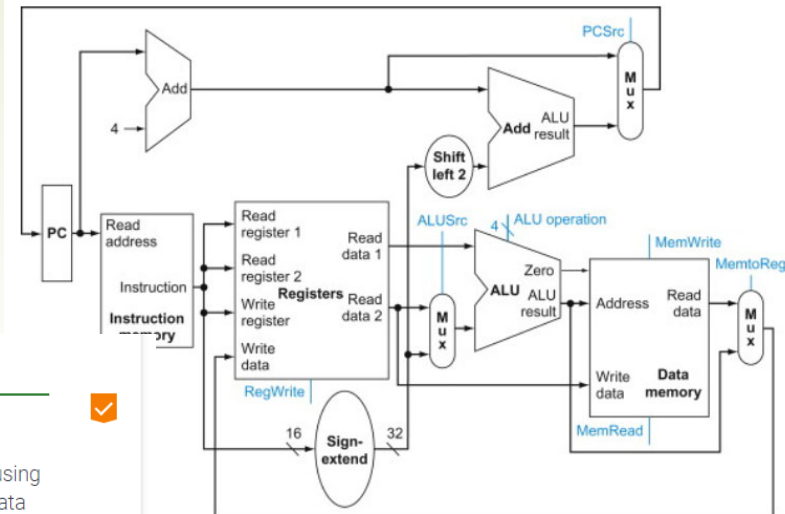
**Correct**

The normal case of fetching the next instruction memory requires  $PC + 4$ , not  $PC + 1$ , since each word is 4 bytes.




addi \$t1, \$a2, 0x45

+6  
45

   


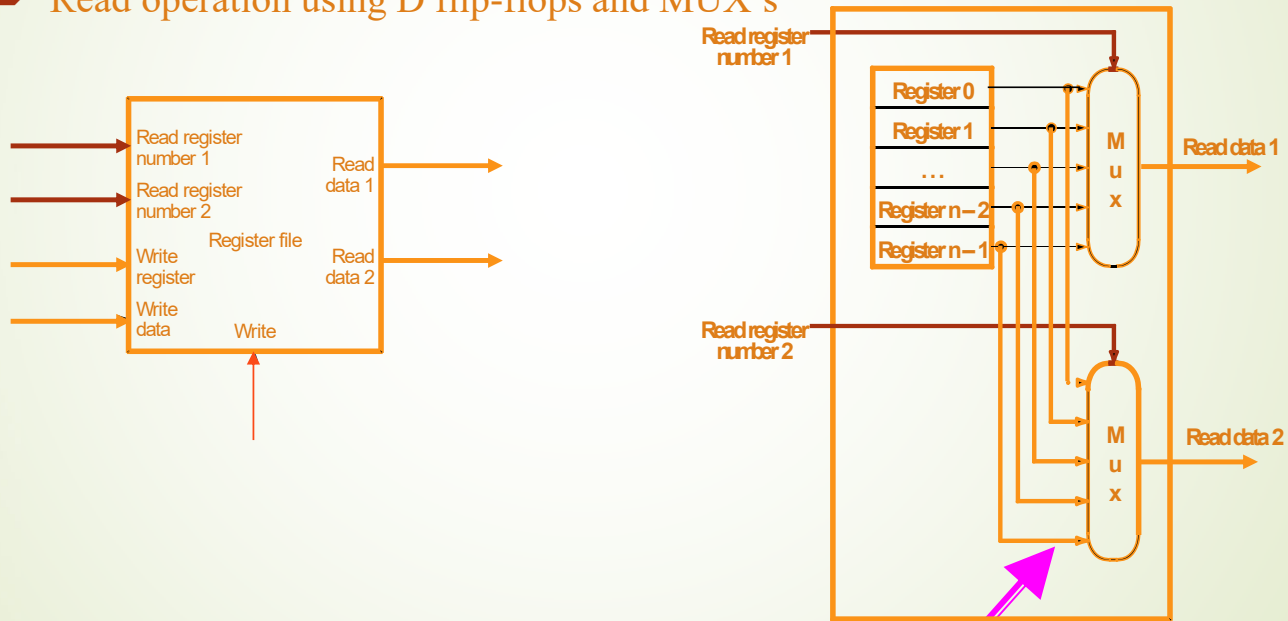
# Register File

- Read operation using D flip-flops and MUX's




*What is the function of "Mux" above?*

# Building the Datapath Of R

  


a. Instruction memory


b. Program counter

 


c. Adder

 


a. Data memory unit

 

b. Sign-extension unit

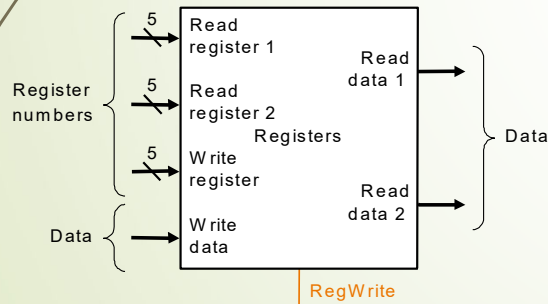


a. Registers

 


b. ALU



 


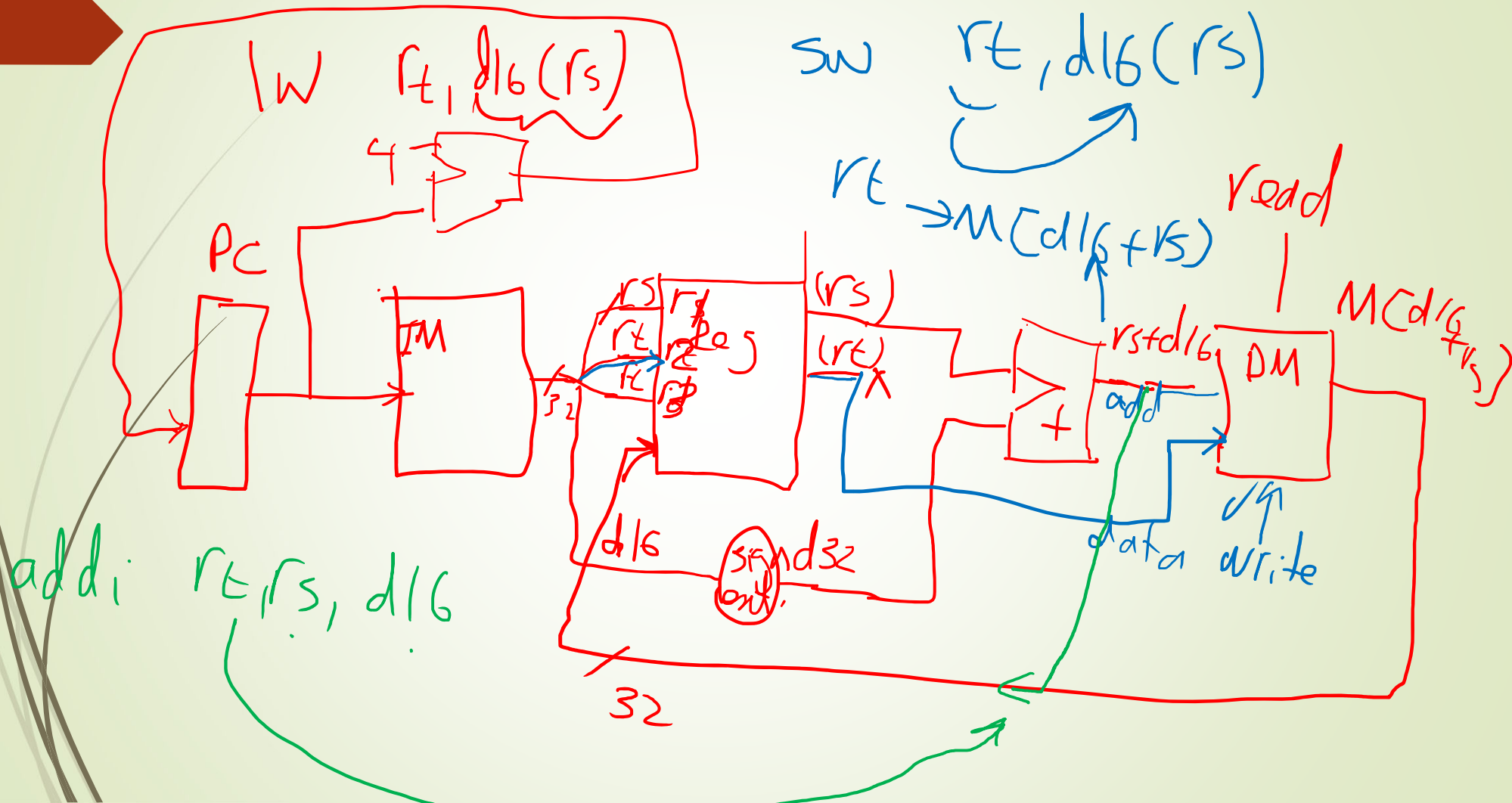10) Draw the data path for only *lw rt, d16(rs)*. Make sure to only use the components that are necessary.



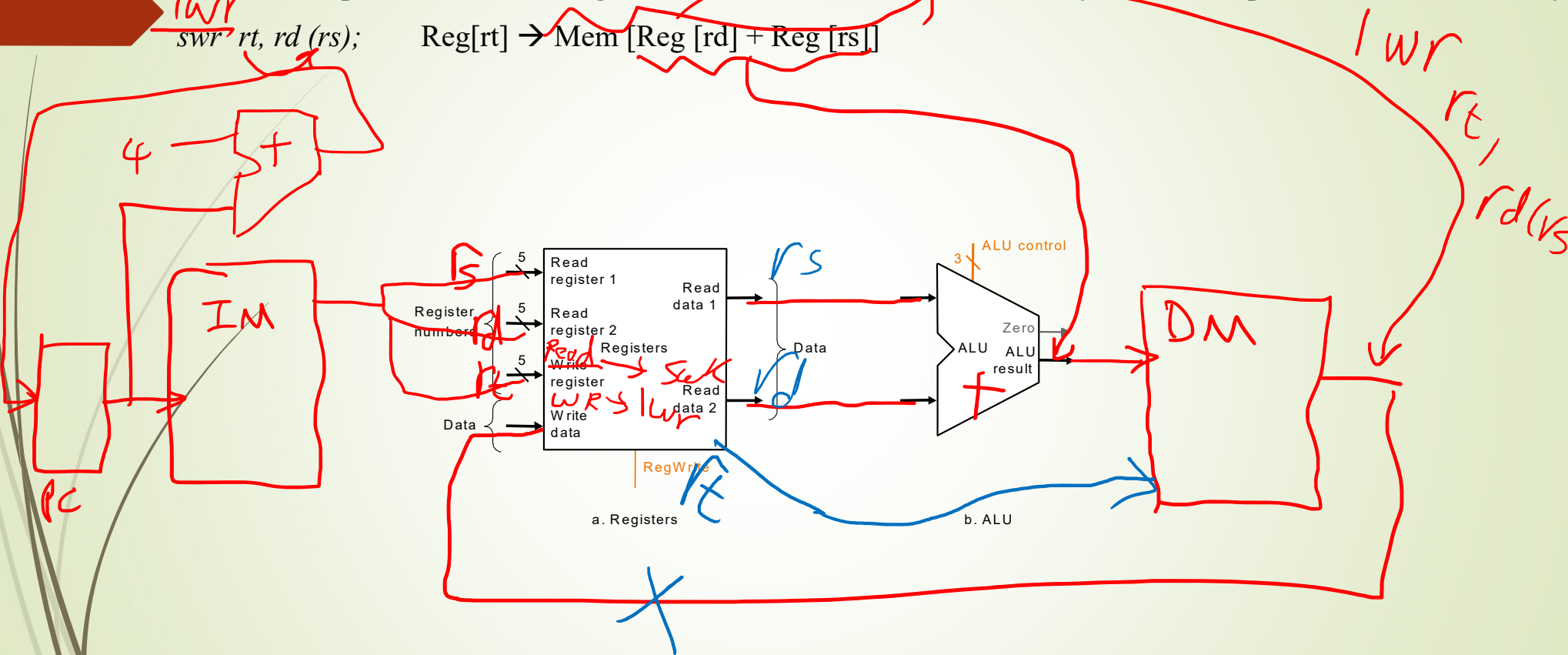11) Draw the data path for the following assumed instruction. Make sure to only use the components that are necessary.

$swr\ rt, rd(rs); \quad \text{Reg}[rt] \rightarrow \text{Mem}[\text{Reg}[rd] + \text{Reg}[rs]]$



12) Draw the data path for the following instruction set:

- *lw* *rt*, *d16*(*rs*),
- *sw* *rt*, *d16*(*rs*),
- *R-type*,
- *bne* *rs*, *rt*, *d16*,
- *swr* *rt*, *rd*(*rs*)

	<i>R<sub>1</sub></i>	<i>R<sub>2</sub></i>	<i>R<sub>W</sub></i>	<i>I<sub>1</sub></i>	<i>I<sub>2</sub></i>	<i>M<sub>W</sub></i>
<i>lw</i> <i>rt</i> , <i>d16</i> ( <i>rs</i> )	<i>rs</i>	X	<i>rt</i>	( <i>rs</i> )	<i>d16</i>	X
<i>sw</i> <i>rt</i> , <i>d16</i> ( <i>rs</i> )	<i>rs</i>	<i>rt</i>	X	( <i>rs</i> )	<i>d16</i>	<i>R<sub>2</sub></i>
<i>R-type</i>	<i>rs</i>	<i>rt</i>	<i>rd</i>	( <i>rs</i> )	( <i>rt</i> )	X
<i>bne</i> <i>rs</i> , <i>rt</i> , <i>d16</i>	<i>rs</i>	<i>rt</i>	X	( <i>rs</i> )	( <i>rt</i> )	X
<i>swr</i> <i>rt</i> , <i>rd</i> ( <i>rs</i> )	<i>rs</i>	<i>rd</i>	<i>rt</i>	( <i>rs</i> )	( <i>rd</i> )	X

