

# EGC442

## Class Notes

### 3/3/2023

**Baback Izadi**

Division of Engineering Programs

[bai@engr.newpaltz.edu](mailto:bai@engr.newpaltz.edu)

# Test 1:


- Chapter 2
  - Performance problems
- Chapter 3
  - MIPS instruction set
  - C to MIPS
  - MIPS to C
  - MIPS to machine code
- Chapter 4
  - Hardware and algorithm for Multiplication
  - Floating Point
  - ALU design

s/t  $r_d, r_s, r_t$

0

$$r_s - r_t > 0$$

s result

 


1

$$r_s - r_t < 0$$




$$54 - (-34) > 0 \quad r_d = 0$$

 

# Making a faster adder Full Addder




Let's look at a 1-bit ALU for addition:

 

$$\text{Sum} = a \oplus b \oplus c_{in}$$

~~$$C_{out} = a b + (a \oplus b) c_{in}$$~~

$$C_{out} = a b + a c_{in} + b c_{in}$$

   

What is the propagation delay of a 32-bit adder?

$$32 \times 2 = 64$$

# Problem with Ripple Carry

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition?
  - two extremes: ripple carry and sum-of-products
- Can you see the ripple? How could you get rid of it?

$$c_1 = b_0c_0 + a_0c_0 + a_0b_0$$

$$c_2 = b_1c_1 + a_1c_1 + a_1b_1$$

$$c_3 = b_2c_2 + a_2c_2 + a_2b_2$$


$$c_4 = b_3c_3 + a_3c_3 + a_3b_3$$

$$c_2 = (b_1 + a_1)(b_0c_0 + a_0c_0 + a_0b_0) + a_1b_1$$

$$c_3 =$$

$$c_4 =$$

Not feasible! Why?

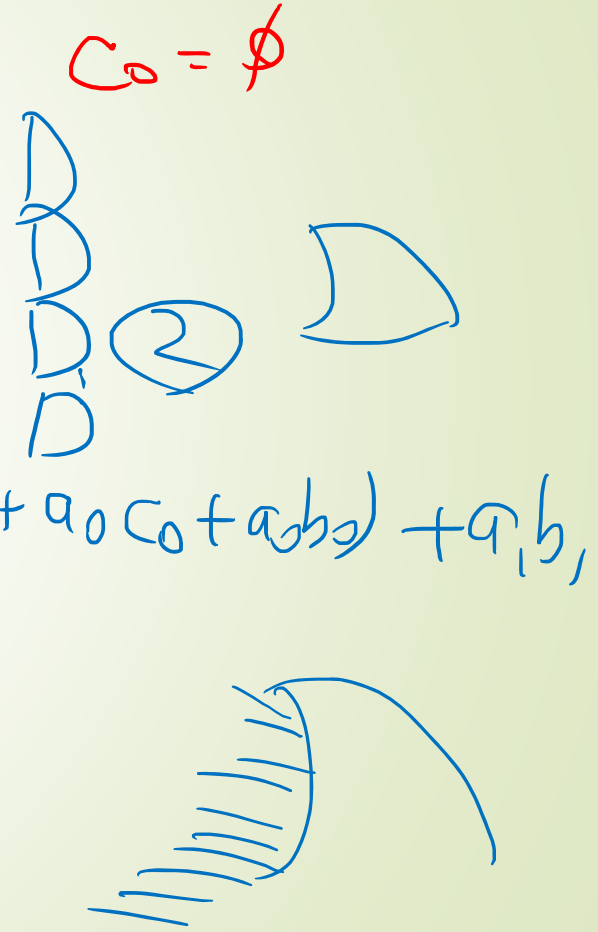

# Carry-lookahead adder

► An approach in-between our two extremes

►  $c_1 = b_0c_0 + a_0c_0 + a_0b_0 = (b_0 + a_0)c_0 + a_0b_0$

► If we didn't know the value of carry-in, what could we do?

► When would we always generate a carry?

$$g_i = a_i b_i$$

► When would we propagate the carry?

$$p_i = a_i + b_i$$

► Did we get rid of the ripple?

$$c_1 = g_0 + p_0c_0$$

$$c_2 = g_1 + p_1c_1$$

$$c_3 = g_2 + p_2c_2$$




$$c_4 = g_3 + p_3c_3$$

$$c_2 = g_1 + p_1g_0 + p_1p_0c_0$$

$$c_3 = g_2 + p_2(g_1 + p_1g_0 + p_1p_0c_0)$$

$$c_4 = g_3 + p_3(g_2 + p_2(g_1 + p_1g_0 + p_1p_0c_0))$$

ripple  
 $4 \times 2 = 8$

   

2. Assume you are asked to design a 64 bit carry lookahead carry adder as indicated below:

a. At the level one, use  $p_i$  and  $g_i$  and  $c_i$ , to express the Boolean function.

b. At the second level use  $P_i$ ,  $G_i$ ,  $C_i$  to express the Boolean function.

c. At the third level use  $P_i'$ ,  $G_i'$ , and  $C_i'$  to express the Boolean function.

$$c_1 = b_0 c_0 + a_0 c_0 + a_0 b_0$$

$$(b_0 + a_0) c_0 + a_0 b_0 \rightarrow c_1 = P_0 g_0 + P_0 c_0,$$

$$c_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 c_0$$

$$c_4 = G_4 + P_4 G_3 + P_4 P_3 G_2 + P_4 P_3 P_2 G_1 + P_4 P_3 P_2 P_1 G_0 + P_4 P_3 P_2 P_1 P_0 c_0$$

$$C_i' = G_i' + G_i' P_i' c_0$$

$$C_i = G_i + P_i G_{i-1} + P_i P_{i-1} G_{i-2} + \dots + P_i P_{i-1} \dots P_0 c_0$$

$$c_1 = g_0 + P_0 c_0$$

$$c_2 = g_1 + P_1 g_0 + P_1 P_0 c_0$$

$$c_3 = g_2 + P_2 g_1 + P_2 P_1 g_0 + P_2 P_1 P_0 c_0$$


$$c_4 = g_3 + P_3 g_2 + P_3 P_2 g_1 + P_3 P_2 P_1 g_0 + P_3 P_2 P_1 P_0 c_0$$

$$C_1 = G_0 + P_0 c_0$$

$$C_2 = G_1 + P_1 G_0 + P_1 P_0 c_0$$

$$C_{32} \leftarrow C_2' P_0'$$



$$C_{48} \leftarrow C_3'$$

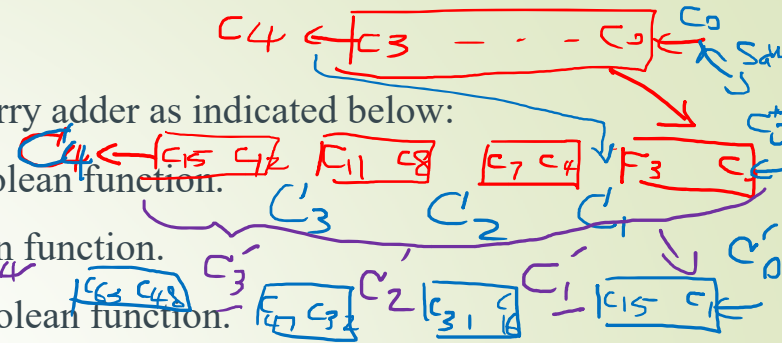

$\underline{16} \times 2 = 32$



Ripple 16 bit

  $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 +$





$D_{-P_i}$   
 $D_{-G_i}$

 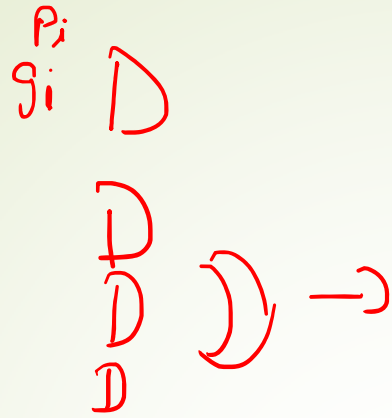

CLA 3 levels (7) 64 bit  
ripple 64 x 2 = 128

# 16 Bit Carry Look Ahead

➤  $g_i = a_i b_i$

➤  $p_i = a_i + b_i$

➤  $c_1 = g_0 + p_0 c_0$

$c_2 = g_1 + p_1 c_1$

➤  $c_2 = g_1 + p_1 g_0 + p_1 p_0 c_0$

➤  $c_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$

➤  $c_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$

➤  $G_0 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$

$P_0 = p_3 p_2 p_1 p_0$

➤  $G_1 = g_7 + p_7 g_6 + p_7 p_6 g_5 + p_7 p_6 p_5 g_4$



$P_1 = p_7 p_6 p_5 p_4$

➤  $G_2 = g_{11} + p_{11} g_{10} + p_{11} p_{10} g_9 + p_{11} p_{10} p_9 g_8$

$P_2 = p_{11} p_{10} p_9 p_8$

➤  $G_3 = g_{15} + p_{15} g_{14} + p_{15} p_{14} g_{13} + p_{15} p_{14} p_{13} g_{12}$

$P_3 = p_{15} p_{14} p_{13} p_{12}$

  

$c_1 = G_0 + P_0 c_0$

$c_2 = G_1 + P_1 c_1$

$c_3 = G_2 + P_2 c_2$

$c_4 = G_3 + P_3 c_3$

$c_5 = G_4 + P_4 c_4$

$c_6 = G_5 + P_5 c_5$

$c_7 = G_6 + P_6 c_6$

$c_8 = G_7 + P_7 c_7$

1. Determine the  $g_i$ ,  $p_i$ ,  $P_i$ , and  $G_i$  values of the following two 16 bit numbers. What is  $C_{out_{15}}$  ( $C_{16}$ )?

$$\begin{array}{r}
 \begin{array}{cccc}
 a_4 & a_3 & a_2 & a_1 \\
 & & & a_0 \\
 0001 & 1010 & 0011 & 0011 \\
 + & 1110 & 0101 & 1110 & 1011 \\
 \hline
 1111 & 1111 & 1111 & 1011 \\
 0000 & a_0 & 0 & 0010 & 0011
 \end{array}
 \end{array}$$

$$p_0 = p_3 p_2 p_1 p_0$$

$$G_0 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$$

$$p_i = a_i + b_i$$

$$g_i = a_i b_i$$

$c_i$

Repeat Using  $P_i$  and  $G_i$

$$P_0 = 0 \quad P_1 = ( \quad P_2 = ( \quad P_3 = ($$

$$G_0 = 0$$

$$G_1 =$$

$$G_2 =$$

$$G_3 =$$

$$C_4 =$$

3. One simple way to model time for logic is to assume each AND and OR gate takes the same time for a signal to pass through it. Time is estimated by simply counting the number of gates along the longest path through a piece of logic. Compare the number of gate delays for the critical paths of the following 64-bit adders

- a. Ripple carry 128
- b. three-level carry lookahead 7
- c. Carry lookahead at level one, and ripple carry between 4 bit modules ~~12~~  $16 \times 3 = 48$
- d. Carry lookahead at levels one and two, and ripple carry between 16 bit modules. 20

