



















Self Dual Circuit

□ Alternative logic is well suited for self-dual

• $f(x) = \overline{f(x)} \rightarrow \overline{f(x)} = f(\overline{x})$

□ Any Combinational circuit with n input variables can be transformed into a self-dual with no more than n+1 inputs

• $f_{sd}(x) = x_{n+1}f(x) + \overline{x_{n+1}}f_d(x)$

• Where $f_d(x)$ is the dual of f(x)

 \Box Example: $f = A\overline{B} + BC$

- $f_d = (A + \overline{B})(B + C)$
- $f_{sd} = D(A\overline{B} + BC) + \overline{D}(A + \overline{B})(B + C)$