

First Name: _____ Last Name: _____

Problem 1 (20 Points)

A cyclic code is to be based on the Generator polynomial $X^6 + X^5 + X^3 + 1$.

- Generate a codeword for the input data 10101.
- Using logic gates, design an appropriate encoder and decoder the given generator.

Problem 2 (20 Points)

- Using full adders and basic gates, design a $7N$ code encoder, where N is a 3-bit binary number.
- Based on the code distance, determine if the code has error detecting and/or error correcting capability.

Problem 3 (20 Points)

Consider a low-cost residue code based on module 7.

- Show how do you obtain residue-7 check bits of $X_7 X_6 X_5 X_4 X_3 X_2 X_1 X_0$ using recursive addition technique?
- What is the theoretical base for this easy encoding process?

Problem 4 (20 Points)

Convert 0 to 29 to RNS using modules [2,3,5,7].


- For the given range, does the code has the capacity for error detection? If yes, how many bits?
- For this given range, does the code has the capacity for error correction? If yes, how many bits?

Problem 5 (15 Points)

Design a totally self-checking checker with 6 inputs. After showing the internal circuitry of one module, you may use block form to implement the design of an 6 input unit.

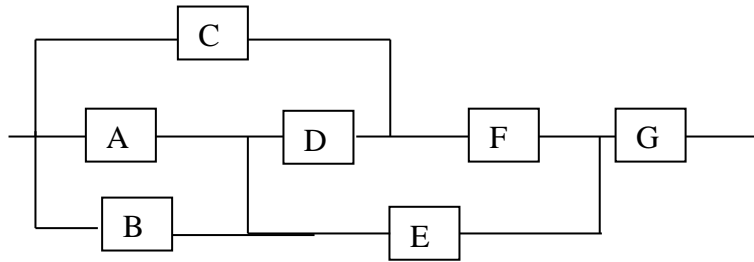Problem 6 (25 Points)

- Determine an exact expression for the reliability of the following system, given that the reliability of each component X is R_X .
- Assume that $R_A=R_B=R_C=R_D=R_E=R_F=R_G=R$, determine the reliability of the system in term of R .
- Determine the upper limit approximation of the system reliability.



Problem 7 (20 Points)

Using the combinatorial model, determine the reliability of a simplex, TMR, and 5MR systems as a function of reliability of a simplex system, $R(t)$. You may assume a fault-free voter. Using MATLAB, plot the reliability of the three systems versus R and comment on their relative reliabilities.

Problem 8 (25 Points)

Using Markov model, determine the discrete solution for the reliability of a 5MR system with λ failure rate and μ repair rate. You may assume that the system initially is fault free. Moreover, you may assume that once the 5MR has 3 more faulty modules, it enters a failed state that can't be repaired. Using MATLAB plot $R(t)$ from 0 to 5 hours using

- a. $\Delta t = 0.01, \lambda = .01$ and $\mu = .01$
- b. $\Delta t = 0.01, \lambda = .1$ and $\mu = .1$
- c. $\Delta t = 0.01, \lambda = .1$ and $\mu = .01$

Due: Friday 3/9/ 2017