

## Solutions

### Chapter 11

#### Problem 1

##### Part a

$$I = \mathcal{E}_m/Z,$$
$$Z = \sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C}\right)^2}$$

As there is no resistor,  $R = 0$ . As there is no capacitor,  $C = \infty$  or  $\frac{1}{\omega_d C} = 0$ . So  $Z = \omega_d L$ , and

$$I = \frac{\mathcal{E}_m}{\omega_d L} = 4.17 \times 10^{-3} \text{ A.}$$

##### Part b

$$i = I \sin(\omega_d t - \phi)$$

where  $\phi$  is given by:

$$\tan \phi = \frac{\omega_d L - \frac{1}{\omega_d C}}{R} = \infty.$$

So,  $\phi = \pi/2$  and

$$i = I \sin(\omega_d t - \pi/2) = -I \cos(\omega_d t)$$

Hence,  $i$  is a maximum when  $\omega_d t = \pi, 3\pi, 5\pi, \dots$ . At these times  $\sin(\omega_d t) = 0$ . So, at these times,  $\mathcal{E} = \mathcal{E}_m \sin(\omega_d t) = 0$ .

#### Problem 2

##### Part a

$$I = \mathcal{E}_m/Z,$$
$$Z = \sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C}\right)^2}$$

As there is no resistor,  $R = 0$ . As there is no inductor,  $L = 0$ . So  $Z = 1/(\omega_d C)$ , and

$$I = \mathcal{E}_m \omega_d C = 5.00 \times 10^{-2} \text{ A.}$$

## Part b

$$i = I \sin(\omega_d t - \phi)$$

where  $\phi$  is given by:

$$\tan \phi = \frac{\omega_d L - \frac{1}{\omega_d C}}{R} = -\infty.$$

So,  $\phi = -\pi/2$  and

$$i = I \sin(\omega_d t + \pi/2) = I \cos(\omega_d t)$$

Hence,  $i$  is a maximum when  $\omega_d t = 0, 2\pi, 4\pi, \dots$ . At these times  $\sin(\omega_d t) = 0$ . So, at these times,  $\mathcal{E} = \mathcal{E}_m \sin(\omega_d t) = 0$ .

## Problem 3

### Part a

The resonant frequency is

$$\omega_d = 1/\sqrt{LC} = 500 \text{ rad/sec}$$

### Part b

The current amplitude is

$$I = \frac{\mathcal{E}_m}{Z} = \frac{\mathcal{E}_m}{\sqrt{R^2 + (X_L - X_C)^2}}$$

At resonance,  $X_L = X_C$ , hence,

$$I = \frac{\mathcal{E}_m}{R} = \frac{10}{4} = 2.50 \text{ A}$$

Also at resonance

$$\omega_d = \frac{1}{\sqrt{LC}}$$

and the voltage amplitude across the inductor is

$$V_L = IX_L = I\omega_d L = \frac{IL}{\sqrt{LC}} = I\sqrt{\frac{L}{C}} = 2500 \text{ V}$$

### Part c

The inductor may have a higher voltage across it than the source because the capacitor voltage can partially (or completely in case of resonance) cancel the inductor voltage.

### Problem 4

$$\tan \phi = \frac{X_L - X_C}{R}$$

Hence,

$$R = \frac{X_L - X_C}{\tan \phi} = \frac{\omega_d L - \frac{1}{\omega_d C}}{\tan \phi} = \frac{2\pi f_d L - \frac{1}{2\pi f_d C}}{\tan \phi} = 140 \ \Omega$$

### Problem 5

Part a

$$Z = \sqrt{R^2 + \left(\omega_d L - \frac{1}{\omega_d C}\right)^2} = 67 \ \Omega$$

Part b

$$I = \frac{\mathcal{E}_m}{Z} = 6.7 \text{ A}$$

Part c


The phase constant is given by

$$\tan \phi = \frac{\omega_d L - 1/(\omega_d C)}{R} = 1.35$$

Hence,

$$\phi = 53^\circ$$

### Problem 6

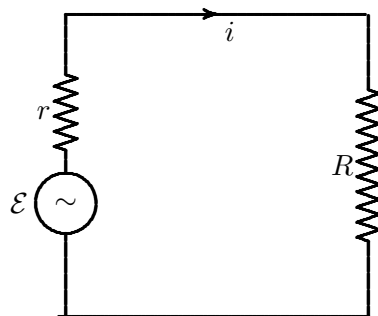

Power dissipation in  $R$  is

$$P = I_{\text{rms}}^2 R$$

where

$$I_{\text{rms}} = \frac{\mathcal{E}_{\text{rms}}}{Z} = \frac{\mathcal{E}_{\text{rms}}}{r + R}$$

So,

$$P = \mathcal{E}_{\text{rms}}^2 \frac{R}{(r + R)^2}$$

The value of  $R$  for which  $P$  is maximum, must obey the maxima condition from calculus:  $\frac{dP}{dR} = 0$ . This gives:

$$\mathcal{E}_{\text{rms}}^2 \left[ \frac{1}{(r + R)^2} - \frac{2R}{(r + R)^3} \right] = 0.$$

The solution to this equation is:

$$r = R.$$

## Problem 7

The voltage of the secondary is

$$V_s = N_s \frac{V_p}{N_p} = 4.0 \text{ V}$$